Electronic Engineering

Incorporating . . . ELECTRONICS, TELEVISION & SHORT WAVE WORLD

VOL. 21 No. 262 DECEMBER 1949 PRICE 2/-

STEREOPHONIC
AMPLIFIER

VORTEXION
LIMITED

257-261 THE BROADWAY, WIMBLEDON, LONDON, S.W.19.

Telephones : LIBerty 2814 and 6242-3 Telegrams : " Vortexion, Wimble, London "

RADIO ENGINEERS — *let us send you this publication*

It contains up-to-date information on BICC Radio Frequency cables which have been developed particularly for use with television receivers.

The construction of the three main types of cable is described and illustrated.

Send to-day for Publication 244 R

BRITISH INSULATED CALLENDER'S CABLES LIMITED
NORFOLK HOUSE, NORFOLK STREET, LONDON, W.C.2

Vacanc
ments a
Engage

VANC
various
nexion
installa
electron
should
should
or equi
three y
Governm
possessi
A lower
Certifica
ments w
ities lat
salary sc
be at th
each yea
Rates o
quoting
Nationa
(K), Yo
applicat
by 9th

THE M
from :
BR); M
C12/49/
Royal A
research
and the
salary
£495–£6
(at age
lower.)
qualifica
with air
performa
work and
and ra
instrume
Applican
these fie
Certificat
in Mathe
There ar
tion wor
are unes
establish
tion for
Register
quoting
16th De

MINIST
unestabli
Royal A
Candidat
good Ho
matical
display,
pulse-cod
qualificat
to £1,17
F.S.S.U.
Technical
Kingsway
should b
1949.

MINIST
Physicist
posts in
establishm
qualificat
but exper
Physicists
in produc
or field t
measurem
mathema
are desir
qualificati
normally
E.O. und
£895 (me

▲

CLASSIFIED ANNOUNCEMENTS

The charge for these advertisements at the LINE RATE (if under 1" or 12 lines) is: Three lines or under 7/6, each additional line 2/6. (The line averages seven words.) Box number 2/- extra, except in the case of advertisements in "Situations Wanted," when it is added free of charge. At the INCH RATE (if over 1" or 12 lines) the charge is 30/- per inch, single column. Prospectuses and Company's Financial Reports £14 0s. 0d. per column. A remittance must accompany the advertisement. Replies to box numbers should be addressed to: Morgan Bros. (Publishers), Ltd., 28, Essex Street, Strand, London, W.C.2, and marked "Electronic Engineering." Advertisements must be received before the 14th of the month for insertion in the following issue.

OFFICIAL APPOINTMENTS

Vacancies advertised are restricted to persons or employments excepted from the provisions of the Control of Engagement Order, 1947.

VANCANCIES exist for Production Inspectors at various Admiralty establishments for duties in connexion with the manufacture, inspection, test and installation of mechanical and electrical (including electronic) equipment for H.M. ships. Candidates, who should be at least 25 and preferably not more than 35, should have completed a full engineering apprenticeship or equivalent training, followed by a minimum of three years' relevant experience in industry or in Government service, and should preferably be in possession of a Higher National Certificate or equivalent A lower qualification such as the Ordinary National Certificate might, however, be considered. Appointments will be temporary but there may be opportunities later of competing for permanent posts. The salary scale is £500 × 20–£625 per annum and entry will be at the minimum, subject to a deduction of £20 for each year by which the age of entry falls short of 30. Rates outside London are a little lower. Write, quoting D374/49/BR to the Ministry of Labour and National Service, Technical and Scientific Register (K), York House, Kingsway, London, W.C.2, for application form which must be returned completed by 9th December, 1949 W 2099

THE MINISTRY OF SUPPLY invites application from: Electrical, Electronic Engineers (Ref. D6/49/BR); Mechanical and Aeronautical Engineers (Ref. C12/49/BR) for posts in the following grades at the Royal Aircraft Establishment, Farnborough and other research and development establishments in S. England and the Midlands: Senior Experimental Officer, salary range £705–£895; Experimental Officer, £495–£645; Assistant Experimental Officer, £220 (at age 18)–£460, (rates for women are somewhat lower.) Grade and starting pay assessed on age, qualifications and experience. Duties mainly connected with aircraft structures, flutter and vibration and performance, aerodynamics, including wind tunnel work and flight testing, armaments, combustion, radio and radar, electronic technique, measurements, instruments and instrumentation, control gear, etc. Applicants should have practical experience in one of these fields and possess at least Higher National Certificate, Higher School Certificate or equivalent, in Mathematics or a science or engineering subject. There are a few posts for duties on library and information work connected with the above fields. The posts are unestablished but opportunties to compete for established posts may occur later. Write for application form, obtainable from Technical and Scientific Register (K), York House, Kingsway, London, W.C.2, quoting appropriate reference above. Closing date on 16th December, 1949 W 2102

MINISTRY OF SUPPLY invites applications for unestablished post Principal Scientific Officer at the Royal Aircraft Establishment, Farnborough, Hants. Candidates should be at least 31, and should possess a good Honours Degree in Physics with good mathematical knowledge and research experience on radar display, digital and analogue computors, pulse and pulse-coded communications. Salary assessed on age, qualifications and experience, within the range £910 to £1,177 (men) or £790 to £1,016 (women) plus F.S.S.U. benefits. Write quoting A264/49/BR, to Technical and Scientific Register (K), York House, Kingsway, London, W.C.2. for application form, which should be returned completed by 20th December, 1949. W 2103

MINISTRY OF SUPPLY invites applications from Physicists and Electrical Engineers for unestablished posts in the Experimental Officer class at research establishments in Southern England. The minimum qualification is Higher School Certificate or equivalent, but experimental ability is of prime importance and, for Physicists, a Degree is desirable. Experience essential in production of electronic equipment including radar, or field trials, or general physical testing or radiation measurement. In one post a sound knowledge of mathematics, and in another drawing office experience, are desirable. Grade and salary assessed on age, qualifications and experience. Candidate will not normally be considered for S.E.O. under age 35 or for E.O. under 28. Senior Experimental Officer, £705–£895 (men) ;Experimental Officer £495-£645 (men), Assistant Experimental Officer £220–£460 (men). Rates for women are slightly lower. London rates are higher. Write, quoting A273/49/BR to Technical and Scientific Register (K), York House, Kingsway, London, W.C.2, for application form which should be returned completed by 9th December, 1949 W 2115

BRITISH ELECTRICITY AUTHORITY, South Eastern Division. Applications are invited for the position of General Assistant Engineer (Communications). Applicants should possess a Degree in Electrical Engineering or Higher National Certificate in Electrical Engineering or equivalent, and have had experience of manual and automatic telephone equipment. A sound knowledge of electronics is desirable. The successful applicant will be required to reside in the Brighton area. Salary will be in the range of £392 8s. and £523 13s. p.a., and is provisional pending negotiations with appropriate organisations. Forms of application may be obtained by sending a stamped addressed foolscap envelope to the Divisional Secretary, British Electricity Authority, South Eastern Division, Lower Ham Road. Kingston-on-Thames, Surrey, and must be returned completed, with copies of two recent testimonials not later than 10th December, 1949 W 2116

MINISTRY OF SUPPLY invites applications from Physicists or Electrical Engineers for posts at a research establishment in South Midlands. Duties connected with development of radar equipments for R.A.F., including preliminary investigation, proving of designs and supervision of development contracts with industry. A good Honours Degree and appropriate experience in industry or a Government Establishment essential. Posts are unestablished but carry F.S.S.U. benefits. Grade and starting salary according to age, qualifications and experience. Normal minimum age for P.S.O. is 31 and for S.S.O. is 26. Principal Scientific Officer, £910–£1,177; Senior Scientific Officer, £670–£860. Rates for women are somewhat lower. Write, quoting A280/49/BR, to Technical and Scientific Register (K), York House, Kingsway, London, W.C.2., for application forms which should be returned completed by 21st December, 1949. W 2121

MINISTRY OF SUPPLY invites applications from Chemists or Engineers for a post as Experimental Officer in a research and development establishment near London. The work involves the design and use of electronic and other instruments required for the investigation of combustion and allied processes. Candidates must possess at least the Higher School Certificate or its equivalent and have a sound knowledge of Chemistry, combined with engineering experience. Ability to direct industrial staff is essential. Inclusive salary range, £495–£645. Rates for women are somewhat lower. The appointment is unestablished but opportunities to compete for established posts may occur later. There are prospects for advancement in salary up to £895. Application forms obtainable from, Technical and Scientific Register (K), York House, Kingsway, London, W.C.2., quoting F.805/49/B,R. Closing date 17th December, 1949 W 2122

SITUATIONS VACANT

THE BRITISH THOMSON-HOUSTON CO. require a Junior Design Engineer for work of exceptional interest on mercury-arc rectifiers. Good prospects for able man. Previous rectifier experience not necessary, but applicants should have Honours Degree in Electrical Engineering and some works training. Salary according to qualifications. Apply, stating age, and details of training and experience to—Manager, Rectifier Engineering Dept., The British Thomson-Houston Co. Ltd., Rugby. W 2029

JUNIOR TRANSFORMER DESIGNER required. Air and oil cooled transformers up to 10 KV. Permanent progressive position. Apply: London Transformer Products Ltd., Cobbold Estate, Cobbold Road, Willesden, N.W.10. W 2031

A QUALIFIED ENGINEER or Physicist required to work on factory design and production problems in modern transmission valve factory. Alternatively, a senior man with extensive valve factory experience would be considered. Salary ranging from £600 to £800 per annum according to qualifications and experience. Write Box W 5857, A.K. Advtg., 212a, Shaftesbury Avenue, W.C.2. W 2063

GRADUATE PHYSICISTS or Electrical Engineers. Several vacancies exist for men of ability in development laboratory of electric lamp works in Yorkshire. Knowledge of high vacuum technique and/or A.C. measurements will be an advantage. Good prospects for men wishing to make a career in industry. Salary range £400–£550 according to experience. Send full particulars of training and experience to Box W 2060. W 2060

BUSH RADIO LTD. Applications are invited from Engineers and Assistants for positions in the following branches: (a) Communications and domestic radio development; (b) Television development; (c) Test gear development. Apply in writing, giving age, qualifications, details of experience, salary required etc., to the Personnel Manager, Bush Radio Ltd., Power Road, Chiswick, W.4. W 2051

ELECTRONIC RESEARCH and Development Engineers required. First Class Honours Degree or equivalent preferred. Vacancies for Senior Engineers with industrial experience and for juniors. Interesting new projects. Pension Scheme. Apply, stating age, qualifications, experience and salary required, to Personnel Manager, Fairey Aviation Company Ltd., Hayes, Middlesex. W 2036

LABORATORY TECHNICIAN for Medical Research Council, Neurophysiological Laboratory in London. Sound knowledge of basic electronics essential. Experience in metal work, photography and experimental techniques preferred. Salary with superannuation and excellent prospects. Box W 2130. W 2130

YOUNG LABORATORY ASSISTANT required, with qualifications up to Intermediate or National Certificate standard, for radio frequency measurement work. Wage according to age and qualifications. Facilities available for part-time study. Apply Secretary, British Rayon Research Association, Barton Dock Road, Urmston, Manchester. W 1012

SENIOR TECHNICAL SALES Representative with experience of communications systems utilising V.H.F., H.F. or microwave equipments. Technical qualifications not essential but sales experience and knowledge of operating and installing communications equipments required. State full details including age and salary required to Box W 2082. W 2082

ELECTRICAL ENGINEER required for the design of complete power supplies for airborne radio equipment. Power up to 1 KW, 800-2,400 cycles. Qualifications: Degree or equivalent in Physics or Electrical Engineering with experience in the above or allied fields including transformer design and voltage stabilization problems. Please write, giving full details to Personnel Department, E.M.I. Engineering Development, Ltd., Blyth Road, Hayes, Middlesex. W 2083

TECHNICAL WRITER required (North London district) for manuals on electronic instruments, radio navigation aids and communication equipment; preferably with a Degree in Physics or Electrical Engineering and experience on installation or maintenance of radar. Write, stating salary required, to Box W 5954, A.K. Advtg., 212a, Shaftesbury Avenue, W.C.2. W 2084

ELECTRONIC ENGINEERS required for progressive posts as Design Engineers. Qualifications: Degree or equivalent in Electrical Engineering or Physics with three years' or more actual design experience in one of the following fields: (a) U.H.F; (b) V.H.F.; (c) Pulse technique; (d) Recording equipment (disk, film or tape). Please write giving full details to Personnel Department, E.M.I. Engineering Development Limited, Blyth Road, Hayes, Middlesex. W 2086

MARCONI'S WIRELESS TELEGRAPH require for their Works at Chelmsford, a Senior Engineer to take charge of the research and development of domestic television receivers. Applicants who must have had extensive experience in this class of work and a capacity for leading a development team should write giving full particulars quoting Ref. 296, to Central Personnel Services, English Electric Co. Ltd., 24/30, Gillingham Street, Westminster, S.W.1. W 2087

CLASSIFIED ANNOUNCEMENTS (Cont'd.)

HELLESDON HOSPITAL, Norwich. Research Assistant required for electro-encephalograph department. Salary £500 × 25 to £600. Applications to, and further particulars from, Medical Superintendent. W 2085

THE ROYAL TECHNICAL COLLEGE, Glasgow. Department of Electrical Engineering. Applications invited for a Senior Lectureship in Electronics. Work to include lecturing to Degree classes, and supervision of post-graduate research. Research experience, preferably in ultra high-frequency work, an advantage, and individual research work will be encouraged. Salary scale £700 × £25–£950, with placing for previous experience and qualifications. Further information and application forms from the Secretary. W 2089

LEADING COMPONENT Manufacturers situated Southern Scotland require Chief Inspector possessing drive and initiative. Applicants must be sound technicians with qualifications at least equivalent to inter-B.Sc., and with experience of modern testing technique. Duties would include dealing with Government Inspection Departments. Initial training period in London. Write stating experience and salary required to Box W 2090. W 2090

MUIRHEAD & CO. LTD., require an Engineer or Physicist to investigate and report on the applications of their instruments in industry and research. A wide knowledge of measuring techniques, the ability to discuss measurement problems with specialist research workers, and an aptitude for writing clear English are essential, whilst education to Graduate standard is desirable. The position is in the Sales Department and is permanent. It offers a salary in accordance with age, qualifications and experience, and scope for advancement. Applicants should send full details of their training and past career to Muirhead & Co. Ltd., Elmers End, Beckenham, Kent. W 2091

CHIEF DRAUGHTSMAN required for light engineering development organisation near Esher, Surrey. Must be a man of considerable experience. Good salary, interesting work and excellent working conditions are offered. Please reply to Box W 2092 W 2092

DEVELOPMENT ENGINEERS with industrial design experience in light engineering required to work near Esher, Surrey. Good salaries and excellent working conditions are offered to qualified men. The work is of an important and interesting character with ample opportunities for advancement in a new organisation. Please reply to Box W 2093 W 2093

A FEW UNUSUAL opportunities occur in the laboratories of Ferguson Radio Corporation Ltd., for Senior and Junior Development Engineers for work on domestic radio and television receivers and electronic equipment for Government services. Applicants must possess a University Degree, preferably in Engineering, or equivalent qualifications. Designer-Draughtsmen are also required for similar work; previous experience essential. Excellent prospects for keen, enthusiastic men. Write with full details to Chief Engineer, Ferguson Radio Corporation, Ltd., Great Cambridge Road, Enfield. W 2094

STANDARD TELEPHONES AND CABLES invite applications for the following situations in the Chemical Laboratory of their valve works at Footscray, Sidcup, Kent. (1) Research Chemist; man between 30 and 35 years, for development and research work on problems relating to thermionic valves and cathode ray tubes. Essential to have a University Degree or Diploma and some experience of this kind of work. (2) Assistant Chemist; man 20/25 years with University Degree or Diploma to assist in problems relating to thermionic valves and cathode ray tubes. Experience of this type of work desirable, but not essential. Good salaries will be paid according to qualifications to those engaged. Applications for the above situations should give full details and be addressed to the Personnel Officer at the above address. W 2096

TOLL PLANT SUPERINTENDENT (Brazil). The Advertiser wishes to thank those applicants who answered the advertisement for this position under Box E.E. 409, at 191, Gresham House, E.C.2, and would state that those applicants whose qualifications were considered suitable have now been advised. W 2097

SENIOR ELECTRONIC Research Engineers required for development of (a) Communication equipment up to 400 Mc/s; (b) H.F. Signal Generators; (c) Aerial systems; (d) Industrial electronic equipment; (e) Development of components. London area. Salary and status commensurate with qualifications and experience. Write in confidence, stating age, full details of qualifications and experience, to Chief Engineer c/o Box W 2112 W 2112

ADVERTISEMENT MANAGER wanted for the monthly technical journal "Electronic Engineering." Must have experience of advertising salesmanship and be capable of running department. Applicants having acquaintance with products of manufacturers and knowledge of electronic industry will be given preference. Send full particulars of experience and age to: Staff Director, Morgan Brothers (Publishers) Ltd., 28, Essex Street, Strand, W.C.2. W 2095

ELECTRICAL ENGINEER required for design and development work on fractional H.P. and other small electric motors. Qualifications: Degree in Electrical Engineering or equivalent with about three years' or more experience in this field. Salary according to age and qualifications. Write giving full details of experience and qualifications to Personnel Dept., E.M.I. Engineering Development Ltd., Blyth Road, Hayes, Middlesex. W 2100

ENGLISH ELECTRIC invite applications from Electrical Engineers for appointments at their Nelson Research Laboratories, Stafford. Applicants should have a sound knowledge of heavy electrical engineering, and experience in the operation and maintenance of heavy electrical plant. A Degree in Electrical Engineering is essential, and an interest in development desirable. Successful candidates will be required for special duties in connexion with short circuit testing. Applicants should write giving full information quoting Ref. 299, to Central Personnel Services, English Electric Co. Ltd., 24/30, Gillingham Street, Westminster, S.W.1. W 2101

YOUNG MAN with B.Sc. or Higher National Certificate in Electrical Engineering required, preferably with some knowledge of measurements to carry out electrical and magnetic measurements on all kinds of special alloys and the application thereof. Full particulars to Box W 2104 W 2104

PHYSICISTS OR ELECTRICAL ENGINEERS. Vacancies exist in the electronics and electrical departments. Subjects covered include thermionic emission, secondary emission, electrical contact phenomena, electronic recording and controlling devices, electromagnetic systems. Age 21-26. Experience not essential except in the case of thermionic emission when some previous work on electron-emitting devices would be preferable. Salary in accordance with age and experience. Apply, in writing, to British Scientific Instrument Research Association, "Sira," Southill, Chislehurst, Kent. W 2105

ENGLISH ELECTRIC invite applications from Electrical Engineers for appointments in the high voltage section of the Nelson Research Laboratories, Stafford. Applicants should have a sound knowledge and experience of H.V. problems and heavy electrical equipment. A Degree in Electrical Engineering is desirable and applicants must be interested in research and development. Write giving full particulars, quoting Ref. 229 to Central Personnel Services, English Electric Co. Ltd., 24/30, Gillingham Street, Westminster, S.W.1. W 2106

APPLICATIONS ARE INVITED by leading manufacturers of radio equipment from young men with electronic experience for the following vacancies: (a) Test and installation of broadcast radio, television and V.H.F. gear. (b) Manufacture of equipment and components. Selected personnel will receive specialised factory training and must be prepared to travel in Great Britain and to serve overseas for short periods. Write giving brief particulars of education and experience to Box W 2107 W 2107

DRAUGHTSMAN required for radio technical handbook work. Ability to produce first-class diagrams from rough notes is essential. Good prospects, permanency and superannuation scheme. Apply stating age, qualification, experience and salary required, to The Secretary, Marconi's Wireless Telegraph Co. Ltd., New Street, Chelmsford. W 2110

A PROGRESSIVE, rapidly expanding organisation, requires an Engineer with an intimate knowledge of electronics to undertake duties including design of mechanical and electrical equipment and instruments, practical investigations, preparation of reports, liaison with other organisations. Only applicants who can work on their own initiative and are capable of taking responsibility need apply. Excellent prospects for promotion. Full particulars including salary required should be sent to Box W 2111. W 2111

TECHNICAL ASSISTANT required by Airmec Laboratories Ltd., Cressex, High Wycombe for their Mechanical Engineering Laboratory. Applicants should have had previous experience in light engineering and electro-mechanical engineering and have technical qualifications to the Higher National Certificate standard in Mechanical Engineering. Applications should be addressed to the Personnel Manager, stating age, qualifications, experience and salary required. W 2120

TELEVISION DESIGN ENGINEER required by company in London for work on new television systems. Degree or equivalent in Electrical Engineering and previous television experience essential. Salary £700 p.a. or higher for suitably qualified candidates. Box W 2108 W 2108

COIL DESIGNER. Experienced engineer required for design of low frequency coils and small power transformers, by laboratory in Esher area. Must be able to see designs through to production stage. This is a progressive and permanent appointment offering excellent working conditions in pleasant surroundings. State full details to Box W 2109 W 2109

DESIGNER for small transformers, preferably with knowledge of the application of transformers and chokes to radio circuits. Also required, designer for power transformers up to 500 KVA, preferably experienced, but man with good electrical qualifications might suit. Merseyside area. State age, qualifications and present position. Box 2113. W 2113

ENGINEER wanted, under 30 years. Applicants should be near Degree standard in Mechanical and Electrical Engineering subjects and have served an apprenticeship. Good practical knowledge, preferably on light work such as domestic appliances, small motors and compressors. Knowledge of thermodynamics an advantage. Merseyside area. State age, qualifications and experience. Box W 2114 W 2114

TECHNICAL REPRESENTATIVE required by manufacturers of high class electronic and industrial measuring instruments in West London area. Applicants must have initiative, experience and some technical knowledge. Good future for right man. Box W 2117 W 2117

ENGINEERS required for servicing radar equipment, technical qualifications—Higher National Certificate or Degree. Previous experience on electronics or radar desirable. Commencing remuneration up to £400 per annum depending on experience or qualifications. Apply: Construction Department, The British Thomson-Houston Co. Ltd., Rugby W 2118

SPECIALITY Radio-Telephone Salesman, salary, comm., expenses; Senior and Junior Development Engineers and Draughtsmen for radio, radar, electronics etc. Service Engineers: radio, television, radar, electronics; wiremen (skilled and semi-skilled), radar, radio, instruments; H.F. repairers, testers, inspectors, radio, television, radar; other positions. Technica Employment Agency, 179 Clapham Road, S.W.9 (BRIxton 3487) W 2119

ELECTRONIC ENGINEER REQUIRED, age 26-35, B.Sc. Degree or equivalent to carry out design development and production. Experience in audio-frequency circuit design, audiometric equipment, industrial electro-mechanical timing devices, coil and transformer winding and production methods and economy both in electronic and light engineering fields essential. Salary £450-£600 p.a. according to qualifications and experience. Box W 2126 W2126

RADIO ELECTRONIC ENGINEER capable design construction up to low power transmitter standard equipment. Possible qualification City of London Guilds Certificate. Excellent prospects. Box W 2123 W 2123

APPLICATIONS INVITED from college trained Engineers with radar experience covering centimetre aerials, wave guides and receivers. Circuit and general electronic experience also essential. Salary offered will be from £650 p.a. upwards according to qualifications and experience. Write giving full particulars quoting Ref. 733 to Box W 2098 W 2098

TELEVISION ENGINEERS required by East London firm with all leading agencies. Salary £9-£10 per week. Permanent position. Only first class men need apply. Leytonia Radio, 828, High Road, Leyton, E.10. Phone LEY 1396 W 2125

JUNIOR Electronic Circuit Engineers required for development and prototype work involving pulse and high frequency techniques. Write stating qualifications, experience and wage required to Labgear Ltd. Willow Place, Cambridge. W 2127

MARCONI'S Wireless Telegraph Company require for their Research Laboratories at Chelmsford, senior and junior research and development engineers for domestic television receivers. Applicants who must have had extensive experience in television receivers should write, giving full particulars quoting reference 266 to Central Personnel Services, English Electric Co., Ltd., 24/30, Gillingham Street, London, S.W.1. W 2129

CLASSIFIED ANNOUNCEMENTS
continued on Page 4

Mullard *miniatures*

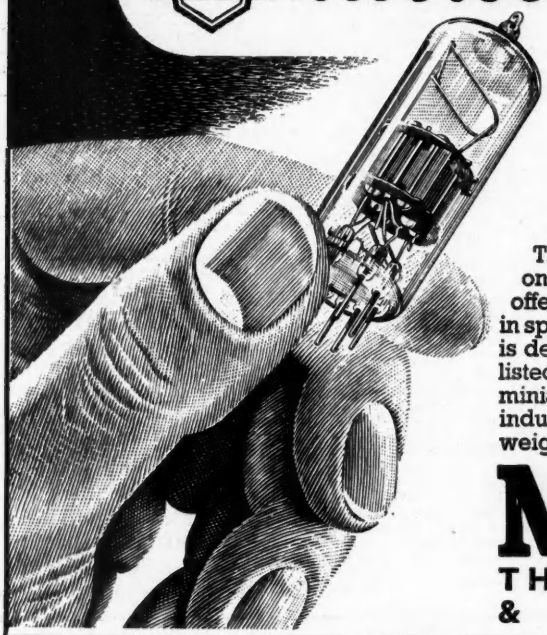

The Mullard range of miniature valves on the B7G base (7-pin button base) offers special advantages where a saving in space, weight and volume of equipment is desired. The mains and battery types listed below meet most requirements for miniature telecommunications receivers, industrial electronic equipment, and light-weight miniature measuring instruments.

Mullard

THERMIONIC VALVES & ELECTRON TUBES

TYPICAL CHARACTERISTICS

No.	Type	Filament or Heater		V_a (V)	V_{g2} (V)	V_{g1} (V)	I_a (mA)	g_m (mA/V)	μ	r_a (KΩ)	R_k (Ω)	R_a (KΩ)	P_{out} (W)
EY91	Half-Wave Rectifier	6.3	0.42	250 (max)	—	—	75 (max)	—	—	—	—	—	—
EC91	V.H.F. Grounded-grid Triode	6.3	0.3	250	—	-1.5	10	8.5	100	12	150	—	—
EF91	High Slope, Sharp Cut-off R.F. Pentode	6.3	0.3	250	250	-2	10	7.65	70 (g_1-g_2)	1000	—	—	—
EF92	V.M., R.F. or I.F. Pentode	6.3	0.2	250	150	-0.65	8	2.5	—	—	—	—	—
EAC91	Diode Triode for Frequency Changing up to 300Mc/s	6.3	0.3	200	—	-2.8	7.5	2.8	36	12.8	—	—	—
EB91 (6AL5)	Screened Double Diode—separate cathodes	6.3	0.3	150 (max)	—	—	9 (max)	—	—	—	—	—	—
EL91	Output Pentode (1.4W Output)	6.3	0.2	250	250	-13.5	16	2.6	12 (g_1 g_2)	130	680	16	1.4
ECC91 (6J6)	V.H.F. Double Triode (Physical Common Cathode)	6.3	0.45	100	—	—	8.5	5.3	33	7.1	100	—	—
DK91 (1R5)	V.M. Heptode Frequency Changer	1.4	0.05	90	67.5	0	1.6	0.3 (gc)	—	600	—	—	—
DF91 (1T4)	V.M., R.F. or I.F. Pentode	1.4	0.05	90	67.5	0	3.5	0.9	—	500	—	—	—
DF92	Sharp Cut-off R.F. Pentode	1.4	0.05	90	67.5	0	3.7	1.0	—	500	—	—	—
DAF91 (1S5)	Single Diode Pentode	1.4	0.05	67.5	67.5	0	1.6	0.625	—	600	—	—	—
DL92 (3S4)	Output Pentode (0.27W Output)	1.4	0.1	90	67.5	-7	7.4	1.58	—	100	—	8	0.27
DL93 (3A4)	A.F. or R.F. Output Pentode	1.4	0.2	150	90	-8.4	13.3	1.9	—	100	—	8	0.7 (audio)
DL94 (3V4)	Output Pentode (0.27W Output)	1.4	0.1	90	90	-4.5	9.5	2.15	—	100	—	10	0.27
DA90 (1A3)	R.F. Diode	1.4	0.15	330 (P.I.V. max)	—	—	0.5 (max)	—	—	—	—	—	—
DCC90 (3A5)	R.F. Double Triode	1.4	0.22	90	—	-2.5	3.7	1.8	15	8.3	—	—	2
2D21	Gas-filled Tetrode	6.3	0.6	400	0	-6	80 (max)	—	250	—	—	—	—

MULLARD ELECTRONIC PRODUCTS LTD · Century House, Shaftesbury Avenue, London, W.C.2.

MVT35A (REV)

CLASSIFIED ANNOUNCEMENTS (Cont'd.)

UNIVERSITY OF BRISTOL. The University invites applications for the post of Technician in the H. H. Wills Physical Laboratory to assist in the development and maintenance of a wide variety of electronic equipment. Experience in building such equipment is essential and some mechanical aptitude will be an advantage. Salary within the laboratory scale according to age and experience. Applications stating age, qualifications and giving details of experience should be sent to the Registrar, the University Bristol, 8, before December 5th W 2124

ENGLISH ELECTRIC require a Senior Circuit Engineer (Electronics) for their Nelson Research Laboratories at Stafford. Applicants must hold a University Degree or Associate Membership of the Institution of Electrical Engineers have had two or three years' industrial experience and be interested in the development of electronic circuits. The work will involve design of special circuits. Write giving full particulars quoting reference 313 to Central Personnel Services, English Electric Co., Ltd., 24/30, Gillingham Street, Westminster, S.W.1. W 2128

SITUATIONS WANTED

YOUNG ambitious graduate B.Sc (Eng.), 2½ years radar-electronics research, desires position with commercial aspects. Sales engineer, representative or consulting assistant preferred. Risk and responsibility willingly undertaken. Box No. W 1025 W 1025

DEVELOPMENT ENGINEER, 11 years present post seeks change. Commercial and M.O.S. VHF AM/FM communication receiver development, television, components. Box No. W 1022 W 1022

BUSINESS OPPORTUNITIES

BRITISH EXPORTERS having extensive connexions in all oversea markets, require sole or partial agencies for British manufactured engineering and allied materials and equipment. Full details to Chemia Products (U.K.), Ltd., 10/13, Dominion Street, South Place, E.C.2. Telephone: MONarch 3517/9. W 2040

EDUCATIONAL

A.M.I.E.E., City and Guilds, etc., on "NO PASS—NO FEE" terms. Over 95 per cent successes. For full details of modern courses in all branches of Electrical Technology send for our 112-page handbook —FREE and post free. B.I.E.T. (Dept. 337B), 17, Stratford Place, London, W.1. W 100

SERVICE

LOUDSPEAKER repairs, British, American, any make. Moderate prices.—Sinclair Speakers, 12, Pembroke Street, London, N.1. W 101

GLASSBLOWING, repetition and scientific by Hall Drysdale & Co. Ltd., of 58, Commerce Road, Wood Green, London, N.22. Phone BOWes Park 7221-2. W106

FOR SALE

WEBB'S 1948 Radio Map of World, new multi-colour printing with up-to-date call signs and fresh information; on heavy art paper, 4s. 6d., post 6d. On linen on rollers, 11s. 6d. post 9d. W 102

FIVE CORE CABLE (9/012) tough rubber sheathed, tinned copper screened 1s yard. Also enamel copper wires Armes, 37, Birchwood Drive, Leigh-on-Sea. W 1021

DESIGNATION and valve-type waterslide transfers, black and silver 1 in. by ½ in. 44 different titles, 68 transfers in all. Most useful for "that special job." Send 2s. 6d. P.O. and S.A.E. to Whixer Co., Farnham, Surrey W 1023

2 FURZEHILL B.F.O. Oscillators Type FHL (list £50 each). 2 Attenuator Boxes for same Furzehill Type 1358 (list £18 each). 2 Avo Valve Testers, 1 Avo H.F. Oscillator, 1 Avo Bridge, 1 Mullard Oscilloscope Type G.M. 3152 (list £50). Laboratory used. All as new. Offers to: A. Kershaw & Sons, Harehills Lane, Leeds, 8. W 1007

VALVES: 1,000 VR78; 2,000 VR92; 1,000 6J5; 1,000 VR65; 5,000 VR65A, 6K7s; 2,000 VRS4, new boxed. All at 3s. 6d. each. XTAL 22 SYLVANIA, 3s. 6d. each. 100 Kc/s, 12s. 6d. each. New Belling & Lee 5 pin, 7 pin plugs and sockets, 6d. each. Pye plugs and sockets 6d. each. 2 pin plugs and sockets 6d. complete. Meters, all types. Amateurs Paradise, 155, Humberstone Road, Leicester. W 1020

MERCURY SWITCHES are made by Hall Drysdale & Co. Ltd., of 58, Commerce Road, Wood Green, London, N.22. Phone BOWes Park 7221-2. W107

BUSINESS FOR SALE

SUSSEX. Genuine electrical and wireless business. Spacious premises in main shopping street with display windows, large shop, workshops at rear. Self-contained flat over, 2 beds, Sitting room, bathroom, kitchen, scullery. Separate entrance. Rent £300 p.a. exclusive. Rates £78 p.a. 21 year lease. Price £4,500. Stock at valuation. Full details, W. G. F. Swayne, F.A.I., 3, Clinton Place, Seaford, Sussex. Seaford 2144. W 2088

WANTED

WE WILL BUY at your price used radios, amplifiers, converters, test meters, motors, pick-ups, speakers, etc., radio and electrical accessories. Write, phone or call, University Radio Ltd., 22, Lisle Street, London, W.C.2. GERrard 4447. W 103

WANTED—"Proceedings at Radiolocation Convention," by I.E.E. Nos. 2, 5, 7. Box No. W 1024.

VELODYNES
MAGSLIPS
SELSYNS

Catalogue and Technical Details on request.
Technical Correspondence invited.

HOPTON RADIO,
1, Hopton Parade,
Streatham High Road,
LONDON, S.W.16.

Telephone: STReatham 6165.

DELARON

Wherever there's current to be countered or voltage to be revolted let Delaron make the doings. One or other of the Delaron grades will possess the right electrical properties plus very desirable mechanical advantages.

In thicknesses from ⅛". Two colours—black and brown, various finishes. Various sheet sizes.

Can be machined easily. May we send you full information?

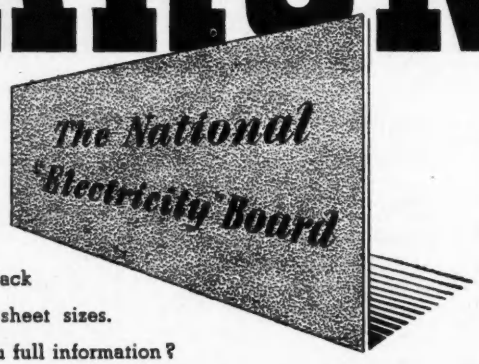

THOMAS DE LA RUE & CO., LTD., Plastics Division, Imperial House, Regent Street, London, W.1.

VALVES FOR TELEVISION RECEIVERS

The T41 and 6K25 thyratrons have been designed for use in scanning generators in both line and frame time base circuits of television receivers having magnetic deflection systems.

RATING:

T41

Heater Voltage	=	4.0 volts
Heater Current	=	1.5 amps.
Max. Anode Voltage	=	400 volts
Max. Peak Anode Current ...	=	500 mA.
Control Ratio	=	20

LIST PRICE 10/6

BASE

T41—Mazda Octal

Pin 1. Heater
Pin 2. Cathode
Pin 3. Anode
Pin 4. —
Pin 5. Grid
Pin 6. Metallising
Pin 7. —
Pin 8. Heater

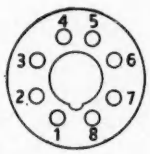

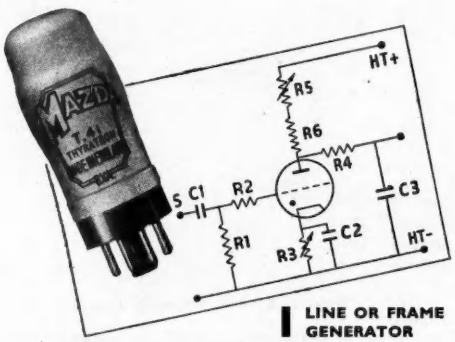

1 LINE OR FRAME GENERATOR

VALUES FOR LINE TIME BASE (1)

R1	=	47,000 Ω	C1	=	50μμF
R2	=	4,700 Ω	C2	=	1μF
R3	=	3,000 Ω	C3	=	0.007μF
R4	=	100 Ω			
R5	=	50,000 Ω			
R6	=	68,000 Ω			

RATING:

6K25

Heater Voltage	=	6.3 volts
Heater Current	=	0.95 amps.
Max. Anode Voltage	=	400 volts
Max. Peak Anode Current ...	=	500 mA.
Control Ratio	=	20

LIST PRICE 10/6

BASE

6K25—International Octal

Pin 1. Metallising
Pin 2. Heater
Pin 3. Anode
Pin 4. —
Pin 5. Grid
Pin 6. —
Pin 7. Heater
Pin 8. Cathode

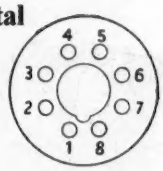

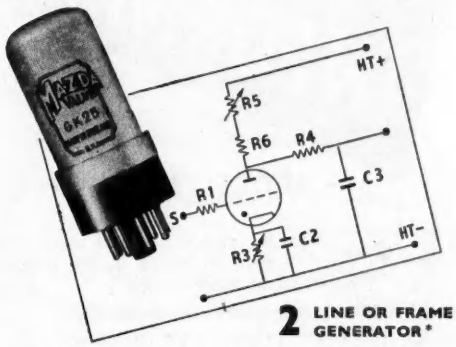

2 LINE OR FRAME GENERATOR*

VALUES FOR FRAME TIME BASE (1)

R1	=	47,000 Ω	C1	=	0.1μF
R2	=	33,000—47,000 Ω	C2	=	50μF
R3	=	5,000 Ω	C3	=	0.5μF
R4	=	220 Ω			
R5	=	100,000 Ω			
R6	=	100,000 Ω			

The two circuits shown are applicable to both valves and illustrate the use of a thyratron as a scanning generator, the output being fed to an amplifier such as the Mazda 6P25, Pen.45, Pen.46 or 6P28. Diagram No. 2 is for use in circuits where the synchronising pulse is obtained directly from the cathode of the video frequency amplifier or the signal diode load.

**In circuit 2 the value of R1 should be between 30,000 and 50,000 ohms. The remainder of the values are as given above.*

EDISWAN

MAZDA

RADIO VALVES AND TELEVISION TUBES

THE EDISON SWAN ELECTRIC CO. LTD., 155 CHARING CROSS ROAD, LONDON, W.C.2

RA.178

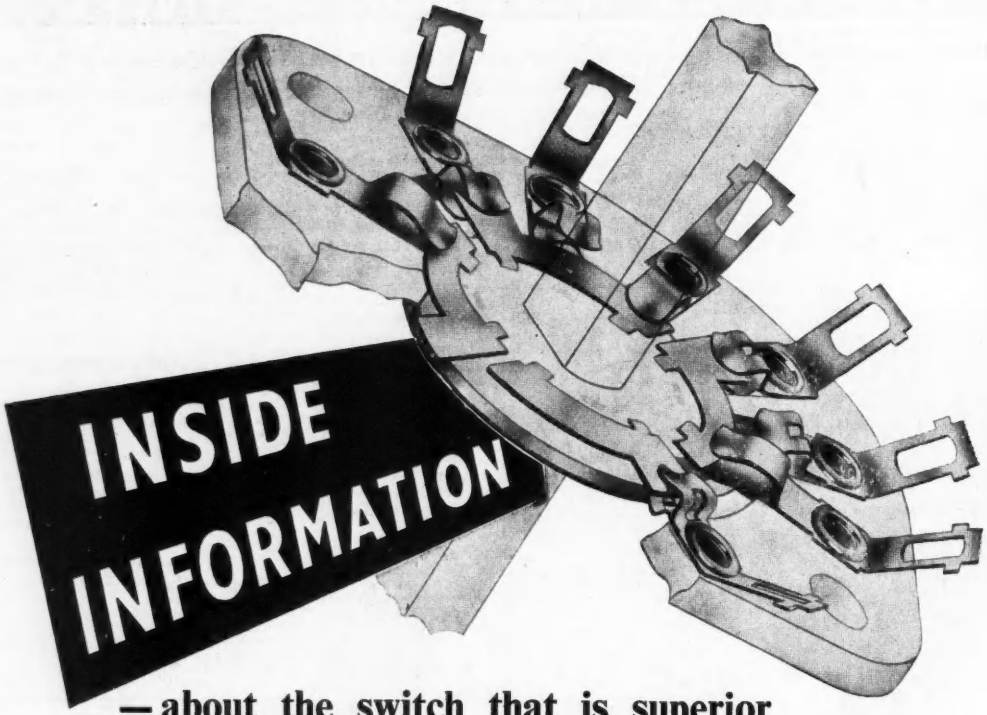

— about the switch that is superior

'OAK' switches — both rotary and push button types — were embodied in the majority of receivers displayed at Radiolympia.

Throughout the radio world, the time-tested basic 'OAK' principles are recognised and acknowledged as superior. They form the basis for the standard inter-service wafer type switch to Specification RCS.151 of the Radio Components Standardisation Committee.

The new miniature types, embodying all 'OAK' basic features, bring the range available in line with today's requirements for miniaturised equipments.

- **Self-aligning floating rotor.**
- **Dual contact surfaces ensure low contact resistance throughout long life.**
- **Fixed contacts of special spring alloy, heavily silver-plated as standard; silver alloy available if required.**
- **Single or multiple wafer construction.**
- **High grade S.R.B.P. or low-loss ceramic insulation.**

NSF

OAK OAK PRODUCTS

SWITCHES

Other British N.S.F. Products include.

Cutler-Hammer appliance switches; Carbon and wire-wound potentiometers for televison and radio applications; Paper tubular capacitors; Wire-wound resistors

SOLE LICENSEES OF OAK MANUFACTURING COMPANY, CHICAGO

Licensees of Igranic Electric Co. Ltd. for the above products of Cutler-Hammer Inc. Milwaukee, U.S.A.

BRITISH N·S·F CO · LTD · KEIGHLEY · YORKS. · *London Office: 9 Stratford Place, W·1 · Phone: MAYfair 4234*

THE OSRAM MINIATURES are becoming more popular every day . . .

OSRAM BATTERY MINIATURES "17" RANGE

Left to Right: The X.17 Frequency Changer; W.17 Vari-Mu H. F. Pentode; ZD.17 Diode Pentode; N.17 Output Pentode

and here's why

These valves, now extensively used by set manufacturers, have been specially designed with a view to H.T. current economy. The filaments, intended primarily to operate from a dry cell, maintain adequate emission during the whole useful life of the cell. Mounted on the popular B7G miniature base, they are compact and extremely robust. Ideal for battery operation in portable equipment such as personal receivers.

Osram VALVES

THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, W.C.2

PHOTO-ELECTRIC RELAY

for "ON" or "OFF" control of ELECTRIC POWER

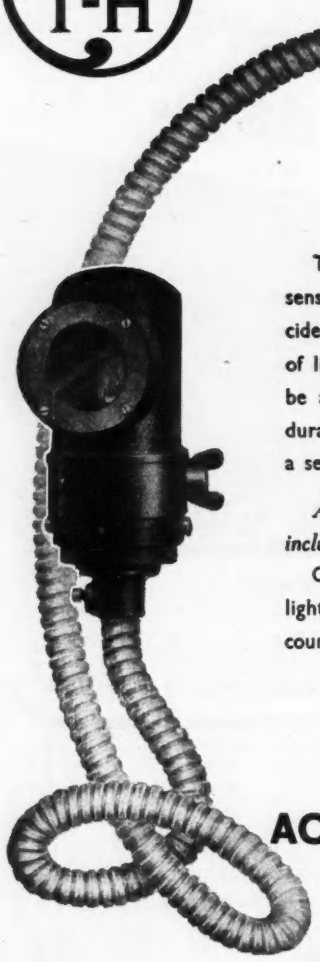

The standard relay is extremely sensitive and responds to the incidence or interruption of a beam of light, the intensity of which may be as low as 1-Foot candle and the duration as short as one-tenth of a second.

Applications to industrial processes include :—

Control of temperature, liquid level, lighting, register, dimensions, weighing, counting, etc. ; also alarm devices.

Delivery from stock

ACTUATED BY LIGHT

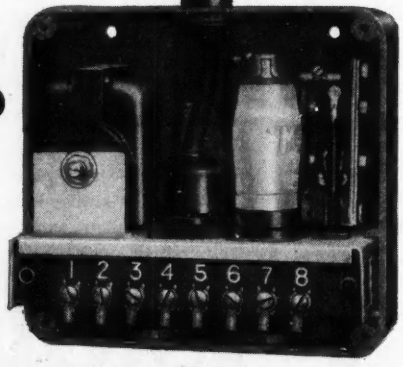

BRITISH THOMSON-HOUSTON

THE BRITISH THOMSON-HOUSTON COMPANY LIMITED · RUGBY · ENGLAND

A3854

R.F. ATTENUATOR
TYPE D-239

THIS small compact attenuator is characterized by a relatively high insertion loss and outstanding accuracy of attenuation at high frequencies. Wire wound resistance elements ensure accuracy, good stability and freedom from noise. It can be used as a bench instrument or for incorporation in other apparatus where its small size is a considerable asset. Two types, giving alternative values of total attenuation, are available.

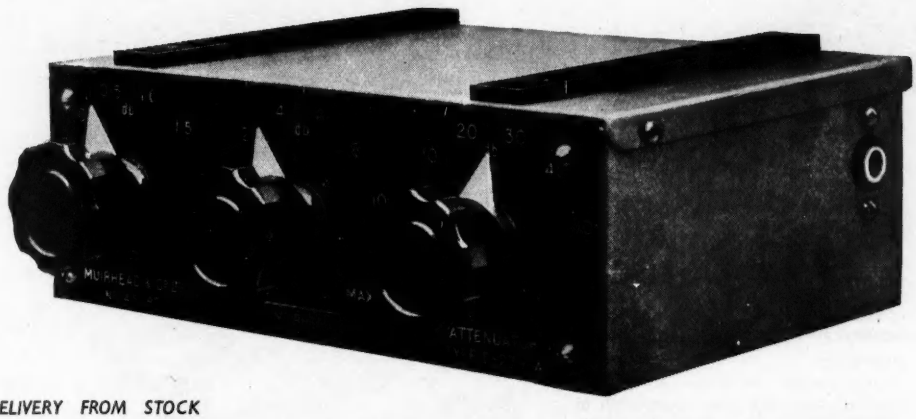

DELIVERY FROM STOCK

BRIEF SPECIFICATION

ATTENUATION RANGE. TYPE D-239-A :	0-61·5 db variable in steps of 0·5 db.
ATTENUATION RANGE. TYPE D-239-B :	0-80 db variable in steps of 1 db.
CHARACTERISTIC IMPEDANCE:	75 ohms (" T "-network).
PERFORMANCE :	At frequencies up to 5 Mc/s and for any setting of the switches the error in attenuation will not exceed ± 0·2 db. Reasonable accuracy is maintained up to 10 Mc/s.
TERMINATIONS :	Coaxial connectors.
INPUT :	3 volts maximum.
DIMENSIONS :	6½" × 2⅜" × 5½".
WEIGHT :	2½ lbs.

Manufactured to a design of the Radio Branch of the Post Office Engineering Department.

Full details are given in Bulletin B-625-A, a copy of which will be sent on request.

MUIRHEAD

Muirhead & Co., Limited, Elmers End, Beckenham, Kent. Telephone: Beckenham 0041-2

FOR OVER 60 YEARS DESIGNERS AND MAKERS OF PRECISION INSTRUMENTS

C.R.C.634

B

WHERE EXTREME ACCURACY IS REQUIRED

Made in Three Principal Materials

FREQUELEX
An insulating material of Low Di-electric Loss, for Coil Formers, Aerial Insulators, Valve Holders, etc.

PERMALEX
A High Permittivity Material. For the construction of Condensers of the smallest possible dimensions.

TEMPLEX
A Condenser material of medium permittivity. For the construction of Condensers having a constant capacity at all temperatures.

Bullers

CAN SATISFY THE MOST EXACTING CUSTOMER

BULLERS LOW LOSS CERAMICS

BULLERS LTD., 6, Laurence Pountney Hill, London, E.C.4.
Telegrams: "Bullers, Cannon, London."

Phone: Mansion House 9971 (3 lines)
Manchester Office: 196, Deansgate, Manchester

NEW!

BELLING-LEE COMPONENTS

For Screened Balanced Twin Cables

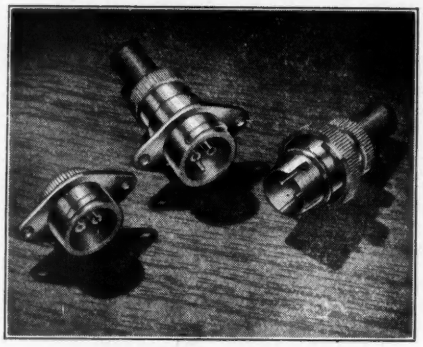

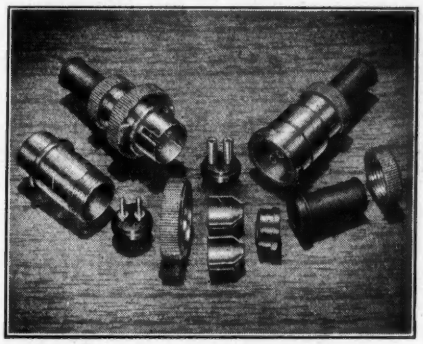

LIST NUMBERS & CABLE TYPES

L.625/P	Flex Plug
L.625/S	Chassis Socket
L.689	Bulkhead Socket
L.690	Line Socket

For use with following cables:

Duradio 28
Telcon B.A.3. P.S.M.
Twinax

and other screened balanced twin cables not exceeding 0.240" dia. over screen.

COMPONENT CHARACTERISTICS

Characteristic impedance 100 ohms
Contact resistance—less than 10 milliohms

Capacitance:

Conductor/conductor 1 pF
Each conductor/screen 2.5 pF

Chassis fixing — 6BA clearance on $1\frac{1}{8}$" centres

Breakdown voltage — pin to pin 4 Kv
pins to screen 2 Kv

A range of lightweight connectors complying with the latest R.E.C.M.F. draft Specification for Screened balanced twin cables, as tabulated.

★ **Complete interchangeability** ★ **Finished for instrument panel requirements**

★ **Positive quick action locking device** ★ **High grade bakelite insulators**

★ **Simple assembly and loading** ★ **Light alloy screened housing**

Makers of good components for over 25 years

BELLING & LEE LTD
CAMBRIDGE ARTERIAL RD., ENFIELD, MIDDX., ENGLAND

FOSTER

TRADE "V.R." MARK

VOLTAGE REGULATING EQUIPMENT

A Comprehensive Range for

High or Low Tension

•

Manual or Automatic Operation

•

High or Low Current

•

Constant or Infinitely Variable Voltage

•

Foster Transformers & Switchgear Ltd

Associated with
LANCASHIRE DYNAMO & CRYPTO LTD

SOUTH WIMBLEDON, LONDON, S.W.19

Laminations

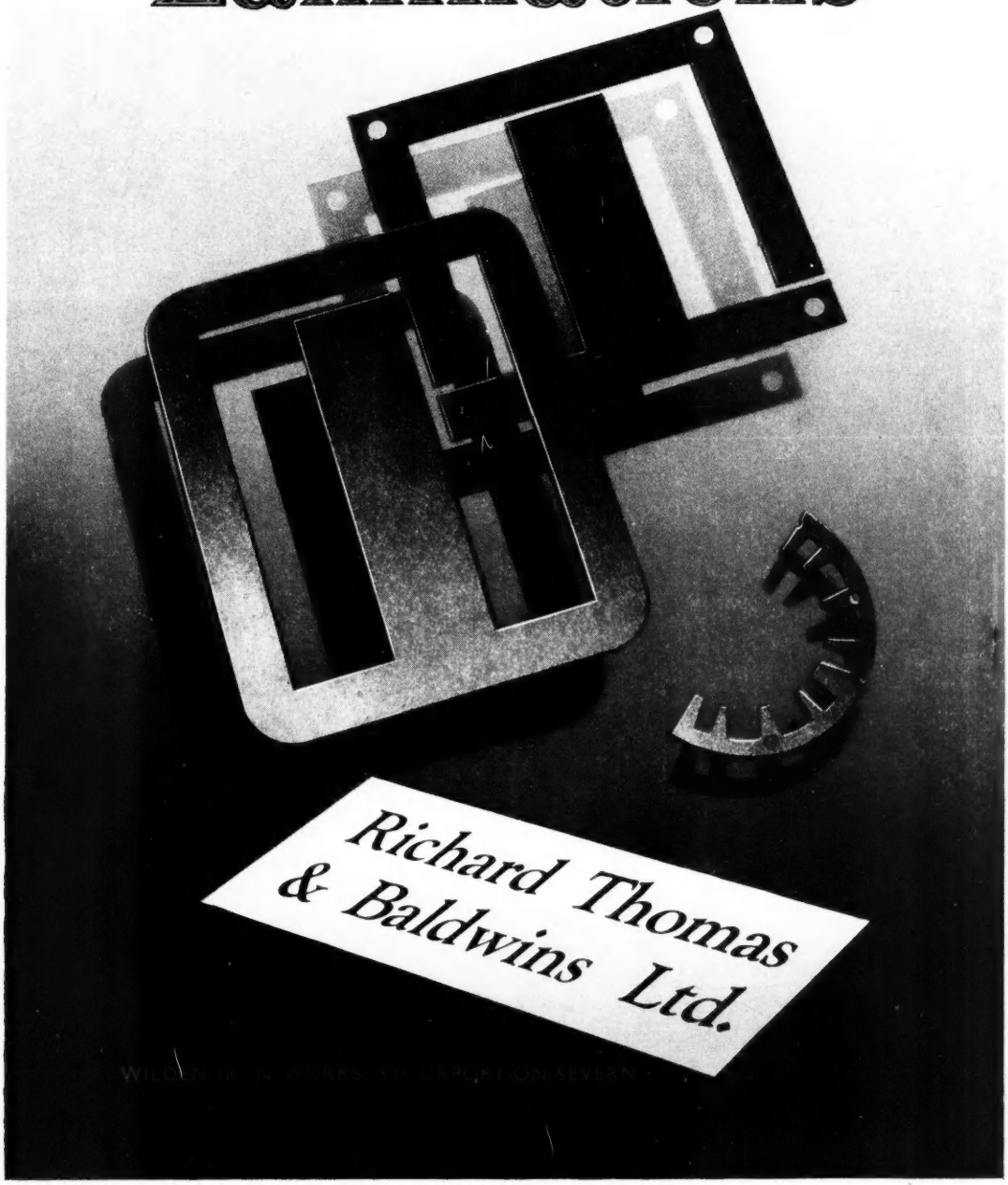

C

T.C.C. CAPACITORS

exclusively specified for the "View Master"

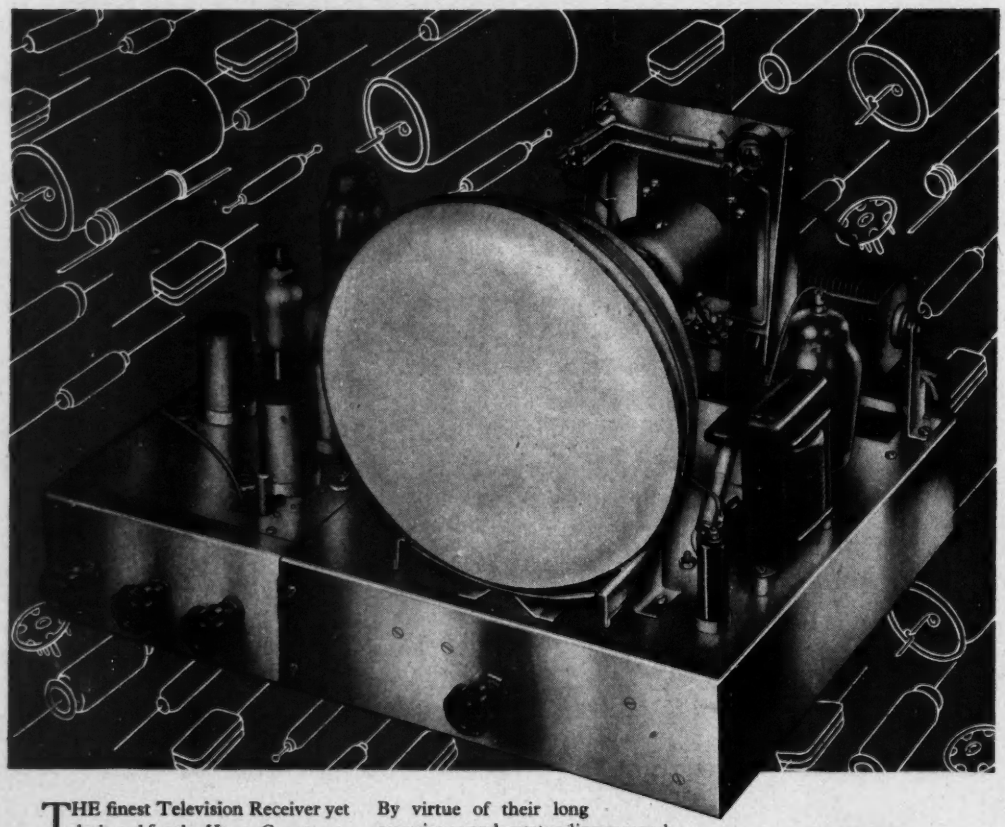

THE finest Television Receiver yet designed for the Home Constructor* uses T.C.C. Capacitors exclusively. The reason is obvious. In any Television circuit capacitors play a vital role. According to their function some must be extremely accurate and stable, others highly resistant to heavy voltage surges. But whatever their function they must all give trouble-free dependable service throughout the life of the Receiver.

By virtue of their long experience and outstanding research facilities T.C.C. can rightly claim to be the logical choice for all capacitor requirements — with a range of types without equal in the industry.

** The "View Master" is fully described in a Constructor Envelope containing 8 full size wiring and assembly drawings together with a 32 page booklet profusely illustrated giving much practical information on Television. Copies 5/- each from all Wireless Shops or Newsagents. In case of difficulty direct from us post free 5/6.*

TCC

THE TELEGRAPH CONDENSER CO., LTD.

RADIO DIVISION

NORTH ACTON · LONDON · W·3 Telephone ACORN 0061

CINTEL

The longest Journey...

begins with one step

'CINTEL' guarantees a step in the right direction where electronics are concerned. We illustrate three typical 'CINTEL' instruments from our wide range for the modern laboratory. Please write for further particulars.

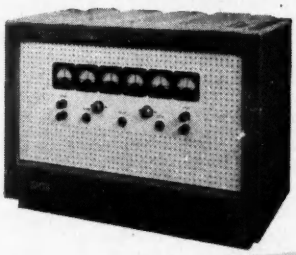

'CINTEL' MICROSECOND COUNTER CHRONOMETER

'CINTEL' R.C. OSCILLATOR & AUTOMATIC FREQUENCY MONITOR

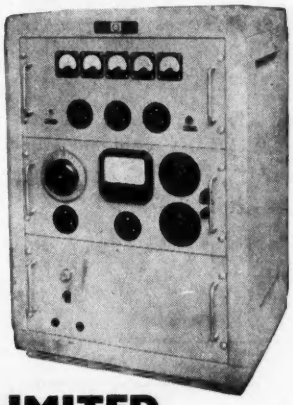

'CINTEL' MUTUAL & SELF INDUCTANCE BRIDGE

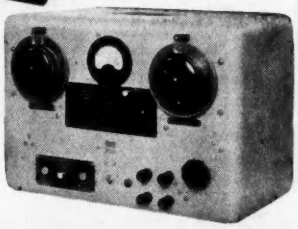

CINEMA-TELEVISION LIMITED

FOREMOST IN THE MANUFACTURE OF

● Counters & Chronometers ● Metal Detectors ● Oscilloscopes ● Photo-Electric Cells ● Cathode Ray Tubes ● Geiger-Muller Tubes ● Electronic Instruments

WORSLEY BRIDGE ROAD · LONDON · S·E·26

Telephone: HITher Green 4600

Northern Agents:
F. C. ROBINSON & PARTNERS LIMITED
308 Deansgate, Manchester 3

Scottish Agents:
ATKINS, ROBERTSON & WHITEFORD LIMITED
100 Torrisdale Street, Glasgow, S.2

CINTEL

REGISTERED TRADE MARK

VALVES For SPECIAL PURPOSES

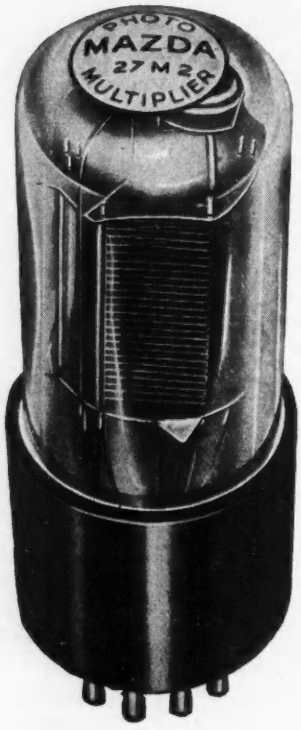

27M2 Nine Stage Photo-Electric Multiplier

The Mazda 27M2 is a high vacuum photo-cell with high response in the visible region. The photo-electric current produced at the cathode is multiplied many times by secondary emission occurring at successive cathodes within the valve.

It is capable of multiplying very small currents produced under weak illumination by an average value of 250,000 times, when operated at 80 volts per stage. When operated at an overall voltage of 600 volts, i.e., 60 volts per stage, followed by a single stage D.C. amplifier, it is suitable for the amplification of changes in cathode current greater than 10^{-14} amperes.

The resultant output current is a linear function of the exciting illumination, under normal operating conditions. Since secondary emission occurs simultaneously, the frequency response is flat up to the frequencies at which transit time becomes a limiting factor.

Because of its sensitivity, low noise level, low dark current and freedom from distortion, the 27M2 may be used for light-operated relays, for film scanning, facsimile transmission, in scientific research involving low light levels, and in many applications where its small size is an advantage.

NOTE.—The 27M2 is similar to the 27M1 except for the wider tolerances on the anode dark current which necessitates a lower anode supply voltage, with a resulting reduction in the current amplification to approximately one quarter of that obtainable from the 27M1.

PRICE £12.0.0 (provisional)

TYPICAL OPERATION

Overall Voltage	800 v.
*Sensitivity	2 A/lumen
Spectral Range	3,300—6,500 Å.

**The sensitivity is on the basis of a lamp colour temperature of 2700° K and a light spot area of 3mm. 15mm. The tube is adjusted to a position of maximum sensitivity.*

DIMENSIONS

Max. Overall Length (mm)	94.0
,, Bulb Diameter (mm)	28.5
,, Base Diameter (mm)	33.4
Light Centre from Seat (mm)	49.2±2.4

It is recommended that the bleeder current in the potentiometer providing the secondary cathode voltages should be of the order of 10 times the maximum working current output of the tube.

EDISWAN

MAZDA

RADIO VALVES AND CATHODE RAY TUBES

THE EDISON SWAN ELECTRIC CO. LTD., 155 CHARING CROSS ROAD, LONDON, W.C.2

RA.181

designed ....

with your specific needs in mind

MODEL 1035

The Cossor general purpose Oscillograph is designed and built by electronic engineers who are themselves familiar with the everyday problems which technicians have to face. The instrument consists of a Double Beam Tube operated at 2kV., a Time Base, Y Deflection Amplifiers and Internal Power Supplies. The 90 mm. screen is flat, and traces are presented over the full area. Signals are normally fed through the Amplifiers, and the calibrated Y-Shift controls provide a measurement of the applied voltages. The Time Base operates repetitively, or by external trigger (for single stroke operation), or at trigger pulse repetition frequency for continuous scanning. A calibrated X-Shift Control is provided for the measurement of Time.

Model 1428
CAMERA

Specially developed for use with Cossor Oscillographs, it provides the simplest means of recording stationary or non-recurrent waveforms and slow transients by the moving film method on standard perforated 35 mm. film or paper. Of robust construction, it has provision for power drive by the Cossor Three-Speed Motor Attachment, Model 1429.

COSSOR

Double Beam

OSCILLOGRAPH

Further details obtainable on application to :—

A. C. COSSOR LTD., INSTRUMENT DIVISION, HIGHBURY, LONDON, N.5

CX11

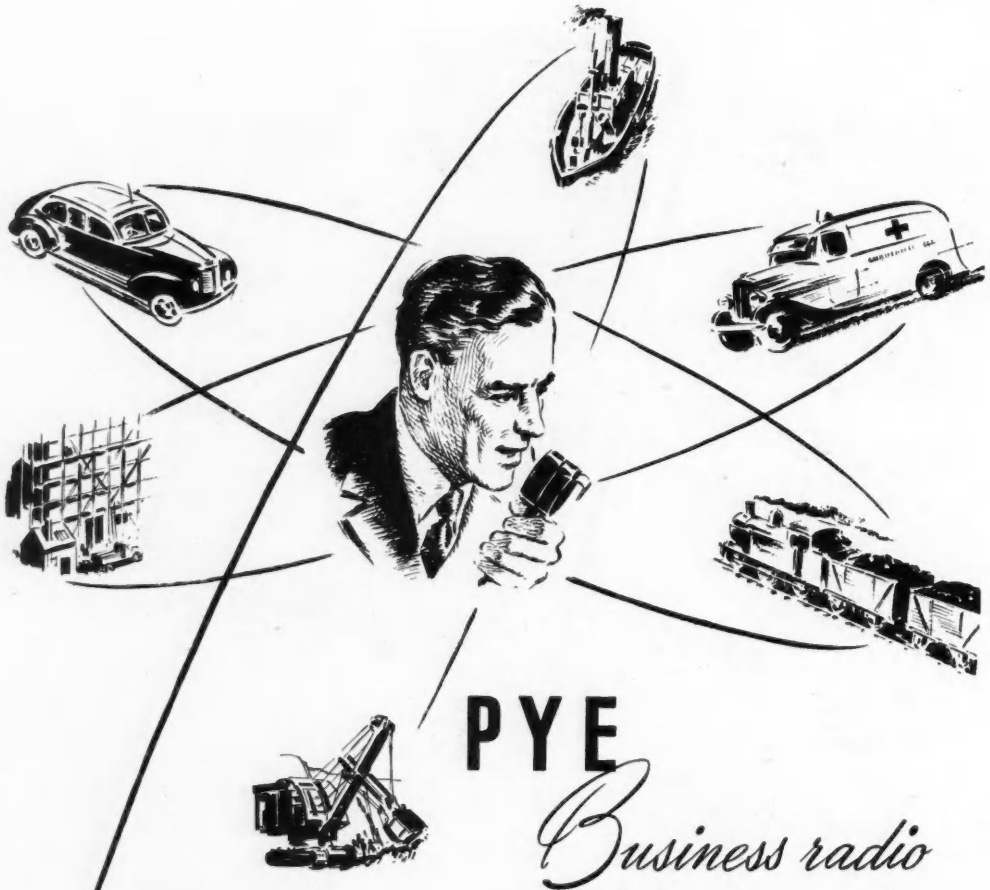

PYE

Business radio

- *Contracting Engineers*
- *Haulage Contractors*
- *Fire Services*
- *Doctors*
- *Ambulance Services*
- *News Editors*
- *Veterinary Surgeons*
- *Building Contractors*
- *Port and Harbour Authorities*
- *Private Hire Companies*
- *Airports*
- *Surveyors*
- *Railways*
- *Agricultural Engineers*

Pye Ltd. announce a complete new range of "fixed" and mobile V.H.F. Radio-Telephone equipment for the Business Radio band 156-184 Mc/s, and for essential services in the 60-130 Mc/s band.
Combining the high performance made possible by modern V.H.F. Radio techniques with reliability and simplicity of operation, this new Pye equipment will meet the exacting needs of Government and Industry at home and overseas.

Further details will be sent on request.

Telecommunications
CAMBRIDGE ENGLAND

PYE LIMITED · TELECOMMUNICATIONS DIVISION · CAMBRIDGE · ENGLAND

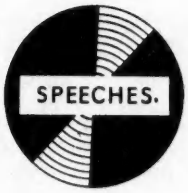

If they are worth hearing . . . they are worth recording!

Simple to operate and readily portable, the E.M.I. Portable Disc Recorder enables brilliant "on the spot" recordings to be made of outstanding events. Produced by E.M.I. technicians with 50 years' experience in recording, this new E.M.I. Portable Recorder is a remarkable technical achievement. Here in transportable form is a complete recording and play-back equipment designed to produce high quality recordings on lacquer blanks without demanding expert knowledge of recording technique. Operation is extremely easy and the equipment which is contained in three transportable cases needs 200/250 volts 50 cycles A.C. mains supply or a Car Battery and converter. Facilities for play-back and for sound amplification form an integral part of the Recorder. **RECORDING BLANKS:** EMIDISC **Play-back** Recording Blanks are ready for playing immediately after cutting. They are available in the following sizes—6″, 10″, 12″, 16″. **PROCESS BLANKS**—enabling the recording to be pressed in quantity, by E.M.I., are obtainable for 11″, 12″, 13″, 17½″ recordings.

E.M.I. PORTABLE RECORDER No. 2300

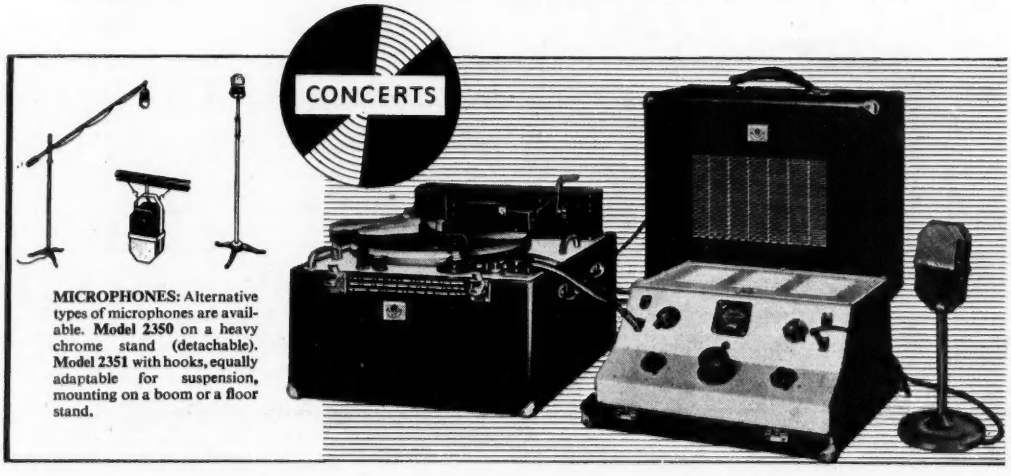

MICROPHONES: Alternative types of microphones are available. **Model 2350** on a heavy chrome stand (detachable). **Model 2351** with hooks, equally adaptable for suspension, mounting on a boom or a floor stand.

A descriptive leaflet giving full details of Model 2300 and Recording Blanks is obtainable on request.

E.M.I. SALES & SERVICE LTD. HEAD OFFICE: HAYES, MIDDX.

S.S.7

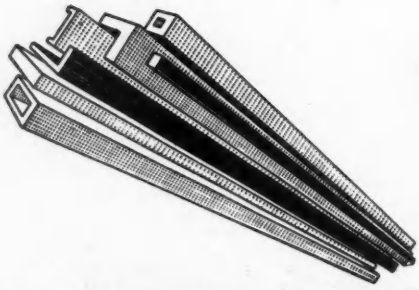

Will it work better in TUFNOL?

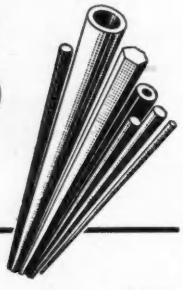

Are you blue about the blue-prints or anything but pro-prototype? This impasse has faced many engineers and manufacturers BEFORE they were introduced to Tufnol. If Tufnol is new to you, consider its merits: it possesses a valuable combination of chemical resisting, electrical insulating and mechanical qualities. Tufnol in action resists moisture and corrosion, withstands extremes of climate, can be lubricated with water, and has good tensile and compression strength—it can be machined as easily as hardwood. Tufnol has won for itself a vital place in most industries. Wouldn't YOUR idea work out better in Tufnol?

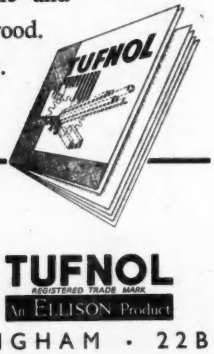

CAN WE HELP YOU?

Our records show many factual examples of this versatile material in action. Much information is already tabulated in Tufnol Publications, but our technical staff are equally keen to discuss NEW problems. Why not write TODAY?

TUFNOL
REGISTERED TRADE MARK
An ELLISON Product

TUFNOL LTD · PERRY BARR · BIRMINGHAM · 22B

231

Electronic Engineering

EDITORIAL, ADVERTISING AND PUBLISHING OFFICES, 28, ESSEX STREET, STRAND, W.C.2.

TELEPHONE: CENTRAL 6565 (10 LINES) *MANAGING EDITOR:* H. G. FOSTER, M.Sc., M.I.E.E. *TELEGRAMS:* LECTRONING, ESTRAND, LONDON

Monthly (published last Friday of preceding month) 2/- net. Subscription Rate: (Home or abroad) Post Paid 12 months 26/-, or $3·75 (U.S.).

Vol. 21. No. 262 December, 1949

CONTENTS

Birth Centenary of Ambrose Fleming—Part I ... 442
By J. T. MacGregor-Morris, D.Sc.(Eng.), M.I.E.E.

An Experimental Crystal Amplifier 448

Discriminator Adjustment 449

Ionisation in Gases 450
By T. H. D. Attewell, B.Sc., M.I.R.E.

H.T. Supply for Television Receivers 456
By C. H. Banthorpe

Television in Birmingham 457

The Hammond Spinet 461
By Alan Douglas

Obstacle Detection Using Ultrasonic Waves in Air 464
By G. Bradfield

A High-Impedance Input Stage for a Valve Amplifier 469
By P. O. Bishop, M.B., B.S.

A Zero-Beat Indicator for Heterodyne Measuring Systems 470
By K. Goldsmith, M.Sc., A.M.I.E.E.

Electronic Equipment 472

Book Reviews 474

Notes from the Industry 477

December Meetings 478

On Progress

ONE of the necessary duties in an editorial office is the reading of the contemporary journals of other countries in order that we may be conversant with the progress and development outside these Isles, and from time to time make comparison with our own achievements.

Reading through these journals we are frequently struck by the resourcefulness with which well established principles are adapted to new and unexpected applications.

It is not surprising that the electronics computor should offer a number of interesting possibilities, but one of the most intriguing to reach us comes, not unnaturally, from Chicago. According to our information an electronic umpire has been developed there for the American game of bowls, and that attention is now being given to a similar machine for baseball.

In the assessment of the possibilities of such a machine, the report is careful to point out, however, that its reception by the spectator may be hostile since it will not respond to any exhortations to "play the game."'

By comparison, our own efforts in this direction have been almost negligible, and our outlook somewhat different. We have tended to keep our referees—and indeed what would be the point in going to Highbury on Saturday afternoon without a referee?—and to concentrate our efforts instead on machines to play our games for us. Our readers will recall that we have already made a humble start in this direction with a "noughts and crosses" machine which incidentally contains a built-in referee to ring a bell should its human opponent attempt to cheat.

However, should we feel depressed at our lack of enterprise we have one solid achievement to record this month, and it is not inappropriate that this issue contains an account of the demonstration of the London-Birmingham Radio Relay Link and that it coincides with an article commemorating the birth centenary of Sir Ambrose Fleming.

The Sutton Coldfield Television Transmitter itself will be the largest in the world with its powers of 35 KW (vision) and 12 KW (sound), and it is claimed that nowhere else in the world does there exist a television radio relay link so technically advanced for continuous public service and which offers such possibilities in telecommunication projects.

Professor MacGregor-Morris in his commemorative article on Sir Ambrose Fleming says "On certain occasions it is well to pause and take stock of the achievements made in a rapidly growing subject and to consider to whom we owe the initial stages of its inception."

In our opinion, the demonstration of the London-Birmingham link is such an occasion.

Birth Centenary of Ambrose Fleming

. . . November 29, 1949

PART I

By J. T. MacGREGOR-MORRIS
D.Sc. (Eng.) London, M.I.E.E.*

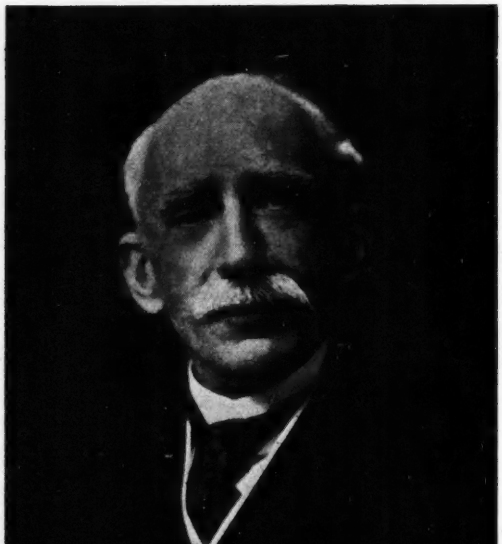

SIR AMBROSE FLEMING

(Courtesy, The Television Society)

ON certain occasions it is well to pause and take stock of the achievements made in a rapidly growing subject and to consider to whom we owe the initial stages of its inception. The present moment seems a suitable occasion to pay tribute to an outstanding figure.

In this journal it is fitting to commemorate the centenary of the birth of Ambrose Fleming, which occurred on November 29 this year, and we propose to do so by giving a brief account of his life and his contributions to Electrical Engineering, together with a more extended description of that part of his work which contributed to the foundation of Electronic Engineering—such as his work in the field of radio valves, cathode-ray tubes and the measurement of the length of electric waves.

If added emphasis be needed for such a course it is contained in a recent utterance of the Vice-Chancellor of Oxford University, made only a few days ago, when he said "I do not know of any subject or study in which, in recent years, the divorce between present practice and past history had been so complete as in the domain of science . . . thus while stress was laid on the up-to-date practical pursuit of science the long period of preparation and development which had led up to it should not be neglected."

Therefore in this article we shall examine the background of scientific knowledge which existed some three quarters of a century ago, and then study how Fleming reacted to it as he grew up, later to become one of our leading electrical engineers.

* Emeritus Professor of Electrical Engineering in the University of London.

State of Scientific Knowledge in the 1870's.

It is difficult for us to place ourselves in the position of such pioneers when the phrase "Electrical Engineering" had hardly been coined. To mention only a few of the practical men of the time, there were Swan, Edison, Hughes, Sir Wm. Siemens, Crompton, and, of the scientists, Wheatstone, John Hopkinson, Wm. Thomson (afterwards Lord Kelvin) and Ambrose Fleming.

At that time most public lighting was done by arc lamps, and for street lighting, as in the City of London, some 40 arcs were run in series supplied with commutator rectified A.C. current, each giving a light output of some two-thousand candles. In those days one of the great topical subjects was that of the sub-division of the electric light, i.e., the production of a lamp suitable for domestic use.

Further, whether transformers should have primaries connected in series or in parallel was still a moot point; also why or how an A.C. transformer worked was so little understood that a great Patent Office refused a patent for a transformer, on the grounds that one could not get out of anything more than one put into it!—in this case it was the current in a step-down transformer.

Electrical Engineering started as Electrical Technology, being a rather crude combination of physics and engineering; before this there was only wire telegraphy to absorb the attention of practical men with a bent for electricity. The electric telephone had not been invented.

In much the same way we have seen a similar change occurring in radio engineering from the enthusiastic wireless crank of half a century ago to the well established radio engineer of the present day.

Survey of the Life of Ambrose Fleming

John Ambrose Fleming, born November 29, 1849, was the eldest son of the Rev. James Fleming, D.D., a Congregational Minister in Lancaster. In the late autumn of 1853 the family moved to Kentish Town, London, where the father continued his ministry until his death in 1879. John Ambrose

showed an early liking for things mechanical, and a growing interest in experimenting. In fact, as he himself said, he was more interested in things than in people.

As he grew up he took a great interest in chemistry. After attending University College Boys' School (London) as a day boy, he entered, in 1867, the college of which the school building formed a part, and in 1870 he was one of the two successful candidates in the First Division of the degree of Bachelor of Science.

A short term of work in the drawing office of a firm of shipbuilders in Dublin was succeeded by some two years spent as a clerk on the Stock Exchange. As this work finished by 4 p.m. Fleming had considerable spare time, which he devoted to improving his knowledge of chemistry, physics and mathematics.

It is interesting that the art of popular scientific exposition was not neglected, for he gives an account of an early experimental lecture which he gave to his parents, and brother and sisters—elaborately prepared in the dining room of their house, concluding with the giving of an electric shock simultaneously to all the assembled audience, with most satisfying results—to the lecturer.

At the age of 21, (1870) he was appointed Science Master at Rossall College where he stayed for two years. Then from 1872-74 he studied at the Royal College of Science; chemistry under Dr. Edward Frankland, and physics under Dr. Guthrie.

By 1874 he was back again at teaching—this time as Science Master at Cheltenham—on the modern side. During the three years in this post Fleming was getting dissatisfied with the limited scope of his knowledge of physics and more especially of mathematics.

To make up this deficiency he decided in 1877 to go to St. John's College, Cambridge, to improve his mathematical knowledge, but specially to work under the famous Clerk Maxwell, the first director of the Cavendish Laboratory, which institution has had a continuous succession of professors of world-wide reputation including Sir J. J. Thomson and Sir Ernest Rutherford.

After the death of Clerk Maxwell in 1879, Fleming undertook some work as demonstrator in the University, during which period he obtained in 1880 the degree of D.Sc. of London.

In 1882 he was appointed to the newly created chair of Mathematics and Physics at Nottingham as its first occupant.

Though he made a success of this new appointment the attractions of London were too strong for his rather practical nature, so he left at the end of the session to join the Edison Electric Light Company. Professor John Hopkinson was their "scientific adviser" while Ambrose Fleming was their "electrician"—probably the term "electrical scientist" would convey nowadays a better idea of his position.

Professor at University College, London, 1885 to 1926

It was not long, however, before he returned to the professorial ranks, this time to the college of his early student days, University College London (Fig. 1), for in 1885 he was apoinpted the first Professor of Electrical Technology at that college. He was to hold this post for a period of over 40 years. This period covers the extraordinary growth of wire telegraphy and telephony, electric lighting, traction, and later the start and growth of wireless valves, amplifiers, oscillators, photo-electric cells, the cathode-ray tube, electron-optics and television; which vast array of subjects is now known as Electronics. During the whole of these 40 years Fleming directed his department with vision and enthusiasm so that University College London was in the forefront of many of these developments.

It was early in this period, in 1887, that he married his first wife, Clara Ripley Pratt, who died in 1917.

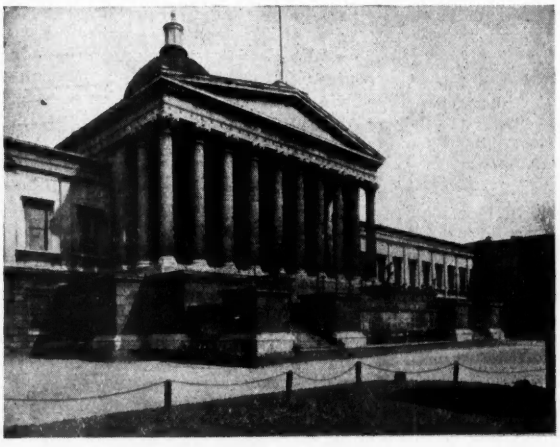

Fig. 1. University College, London. The electrical laboratories where Professor Fleming worked are on the first floor, to the right of this photograph

(Copyright, Country Life)

(i) Transformer Tests

We shall now follow more closely some of Fleming's achievements during this period of 40 years. From 1885 to 1895 Fleming was one of the leading exponents of the theory of alternating current transformers, and of their practical performance. Incidentally the two volume treatise which he wrote on "The Alternate Transformer" was for many years the premier treatise on the subject. In one of his diaries he states that this book was written in its entirety after 10 o'clock at night.

In 1890 Fleming was engaged on an almost classical investigation on the behaviour of power transformers under various conditions of load. That we may understand the difficulties of making reliable measurements of alternating voltage, current and power, we should recall the fact that the only trustworthy instruments available at that time for such purposes were the Cardew Hot-Wire Voltmeter and the Siemens' Electrodynamometer, apart from the Kelvin Electrostatic Voltmeter and the Kelvin ampere balance. The Wattmeter for alternate current measurements of power was hardly existent, and the importance of reducing the inductance of the shunt circuit of the wattmeter in comparison with its resistance, when the load was highly inductive, was only beginning to be appreciated by practical men. In fact, Fleming and Swinburne actually constructed their own wattmeters, and even then such men laboriously checked their results by the 3-voltmeter method which re-

quires a supply giving about double the working voltage of the transformer, a condition not always easy to obtain.

During the work on these transformers the development of the instruments and the low voltage part of the testing was done at University College, but by far the greater part was carried out at the Engineering Offices of the London Electric Supply Corporation, Adelphi Arches, Charing Cross. At this time Mr. J. C. Shields was Dr. Fleming's assistant, and he spared no pains to ensure that the results were reliable. The experiments extended over a period of five months.

All the results were collected together in a paper entitled "Experimental Researches on Alternate Current Transformers," which Fleming presented to the Institution of Electrical Engineers in November 1892. The paper excited great discussion. The presentation of the paper, and the discussion occupied five consecutive Thursday evenings, and it was not until February 9, 1893, that Fleming was allowed to reply, and he took the whole evening to do this.

Undoubtedly this paper and the discussion which it evoked was a great contribution to the clarification of the operation of power transformers.

Fleming did not let the grass grow under his feet, for as a result he delivered four Cantor lectures to the Society of Arts on "Practical Measurements of Alternating Currents" and these were illustrated fully by experiment. Later on he was asked to direct and arrange to carry out further experimental investigations, this time for the City of London Electric Lighting Company on the ageing of core losses in transformers, and later, on the waveform of the alternators at Bankside on open circuit and when on load.

We have examined this branch of his work, so as to bring out its thoroughness and to bring home the fact that it was his combination of the mastery of the underlying principles involved, and a real gift of exposition, which resulted in practical men coming away from his Cantor and other lectures feeling that they had got hold of something of which they could make use.

(ii) Illuminating Engineering

As our second example, we take Fleming's contributions to the development of electric lamps of the filament type, and their photometry. From 1885 to 1895 the Gas Referees and Examiners were the principal users of photometric methods in London, as they were appointed to ensure that gas supplies were up to the specified standard of illuminating power. Their tests were carried out chiefly by trained chemists, working at various stations throughout London, at irregular times, these times being entirely unknown to the gas companies. The Bunsen "Grease-spot" was the photometer, and originally the standard was the "good old Parliamentary Candle" made of the best spermacetic wax, and burning 120 grains in the hour. As it very rarely burned at the specified rate, and as there was no legally agreed factor for correcting the light output when the rate of burning departed from the 120 grains/hour—it was a most untrustworthy standard. Furthermore, it was affected by draughts, variations of barometric pressure and degree of humidity of the atmosphere; its only real qualification as a standard was that of simplicity. Oil and pentane flame standards, with or without Methven slits were being tried out, and as a result the Vernon Harcourt 10 C.P. Pentane Lamp became established at a later date as the standard, but here again there were uncertain corrections, for barometer and moisture and also for vitiation of the atmosphere. At this time errors of 10 per cent or more were quite likely.

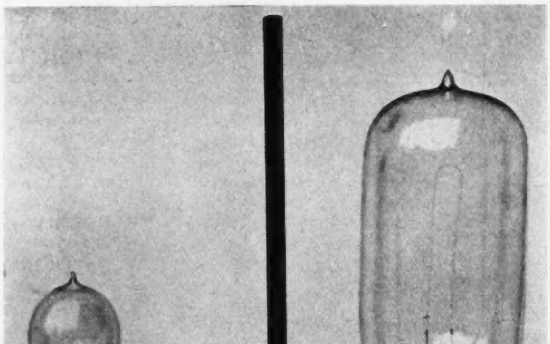

Fig. 2. One of Fleming's "Pendar" large bulb carbon filament standard lamps (*right*) and a contemporary commercial 32 c.p. carbon lamp (*left*)

(Courtesy, The Television Society)

Such then was the unsatisfactory position when Fleming brought his powers to bear on the subject. Owing to his connexion with the Edison and Swan Company as "advising electrician" from 1883 onwards he had ample opportunities of estimating the importance, as well as the difficulties, of accurate photometry.

I cannot do better than take the rest of this section from my friend Arthur Blok's Third Fleming Memorial lecture delivered in 1948, as Arthur Blok himself was also an enthusiast about illuminating engineering.

Speaking of the position at the turn of this century, he says:

"Fleming had long regarded photometric work as a necessary component in electrical engineering training and the light-testing gallery at University College was, according to the standards of the nineties, remarkably well equipped. He seemed to have a prophetic knowledge that electric lighting was soon to become a matter of skilled engineering . . . For years Fleming had been focusing his attention on the possibility of a practical standard of light intensity which would be less variable and more a working tool than the erstwhile oil lamp standards.

"He had turned, therefore, to

incandescent filaments *in vacuo* and he had initiated much work on the changes in luminous emission from carbon filament lamps, whether caused by changes in the filaments themselves or by blackening of the bulbs. At the Pender laboratory at Gower Street we were all in this and would often emerge from the photometric gallery after hours of close work with the Lummer-Brodhun photometer blinking like owls in the noon-day sun. The result of all this work was the setting up of the " Pender " series of standard lamps comprising carbon filaments which had been seasoned *in vacuo* and were then remounted in large new bulbs, so big as to minimise blackening. (Fig. 2.) They may, I think, be regarded as the foundation on which all subsequent practice in incandescent filament standards was based."

(iii) Telephonic and Radio Frequency Research

For a third example of Fleming's method we might take his contributions to the study of the properties of dielectrics at telephonic frequencies. These were partly undertaken in conjunction with the late G. B. Dyke; also his notable work on the Edison effect culminating in the introduction of the " Fleming " valve as the first reliable receiver of radio signals and one with which measurements of signal strength could be made. In addition there is his work on the measurement of the length of electric waves (a " cymometer " is shown in the foreground of Fig. 3) and on cathode-ray tubes.

Enough, however, has been said to show Fleming's method, i.e., that of concentrated study combined with experiment. As the work proceeded he added experimental lectures to scientific bodies, as well as to his students. In each subject which he took up it will be found that a substantial contribution was made to the practical side of the subject, sometimes in the form of a practical contribution to the instrumental side, sometimes by means of an I.E.E. paper, and again at other times in the form of a treatise on the subject.

Electrical Measurements

To present-day engineers it is amusing to recall the primitive arrangements which were in use in the early days for the supply of electric current operating electric arcs in lighthouses. As the generating plant required considerable space, and the fuel used was coal, only lighthouses on the mainland could use such equipment, for example, the North Foreland and the Lizard.

About a century ago, when such sources were introduced, alternating currents were used. The alternator had a set of permanent magnets for its field, and was driven by a steam-engine supplied from a coal-fired boiler. The electric circuits were reduced to as simple a form as possible for the sake of reliability, thus reducing risks of failure of the light to a minimum.

In those days practical electrical measuring instruments were only beginning to be developed, and so no ammeters or voltmeters were included, nor for that matter any fuses, nor any automatic safety devices, as these had hardly been thought of. Thus the attendant had no means of knowing what was the correct speed at which to run his engine to produce the best performance of the electric arc, and I have it on good authority that the attendant ran up his alternator to what he thought was the right speed, and then popped his head out of the engine room to have a peep at the arc. If it was not bright enough he put on a few more revolutions, if too bright he screwed down to stop-valve a bit.

As the months went on the attendant found that he had to run his alternator faster in order to get enough light. This was due to the fact that the permanent magnets were getting weaker with use. When the engine was running uncomfortably fast, a change-over had to be made to a spare set, while the magnets of the first machine were dismantled and re-magnetised.

Such then was the position when many of the leading electricians like Siemens, Swinburne, Wm. Thomson, Evershed, and others, tried their hands at inventing measuring instruments.

As for Fleming, he developed an alternating current voltmeter, the direct current potentiometer and an alternating current wattmeter. Of these only the D.C. potentiometer has survived.

In 1882 his attention was turned to the need for quick and reasonably accurate workshop methods of measurement. Perhaps his mind was further stimulated in this direction by his contact with another pioneer in electrical engineering, the late Col. R. E. B. Crompton.

It is clear that Fleming was the originator of the idea of making the apparatus direct reading by using the simple device of connecting in series with the Poggendorff potentiometer, a continuously adjustable resistance (see Fig. 4) which is adjusted through the medium of a standard cell of known E.M.F., so that the value of any unknown voltage can be read off directly in volts. Avowedly this is a very simple addition, but it resulted in

Fig. 3. The first telecommunications laboratory for undergraduate teaching, University College, London

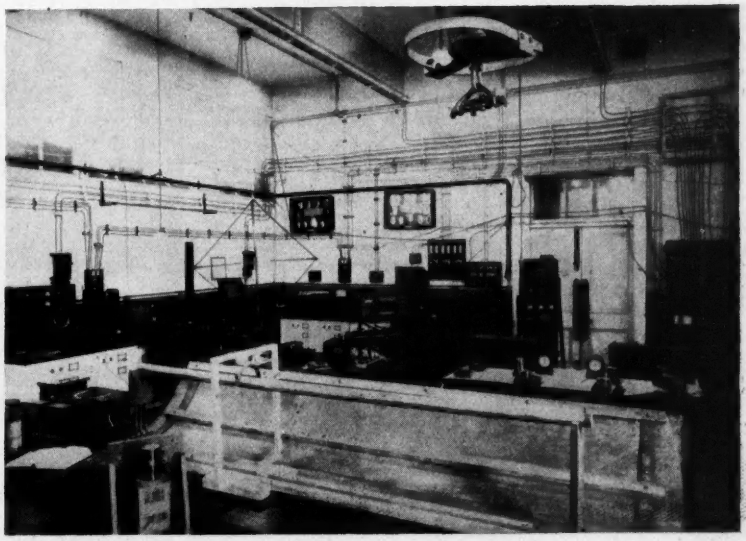

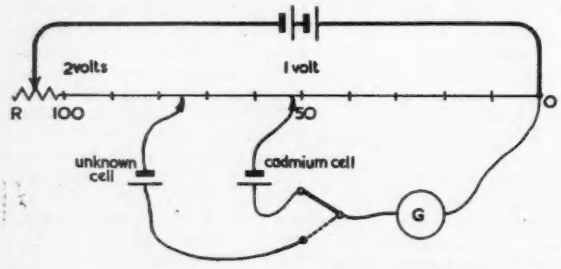

Fig. 4. Fleming's modified Poggendorff potentiometer for direct reading of unknown cell E.M.F.s

the arrangement being adopted almost immediately for practical work. It was in 1883 that Fleming made the first direct reading potentiometer set to read current and voltages in amperes and volts. During the next few years Crompton turned it into a more practical shape, abolishing mercury cups, and altering other items, so that it became more portable.

At first it was possible to attain an accuracy of perhaps ¼ per cent. Nowadays, owing to the better knowledge of materials available, and to the introduction—first of the Clark cell and later of the Weston cadmium cell, the accuracy of such measurements has been increased by at least one hundredfold, but even in its modern form it still embodies the Fleming principle of direct reading, and the Crompton desire for compactness and portability; indeed, as we all know, it has become an absolute necessity for any laboratory worthy of the name.

Quite naturally such pioneering work in the field of electric measureing instruments and their use in testing dynamos and other apparatus forced upon Fleming the real need for the establishment of some authoritative body which could certify as to the correctness of their indications.

Urged by this conviction we find in 1885, Fleming prepared a paper to read before the Society of Telegraph Engineers and Electricians (later to become our I.E.E.) entitled "On the necessity for a National Standardising Laboratory for Electrical Instruments" which resulted in a proposal for a National Electric Standards Laboratory.

However, though this paper may be considered to be the starting point of the movement, it was not until 1890 that the Board of Trade Electrical Standards Laboratory (Fig 5) was established, at first under the direction of Major Cardew, and later Mr. A. P. Trotter. The work of this laboratory was finally transferred to the National Physical Laboratory, Teddington, which was founded in 1901.

Measurements at Radio Frequencies

Many years later when the new subject of electric wave telegraphy was being developed, Fleming again turned his attention to devising measuring instruments, this time suitable for the new technique.

Thus we find him at work on apparatus for the measurement of small capacitances and inductances, and such apparatus was developed in conjunction with his right-hand man, Mr. (afterwards Professor) W. C. Clinton, while later on, with the help of his assistant, Mr. G. B. Dyke, he developed other apparatus and carried out tests in this new field.

Then his electric wave measurer—called by him a cymometer—was probably the first practical device for measuring the length of long electric waves. This was in 1905.

Popular Scientific Lectures

No account of Fleming's activities could have any semblance of completeness were it not to make reference to his popular scientific lectures. Fleming's ideal in these lectures was that of Michael Faraday, and I venture to think that Ambrose Fleming was a very good second to that "prince of scientific lecturers."

Quite apart from his highly successful Christmas lectures for juvenile audiences at the Royal Institution, Fleming was in great demand by many of the larger provincial lecture societies from Greenock in the north to Portsmouth in the south. In one session he delivered 24 such lectures, practically all of which were experimentally illustrated. Many of the experiments were devised to be shown as shadows of miniature apparatus working in the lantern slide carrier, thus being easily visible to the entire audience and at the same time contributing greatly towards portability.

Retirement at Sidmouth

On Fleming's retirement in 1926 he settled at Sidmouth, where he had built a house.

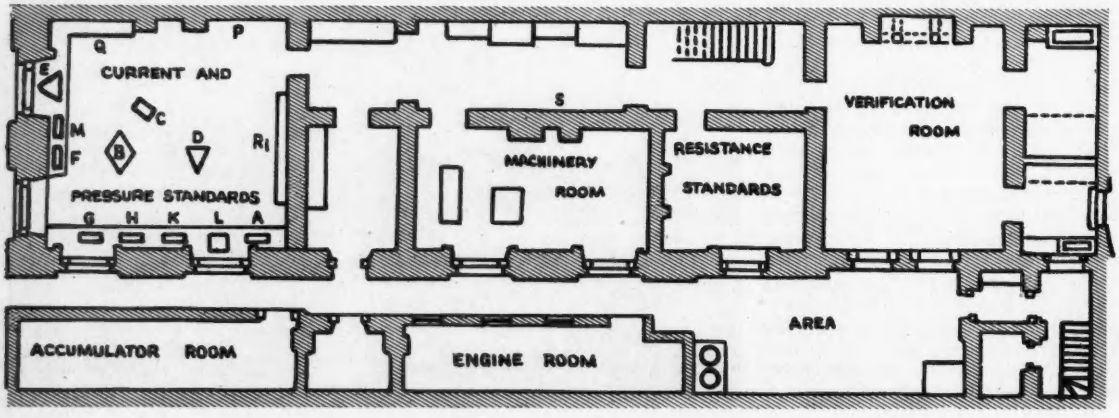

Fig. 5. Floor plan of the Board of Trade Electrical Standards Laboratory where measurements commenced in 1894

For some years he often went up to London visiting his old college, and, as Dr. W. H. Eccles writes in "Nature," he (Fleming) "was quick in his movements. This celerity was characteristic; even when he was in the middle seventies, one could see his linear figure threading quickly a populous corridor in the College, intent on a goal, looking neither right nor left, overtaking everybody. Indeed, in intellectual as well as material things Fleming's main principle of action was full-speed ahead."

In 1933 he married as his second wife Miss Olive May Franks, "a singer of wonderful charm"—who survives him.

For over fifteen years he was president of the Television Society of London. He was an ardent supporter of the late J. L. Baird—that remarkable inventor of television whose success was due to his foresight and continuous pertinacity in spite of great opposing forces. Fig. 6 shows the two friends together on the occasion of a television demonstration.

Honours came to Fleming late in life, but when they did come they were showered upon him. In 1929 he received a knighthood, and, among other honours, the Hughes Medal of the Royal Society. He was made Emeritus Professor in the University of London in 1926, Honorary Fellow of St. John's College, Cambridge, 1927, Faraday Medallist of the I.E.E., 1928, and was awarded the Radio Medal, U.S.A., 1933, and the Franklin Medal, U.S.A., 1935.

Conclusion

Fleming was always intensely interested in any phenomenon connected with sparks, arcs and the discharge of electricity in semi-vacuous spaces such as the old-fashioned Geissler tubes and the modern neon tubes, the production of X-rays and the Edison effect, i.e., the conduction of negative charges across vacuous spaces.

He examined experimentally with enthusiasm the Edison effect on his return from America in 1885, reading a paper to the Physical Society of London on his experiments and giving a Friday evening discourse at the Royal Institution, London.

Later, in 1896, he made a further study of these effects, the results being published in a Physical Society paper in that year. About the same time he studied the focusing of a beam of cathode rays by means of a short or squat solenoid and also the properties of X-rays, and later the subject of photo-electricity.

It will be noticed that all these have to do with the behaviour of electricity in spaces between solid (or liquid) conductors, in fact, studies of the behaviour of free electrons in gases or rarified spaces.

It is now clear that such studies were a first-class preparation for the understanding of the subject of electronic engineering which was yet to be born, thus preparing Fleming to make the great advance of the application of the Edison effect to radio-telegraphy reception. It shows the importance of taking a lively interest in new phenomena which may not be obviously of direct value to one's immediate work, if one has reasonable hope of making major contributions to one's profession.

The younger generation of scientists and engineers have not perhaps such opportunities of making radical new discoveries in our profession as had Fleming and his contemporaries, but there is no doubt whatever that any young man or woman who essays to make electronic engineering his or her life's work, should, like Fleming, see to it that their knowledge rests on broad foundations, including such subjects as physics and mathematics, and for that matter chemistry. By so doing, when any new discovery comes along they will be able to get to grips with the fundamentals of the phenomenon, and thus be in the forefront with those who are able to use such knowledge with certainty for practical applications.

In Fleming's life we see this aspect illustrated time and time again, e.g., in the case of the practical application of transformers, the development of electric lamps of the filament type and in the invention of the radio valve—to take only three cases.

In addition to such individual pioneering, the importance of trying to understand the other fellow and his point of view is becoming more and more essential, as much of our scientific work, especially on the engineering side, has to be done by teams. This side of present-day research and development cannot be overstressed. The days for such men as Faraday, Hughes and Heaviside may be largely over; they ploughed their lone furrows; instead, we find the loosely-knit teamwork led by such men as Sir J. J. Thomson and Sir Ernest Rutherford with "families" of scientists or the equally important teamwork of such groups as, for example, the T.R.E., which have come to the front in recent years.

Fig. 6. Sir Ambrose Fleming and J. L. Baird in the Baird Television Company's studio at the Crystal Palace, 1936.

(Courtesy T. M. C. Lance)

Bibliography.

"Memories of a Scientific Life," by Sir Ambrose Fleming. Marshall, Morgan & Scott.

"Ambrose Fleming — His Life and Early Researches," by Prof. MacGregor-Morris, *Jnl. Telev. Soc.*, Vol. 4, No. 11, Sept., 1946.

"Some Personal Recollections of Sir Ambrose Fleming," by Arthur Blok, *Jnl. Telev. Soc.*, Vol. 5, No. 8, Nov., 1949.

An Experimental Crystal Amplifier

WRITING in *Radio-Electronics* for May 1949, Rufus Turner describes an experimental Transistor which was made for him by R. Jacobson, using a 1N34 germanium diode. As these rectifiers are fairly readily available from surplus disposal stores, this account of the making of a Transistor is reproduced for the benefit of those wishing to experiment with the new amplifier.

An account of the operation of the Transistor was given in ELECTRONIC ENGINEERING for September 1948. The following notes deal with the construction and testing of the unit. Two 1N34's will be required to provide the two catswhiskers, leaving a spare crystal.

The 1N34 consists of two threaded brass end plugs which are screwed into opposite ends of a small ceramic tube. The tungsten whisker is soldered to one of these plugs and rests upon the surface of the germanium wafer. The wafer is soldered to the end of a brass pin passed through a central hole in the other end plug and held by a setscrew. These parts are all shown, ready to go together, in Fig. 1. After adjustment at the factory, the ceramic tube is filled with wax. This wax has been injected through a hole in the side of the ceramic tube; this hole served previously for an access point through which the whisker could be moved about to various spots on the germanium surface during electrical adjustment.

Fig. 1. An exploded view of the transistor when ready for assembly

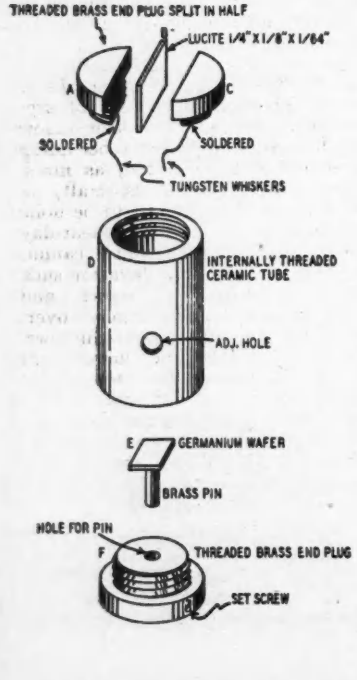

After obtaining two 1N34's, the first step in the construction of the triode is carefully to pick out the sealing material which plugs the hole in the ceramic tube of each unit. This may be done with a needle, being cautious not to dig any deeper into the unit than the thickness of the ceramic wall. The next step is slowly to melt out the wax by heating the entire unit. Hold it high over a low flame. Make no attempt to rush this operation. The wax will run out through the side hole. After the wax has been expelled, the tinned ferrules which hold the pigtails may be peeled off the end of each unit with the aid of diagonal cutters. This will expose the two brass end plugs which then may be unscrewed.

After removing the end plugs, unsolder the whiskers from their plugs and bathe them in carbon tetrachloride. The next step requires painstaking care: saw one of the whisker plugs vertically in half, using the thinnest obtainable jeweller's saw blade, to obtain the two separated halves as shown as parts A and C in Fig. 1. Solder one whisker to each half. The tungsten wire is a little tricky to solder and may require acid soldering flux. If the latter is used, wash the finished job thoroughly in strong soapy water, give several rinsings in clear water, then dry the parts and bathe them in carbon tetrachloride. Next, using Duco cement, fasten the two halves of the split end together with an insulating separator (part B in Fig. 1) made from Lucite or Plexiglas 1/64 in. thick. Be careful to keep the threads of the split plug aligned. Then, with a needle, toothpick, or slender tweezers, bend the tips of the whiskers together until they have the smallest separation without actually touching each other. It will help to use both a magnifying glass and continuity meter in this operation.

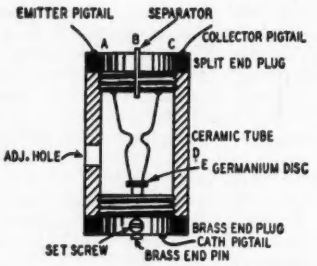

Fig. 2. The assembled crystal amplifier

Screw the two-whiskered plug back into one end of the ceramic tube, and the germanium-holding plug F into the other end. Using a magnifying glass look through the tube hole to see whether the whiskers are both in contact with the germanium surface and also whether threading in the germanium plug has twisted them. If the whiskers are twisted or are touching each other, separate them with a needle or tooth-pick inserted through the hole. If they are spread too far apart, push them closer together with the needle. If the whisker tips are not in contact with the germanium surface, loosen the setscrew in the germanium end plug and cautiously push the end of the germanium pin inward by means of a pin inserted into the centre hole of the plug, until contact is made. Then retighten the setscrew.

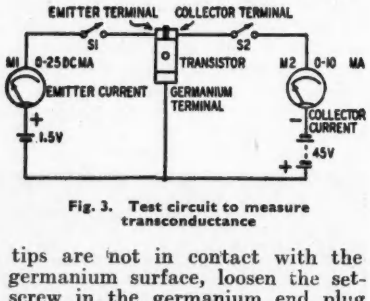

Fig. 3. Test circuit to measure transconductance

The final step is to solder a wire pigtail lead to each half of the split whisker plug (A and C in Fig. 2) and also to the germanium plug F. The soldering operation must be completed quickly in order not to melt the solder holding the whiskers or damage the germanium wafer.

Throughout the construction, take care not to handle the germanium wafer or the whiskers with the fingers any more than is absolutely necessary. If there has been exces-

sive handling, both the whiskers and the germanium wafer should be bathed in carbon tetrachloride or lacquer thinner.

Fig. 2 shows how the completed transistor assembly appears in cross section. Letter symbols are the same as those in Fig. 1. The distance between the catswhiskers is exaggerated in the sketch.

Adjustment

After the unit has been assembled, set up the test circuit shown in Fig. 3, and test the crystal triode according to the following procedure. Either half of the split end plug may be chosen as emitter or collector.

1. With switch *S*2 open, close switch *S*1. The emitter current, read with milliammeter *M*1, should not exceed 20 mA and undoubtedly will be in that neighbourhood at the outset.*

2. Open *S*1 and close *S*2, The collector current, read with milliammeter *M*2 should not exceed 0.5 mA.

3. If emitter or collector current is in excess of the values given, reverse the emitter and collector terminals and repeat steps 1 and 2. If the currents still are excessive, unscrew the germanium end plug, loosen the setscrew, and rotate the germanium pin to expose new surface points to the whiskers. Reinsert the end plug, respace the whiskers.

4. Close switch *S*2 and record the reading of milliammeter *M*2 as *I*1.

5. Leaving *S*2 closed, close *S*1, noting the new reading of milliammeter *M*2. Record this second *M*2 deflexion as *I*2.

6. The transconductance is

$$\frac{1{,}000\ (I2 - I1)}{1.5}$$ micromhos.

The builder should aim for the highest transconductance he can obtain with a given germanium wafer. Magazine articles have reported transconductances as high as 15,000 micromhos. The author has found that transconductances of 1,000 to 3,000 (comparable to such tubes as the 6J5, 6SQ7, 6T7, etc.) may be obtained readily with little or no adjustment on a transistor of the type described in this article. Rotating the germanium wafer to expose better spots to the two whiskers has yielded transconductances a little higher than 5,000.

After all adjustments are completed, the side hole in the ceramic tube should be closed with a small piece of Scotch tape. We do not recommend filling the interior of the unit with any of the waxes ordinarily available to the home experimenter.

* The Editor of *Radio Electronics* comments that the 20 mA emitter current is very much greater than the figures commonly published. These range from a fraction of a milliampere to 1 or 2 mA. Transistors made by different experimenters vary widely for reasons still unknown. The performance of transistors made by readers therefore may be entirely different from that of the one described here.

DISCRIMINATOR ADJUSTMENT

A DIFFICULTY encountered in the lining-up of discriminators in F.M. receivers or in A.F.C. circuits is that the test instrument, connected into the circuit for the purpose of alignment, introduces an additional capacitance. The adjustments are carried out with this capacitance across the circuit and, when the test instrument is disconnected, the circuits will no longer be in correct adjustment.

A method of avoiding this error is to provide a valve voltmeter in the form of a diode with a load resistor permanently connected in the circuit. For instance, the diode may be connected to the anode of a valve driving a Foster-Seeley form of discriminator and the low potential end of the resistor may be earthed through a link. When adjustments are to be made, the earthing link is replaced by a suitable microammeter. Alignment consists in adjusting the primary circuit for maximum deflexion and the secondary circuit for minimum deflexion.

If, for economy, it is desired to incorporate the voltmeter diode in the same envelope as that used for tuning indication, it will usually be found that the coupling between them is undesirably large. This may be nullified, without loss of economy, by using a double-diode-triode valve with the two diodes strapped together as a part of the tuning indicator circuit and the grid-cathode portion as the voltmeter diode. The necessary shielding between the two circuits is conveniently achieved by earthing the anode.

The Figure shows a circuit which uses these principles.

—Communication from E.M.I., Ltd.

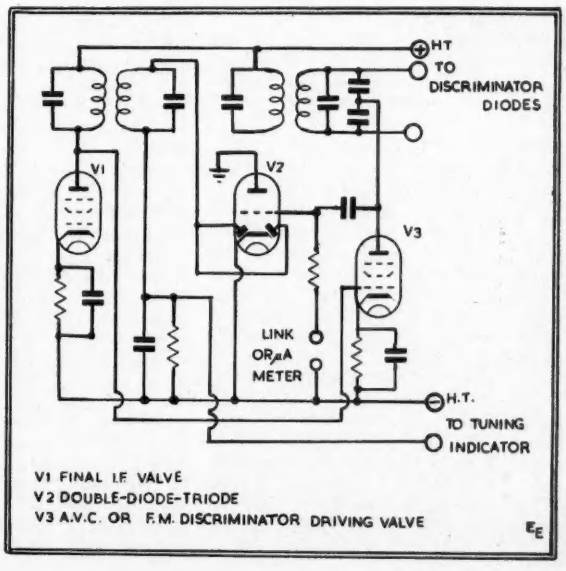

The schematic shows a double-diode-triode valve used in the application described. The two diode anodes are strapped together for tuning indication, and the grid becomes the anode of the voltmeter diode

IONISATION IN GASES—

The Ionisation Chamber and the Geiger Counter

By T. H. D. ATTEWELL, B.Sc., M.I.R.E.

IT has long been known that air, an insulator for all practical purposes, can become conducting in the presence of X-rays and of radioactive substances, and that this is due to the formation of ions and free electrons in the gas. To obtain a picture of the process of ionisation it is helpful to examine the energy relationships of an electron with the atom of which it forms a part.

For simplicity we shall consider first the hydrogen atom, which has a nucleus consisting of one proton, with which is associated one orbital electron. Now it was first suggested by Bohr that the extra-nuclear electrons in an atom can move only in certain definite "permitted" orbits, and that radiation occurs discontinuously in discrete "wave-packets," called quanta, when an electron makes what is, effectively, an instantaneous transition from one permitted orbit to another nearer the nucleus. This is shown diagrammatically in Fig. 1. He further postulated that the energy of the quantum is proportional to the frequency (ν) of the emitted radiation, or:—

$$E' = h\nu \quad \ldots\ldots\ldots\ldots\ldots\ldots \quad (1)$$

where h is Planck's constant, having the dimensions of action and being equal to 6.624×10^{-27} erg. sec.

With each permitted orbit there is associated a particular total energy E (kinetic plus potential) for an electron placed in it. This total energy is readily calculated for the simple Bohr picture of the hydrogen atom, in which one assumes circular orbits, and also that it is only the angular momentum of the electron which is quantised, that is, restricted to "permitted" values only. It is found that these values are given by $nh/2\pi$ where n is a positive integer, called the principal quantum number, having the possible values 1, 2, 3, . . . etc.

The derivation is given in the Appendix, and, by substituting for

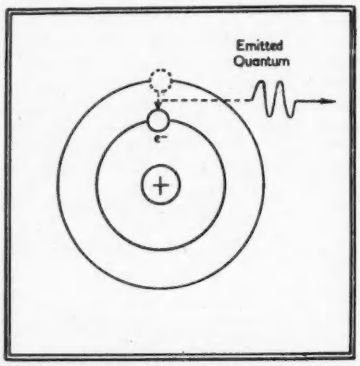

Fig. 1. Electron jump accompanied by the emission of a quantum of radiation

the various quantities in the relation found there we can calculate the value of E for the innermost orbit by putting $n = 1$. Similarly, by putting $n = 2, 3, \ldots$ etc., we derive the value of E for orbits successively further out. Writing these as $E_1, E_2, E_3, \ldots$ etc., respectively, they may be illustrated by the energy-level diagram of Fig. 2. The lowest level E_1 is known as the Ground State and is represented by a horizontal line. Above this are drawn further lines to represent the other permitted levels E_2, E_3, . . . the spacing between these lines corresponding to the differences in energy which they represent. Since $E \propto 1/n^2$, the lines become closer as their level rises until they merge at the terminating level E_n where $E = 0$, (at all other levels E is negative in sign). An electron reaching this level can be said to have escaped from the atom in doing so, and leaves behind a positively charged ion. The energy step marked ϵ_1 is therefore the energy needed to ionise a hydrogen atom in the ground state. Since this involves removing unit electronic charge, we may refer to this step as the ionisation potential, and express it in volts.

The steps P_1, P_2, . . . are the first and second . . . etc., excitation potentials. An electron might be raised from the ground state to E_3 (say), by the absorption of energy. The atom is then said to be "excited." If the electron now returns direct to the ground state a photon will be emitted according to the relation

$$E_3 - E_1 = h\nu$$

It must be noted that the above discussion is a simplification of the problem. We have restricted ourselves to circular orbits, and have introduced only one quantum number (n). In fact four quantum numbers are needed to describe the system completely, and we are obliged to relinquish our fixed orbits in favour of the more nebulous concept of a probability-functional charge distribution in space. In more complex atoms the energy levels fall into a number of groups, and not all the possible transitions between levels are permitted.

However, the general picture of ionisation so far given, using hydrogen as an illustration, is sufficient for our purpose, and ionisation in complex atoms can be regarded as the removal of one or more of the outer (valency) electrons. The energy required is not readily calculable as for hydrogen, but may be found experimentally. Some excitation and ionisation potentials are collected for reference in Table 1.

For a more complete treatment of

Fig. 2. The energy-level diagram

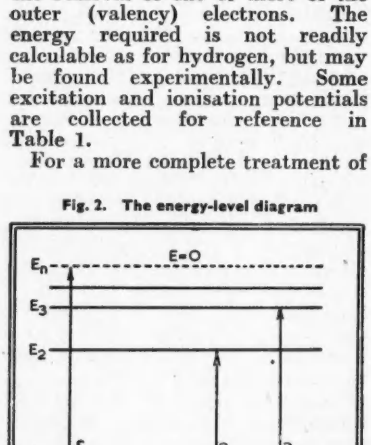

* E. K. Cole, Ltd.

the subject a specialised account may be consulted.[1]

Negative Ions

In addition to ionisation by the loss of an electron, there is a second ionising process. Some atoms in particular show a tendency to acquire electrons in excess of their normal complement, so forming negative ions. Fluorine, chlorine and oxygen are typical examples. The tendency to form negative ions is predictable from the electron affinity of the atom, defined as the energy set free when enough electrons are added to a gram-atom of the element to convert the whole to ions of normal valency. For fluorine this amounts to 98.5 K.cals. mole^{-1}, while for oxygen it is negative, being −168 K.cals. mole^{-1}. Thus energy is liberated when fluorine "adds on" electrons, and absorbed when oxygen does so, consequently the latter forms negative ions less readily than the former. Negative ions will be referred to in connexion with Geiger counters, but ignored in Ionisation chambers, where their presence does not materially affect the present discussion.

Mobility and Recombination of Ions

If ions are produced at a steady rate, by, let us say, X-rays, in a volume of gas across which a constant potential is maintained between a pair of electrodes, then negative ions and electrons will drift toward the anode, while positive ions move toward the cathode. Under unit field (1 volt/cm.) the velocity for ions is of the order of 1 cm./sec. at normal pressures, and is much higher for electrons, the value for the latter depending on the nature of the gas. The velocity in cms./sec. under unit field at 0° C. and 760 mms. pressure is termed the mobility.[2]

In a system such as that indicated above, not all the ions are actually collected by the field, and in the absence of the field ions do not accumulate indefinitely, even though they are being formed at a constant rate. The reason is simply that ions of opposite sign, or ions and electrons, are frequently in collisions resulting in charge neutralisation with formation of neutral atoms, and equilibrium is reached between the three processes—formation, collection, and recombination. It may be shown very readily that the rate of recombination is proportional to N^2, where N is the number of ion-pairs present, and that recombination alone, in the absence of formation and collection, occurs according to the law:—

$$dN/dt = -\alpha N^2$$

where dN/dt is the rate of disappearance of either kind of ion and α is a constant.

The Townsend Avalanche

If the gas pressure in the system is now reduced, the mean free paths of the particles are increased proportionally. By reducing pressure and increasing the field it is possible to arrive at a condition where an electron (say) is sufficiently accelerated to enable it to eject another electron from the next atom it strikes. The ejected electron may now ionise a further atom. The whole process is cumulative, and results in an avalanche of ions, which may have been started by one electron only. The phenomenon is named after Sir J. Townsend, a pioneer in these studies, and is also referred to as "gas amplification."

Ionising Agents

We may now very briefly summarise the more important ways in which the energy needed for ionisation is provided. These are:—

(a) Collisions with particles whose kinetic energy is used up in ionising the neutral atom and in imparting kinetic energy to the resultant ions. The particles with which we are concerned are ions and electrons already present, electrons from radioactive disintegration (β-particles) and helium nuclei (α-particles).[3] (b) Ionisation by X-and γ-radiation.[4] Of the various possibilities here, two will be sufficient for our immediate consideration:—

(i) The photoelectric effect. An incident photon is completely absorbed by a neutral atom and an electron is rejected. The photon energy appears as ionising energy plus the kinetic energy of the ions formed. Photoemission is proportional to (approximately) the fourth power of Z, the atomic number of the material irradiated.

(ii) The Compton effect. Here the photon is elastically scattered from an electron in an atom, the electron recoiling out of the atom. The emergent photon thus has an energy lower than it had on incidence, but may still be able to ionise further atoms. The effect is relatively independent of Z, and occurs at higher energies than the photoelectric effect. For γ-rays of energy around 5 KeV. and below, nearly all electrons ejected are photoelectrons. At about 100 KeV. the proportion is 80 per cent Compton and 20 per cent photoelectrons, while above 800 KeV. only the Compton effect is of major importance.

Classification of Counters

We have seen how neutral gas atoms may give rise to ions when they absorb radiation of sufficiently high energy (low wavelength), or are in collisions with various particles. The collection of ions so formed provides a method whereby such radiation and/or particles may be detected, and we may now

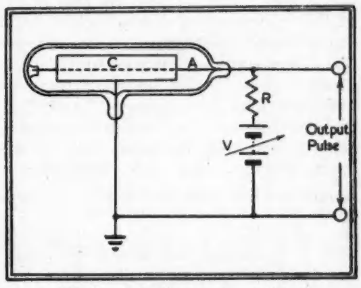

Fig. 3. A basic counter system

examine the various types of detector, more usually termed "counters," using this principle.

Consider the simple arrangement of Fig. 3. Some suitable thin-walled container is provided with a wire anode (A), and a concentric cylindrical cathode (C), and is filled with a simple gas at low pressure, let us say Argon at 10 cm. Hg. The cathode is earthed, and the anode is connected to a variable potential (V) through a resistor (R). Imagine that one single α-particle, entering the space between anode and cathode, gives rise to 10^4 ion pairs, but that a certain β-particle gives only 100 ion pairs on entry. When the voltage V is being applied, either of these events will result in a burst of ions being collected, and hence a voltage pulse appearing across R. We now plot the amplitude of this pulse against V for each of the two events as in Fig. 4, which is not to any particular scale.[5]

Between the origin and A, the pulse heights increase with V as more and more ions are collected

before they can recombine. Between A and B, the heights are independent of V and are proportional to the initial number of ions formed. In this region the counter is said to function as an ionisation chamber, and it is apparent that the counter is saturated, that is, for all practical purposes, the whole of the ions initially formed are collected. Until B is reached there is no gas amplification. Above B, however, the field is sufficient to produce gas amplification, and larger pulses are recorded. Between B and C the pulse amplitudes remain proportional to the initial number of ions, and a counter operating in this region is known as a Proportional Counter. The gas amplification factor rises steadily over the region BC, being of the order of 10^4 at C, and continues to rise in the region CD, where, however, the pulse amplitude is no longer proportional to the initial ionisation, rising more rapidly for smaller numbers of ions than for higher. At D, both initial events give output pulses of the same height, and this is the criterion for the commencement of

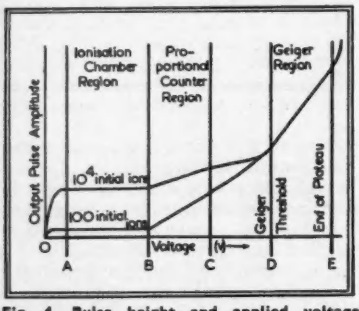

Fig. 4. Pulse height and applied voltage relations in the counter of Fig. 3, taken from S. A. Korff: "Electron and Nuclear Counters," (D. Van Nostrand Company Inc, 1946)

the Geiger region, which extends from D to E. Here the pulse height continues to rise with applied voltage as the gas amplification factor increases, but above E the counter goes into a continuous discharge. Although called continuous, this discharge actually consists of a large number of separate and overlapping breakdowns, in which the gas amplification factor may rise as high as 10.[8]

In this manner three types of counter are distinguishable: the Ionisation Chamber, the Proportional Counter, and the Geiger Counter. Each has its own sphere of especial usefulness, but here we shall confine ourselves to the first and last types, which are perhaps in more general use than the Proportional Counter.

The Ionisation Chamber

Ionisation chambers are used mainly for the measurement of X- and γ-radiation and for the qualitative detection of β-particles, and form the basis of numerous health monitors.[6, 7]

The usual arrangement of this class of instrument is shown in Fig. 5. The chamber (*C*) consists of two electrodes held at about 20-100 volts apart by the battery (*B*), and contains the gas, which is usually air at ordinary temperature and pressure. Ions formed in *C* give rise, when collected, to an ionisation current (*i*), which, flowing through a high resistor (*R*), provides the input for the electrometer circuit. (*E*). Indication is usually by a meter directly calibrated in dosage, expressed in röntgens per hour. The electrometer circuits may follow conventional practice and will not be discussed further.

The design of the chamber may be pursued along the following lines. First, the necessary volume of gas must be fixed, since the total ionisation produced by steady irradiation is proportional to this quantity. From the circuitry to be used we find the maximum input voltage required for a full-scale reading of whatever intensity it is desired to measure. Suppose this turns out to be one volt for one röntgen per hour. We next select a value for the input resistor, such that the input time constant is not too high, remembering that the total input capacitance may well lie in the region 10-50 *p*F. Suppose we choose 10^{10} ohms, so that the time constant will not exceed 0.5 sec. Then the ionisation current required will be 10^{-10} amp.

Now one röntgen produces 1 *e.s.u.* of charge in 1 c.c. of air at 0° C. and 760 mm. pressure by definition, so that for 1 röntgen per hour in 1 c.c. of air the ionisation current will be $1/(3600 \times 3 \times 10^9) = 9.26 \times 10^{-14}$ amp. In general, if V is the required volume in c.c., Rg the radiation received in röntgens per hour, and i the ionisation current, then

$$i = 9.26\ V.Rg \times 10^{-14} \text{ amp} \quad \ldots (2)$$

In the above case, therefore, the required volume will be 1080 c.c. In calculating the volume it is advisable to allow for the worst circuit conditions (input resistor on lower tolerance limit, etc.) and then provide a calibration control which reduces the sensitivity of the circuit under better conditions.

We have now to fix the form of a chamber to give the calculated volume, and to satisfy two other conditions, namely, to have the lowest practicable electrical capacitance, and to have an even field distribution. The first of these conditions keeps down the input time-constant, while the latter is necessary if high polarising voltages are to be avoided. If "pockets" of low field are present, recombination is encouraged, and is always proportional to N^2 as we have seen, so that as the incident radiation increases in intensity, more volts must be

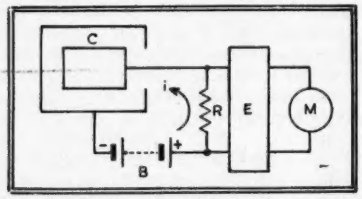

Fig. 5. Block schematic of an ionisation chamber instrument

applied to collect the same proportion of the ions as before. The effect is present in all practical chambers, but becomes serious, introducing non-linearity of scale, where the chamber shape is unfavourable. An example is shown in Fig. 6, where saturation curves for two chambers are reproduced. The three full curves are for a typical cylindrical chamber of some 450 c.c. volume, the indicated intensity (% of *F.S.D.*) being plotted against the chamber voltage for each of the three incident intensities shown. The dotted curve is for the same system, the outer cylindrical wall being replaced by one of square section so as to enclose the same free volume. It is always wise to determine such curves, using an X-ray source for convenience, when a new design of chamber is constructed, so that one can tell at a glance whether the proposed polarising voltage is adequate for the application in mind.

The most usual arrangement to avoid field discontinuities, as far as possible, uses two concentric cylinders as the electrodes. Now, for a point distant r from the axis of two such cylinders of radii r_c, r_a, the field

X in terms of the applied voltage V is given by:—

$$X = \frac{V}{r \log_e (r_c / r_a)} \quad \ldots\ldots\ldots (3)$$

Hence to enclose a given volume between the cylinders, making X as high and as linear as possible, r_c and r_a should be made large, so that $r_a \rightarrow r_c$. Against this must be set the considerations of total bulk and chamber capacity. As a guide to what may be acceptable in practice the chamber used in the experiment of Fig. 6 had the dimensions:—

Collector (anode) 3.8 cm. dia × 6.7 cm. long.

Outer wall (cathode) 8.6 cm. dia. × 9.2 cm. long.

Capacitance approx. 15 *p*F, assembled, with guard ring.

Next the material for the collector and outer wall must be chosen. When this material is irradiated, electrons are produced by the photoelectric effect and by the Compton effect as outlined above. For γ-ray energies below about 5KeV., nearly all the electrons arise from the photoelectric effect, while above about 800 KeV., nearly all arise from the Compton effect. Since, as stated before, the *P.E.* effect is proportional to Z^4, and the *C.E.* is independent of Z, it follows that the number of electrons removed from the wall and entering the gas will be greater, pro rata, at lower radiation energies than at higher. Now the röntgen is defined in terms of ionisation in air ($Z \approx 7.7$), hence, if the device is to read röntgens directly for all intensities, the solid material of the chamber must also have $Z \approx 7.7$. Many hydrocarbon materials satisfy this requirement to a good approximation, and presspahn, S.R.B.P., etc., are satisfactory. Since a conducting surface is necessary, they must be coated with colloidal graphite. Alternatively, one may use a metal wall (e.g., brass) and line the inside of the outer cylinder and the outside of the inner one with presspahn. This suppresses photoelectrons formed in the brass, and acts effectively as an air wall. Again the inner surfaces must be coated with colloidal graphite, preferably the naphtha- or alcohol-based types, which do not appear to give rise to distortion on drying out. The thickness of all walls must be sufficient to ensure equilibrium between the incident radiation and the ejected electrons, i.e., an electron ejected just at the outer surface must be stopped within the wall thickness. About 1 mm. is usually chosen. If very low energies are to be measured the wall may have to be reduced to permit γ penetration, but the measurement of extreme ranges is outside the scope of this article.

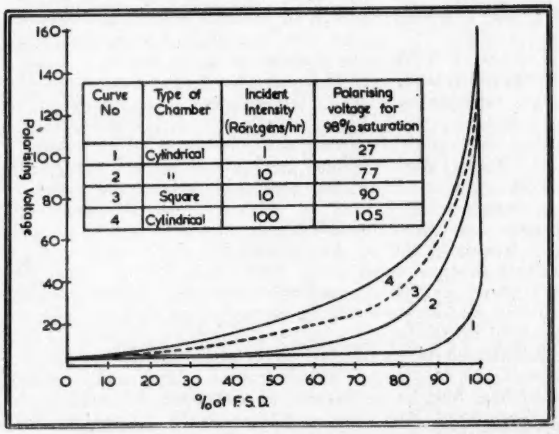

Curve No	Type of Chamber	Incident Intensity (Röntgens/hr)	Polarising voltage for 98% saturation
1	Cylindrical	1	27
2	"	10	77
3	Square	10	90
4	Cylindrical	100	105

Fig. 6 (*left*). **Measured saturation curves for an ionisation chamber**

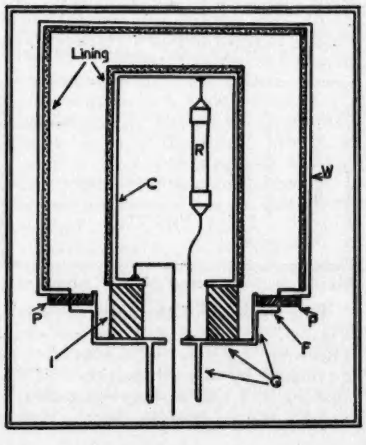

Fig. 7 (*below*). **Section showing a typical chamber construction**

Detection of β-particles

β-particles cannot be measured quantitatively by the Ionisation Chamber unless the type and geometry of the source are known, but they may be detected qualitatively by allowing them to enter the chamber by a thin window. This may be of wire gauze dipped in a solution of distrene and allowed to dry, thus giving a film of distrene a few mils. thick, and coated thinly on the inner surface with colloidal graphite. The window is made to form part of the outer wall, and should be arranged so that the solid angle for the entry of β-particles from an external point source into the free volume of the chamber is as large as possible. When not in use the window may be covered externally by a metal flap so that γ measurements may be made in the presence of β background if desired. The gauze used may be of mesh between 40 and 80 per square inch, and the wire of which it is made should be as thin as possible, to avoid undue absorption of the β-particles by the metal.

The Guard-ring and Insulator

In Fig. 7 is shown a diagrammatic representation of a complete chamber. The collector electrode (*C*) is supported on the main insulator (*I*), which in turn is fixed to the guard-ring (*G*). This carries a flange (*F*) on which the outer wall (*W*) is supported via an insulator of paxolin (*P*). Regarding the main insulator, a resistance three orders higher than the input resistor used, or in any case not less than 10^{14} ohms, should be aimed at. Volume resistivity is seldom troublesome, but the surface must be lyophobic and perfectly smooth and free from machining marks. Moulded polystyrene or polyethylene are frequently used, but glass should be avoided unless silicone treated; even then it is not completely trustworthy. The insulator must not be handled; it may be cleaned in pure methyl- or ethyl alcohol (A.R.), after which it must be dried thoroughly before use, since the alcohols are slightly conducting.

The guard-ring avoids the appearance of the supply voltage across the main insulator, prevents the col-

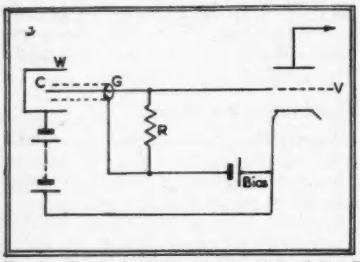

Fig. 8. Connexions to the chamber of Fig. 7

lector from "seeing" any random potentials outside the chamber, and also prevents the deposition of ions on the insulator, which should not be able to "see" any part of the outer wall. The chief practical difficulty is to make the guard-ring effective without too much increase in chamber capacitance, but the design is, fortunately, not over-critical and there is seldom much trouble involved in meeting the requirements. Fig. 8 shows the connexions to the chamber and guard-ring as used with an electrometer (V).

Since quite small changes in the capacitance of the system produce appreciable input voltage changes in the amplifier, most ionisation chambers tend to be microphonic. Their construction must therefore be made rigid, and, if necessary, they may be elastically mounted together with the electrometer valve and input resistor. Often the latter may be conveniently mounted inside the collector, as in Fig. 7, while some of the smaller electrometers can be stowed inside the guard-ring or an extension provided thereon for the purpose.

Geiger Counters

We now pass on to counters operating in the Geiger region DE of Fig. 4. In this type we are interested in counting the output voltage pulses due to the arrival in the counter of individual particles, and the operation is quite different from that of the ionisation chamber. The construction is, again, normally concentric, but the central cylinder is made of wire of the smallest practical diameter in order to make the field intensity as high as possible near the wire. The gas filling may be one of two types which give vastly different characteristics to the counter, and these will be considered separately. The first type is a simple gas at about 10 cm. Hg. pressure (Argon is a common choice), giving what is known as an externally quenched, or non-self-quenched counter.

The non-self-quenched counter

The anode is connected via a resistance to a source of D.C. of about 1-2 KV. Let us now see what happens when an initial ionising event occurs in the counter due to the arrival of a particle. A free electron liberated by this event is accelerated toward the anode. The operating conditions in these counters are such that the electron acquires enough energy to produce further ionisation when in the high field region near the wire, and here an avalanche is formed in the manner previously described. Not all the ionisation produced arises directly, some is the result of indirect processes. For example, while yet some distance from the wire, an electron may gain enough energy to excite, but not ionise, a gas atom. This atom shortly returns to the ground state, emitting a photon, which may give rise to a photo-electron on interaction with the cathode wall. This electron now produces further ionisation, and so on. Since most of the ionisation occurs near the anode, the electrons, with their high mobility, are rapidly collected, leaving a positive ion sheath around the anode. The positive ions move out more slowly toward the cathode, and this action is equivalent to a steady increase in the effective diameter of the anode, as a result of which the field intensity, given by Equation 3, falls off until it can no longer support the formation of further avalanches, and the discharge ceases. The ions are then collected, in a time of the order of 10^{-4} sec., while the separation of charge is recorded as a voltage pulse across the series resistor.

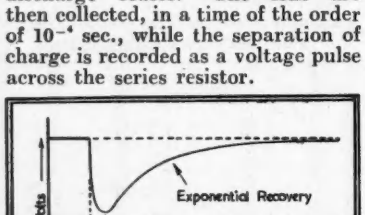

Fig. 9. Form of Geiger counter output pulse

This pulse is of the form shown in Fig. 9; a sharp fall in potential followed by an exponential rise governed by the capacitance of the system and the series resistance.

As the positive ions closely approach the cathode surface, the work function of the latter is overcome by the intense field, and electrons are emitted.[8] These neutralise the ions, but, since the ionisation potential of the simple gas atom normally exceeds the cathode work function, the neutral atom formed possesses the difference energy, i.e., it is excited. On return to the ground state a photon is emitted: this may produce a photoelectron from the gas or the cathode, which in turn may start a fresh discharge if the counter voltage has returned to normal. To prevent this we must use what is described as an external quenching device. The two principle devices used are, first, a multivibrator circuit which reduces the counter potential by several hundred volts after each pulse, and secondly, a very high series resistor ($10^9 - 10^{10}$ ohms) so that the output pulse itself provides the required drop in potential. In any case, the potential must be kept down until all the ions are completely collected and the counter is again stable.

This means that the non-self-quenched counter is unsuitable for high counting speeds, and cannot distinguish between the closely spaced arrival of particles even if these are only infrequent events, or, in other words, it has poor resolution.

An improvement in this respect results from the use of the self-quenched counter, whose action will be described next.

The Self-quenched Counter

This second type of Geiger Counter is obtained by adding to the simple gas used in the first type above about 10 per cent of a poly-atomic vapour, nearly always organic, for example ethyl alcohol. The molecules of such a vapour exhibit, in addition to the electronic excitation levels already described, a series of other energy levels due to quantised increases in the energy of vibration and rotation of the molecules. With each electronic energy level is associated a series of vibrational levels, and with each of the latter is associated a series of rotational levels. This property causes a modification of the counter action. First, during the avalanche few photoelectrons are formed as in the non-self-quenched type, since photons emitted from the simple gas (often called the vehicular gas) are readily absorbed by the complex

molecules, which are thereby excited to higher vibrational and rotational levels. The probable time for which a complex molecule remains excited is large compared with the probable time which elapses before it dissociates into fragments, dissipating in kinetic energy the energy of excitation, so that few photons arrive at the cathode. These will be negligible if the photoelectric efficiency of the cathode is low, which is desirable. The discharge is formed near the anode as before, and shows little tendency to spread radially, since few photoelectrons are formed outside the positive ion sheath; instead, it spreads laterally until stopped by field discontinuities, usually at the counter ends. The field is reduced as before by the ion sheath, and the discharge stops. As the sheath moves out toward the cathode, there is a transfer of charge from the simple gas ions to the complex molecules, as the result of collisions, since the latter have the lower ionisation potentials (See Table 1). This low ionisation potential is one of the criteria for the quenching gas. By the time the cathode is reached, practically all the charge resides on complex ions only. Once more electrons are drawn out of the wall and neutralise the complex ions to form excited neutral atoms. As indicated above, these in general dissociate before they are de-excited, so that there is no photon emission and no photoelectrons are formed. Consequently, there are no spurious avalanches, and the voltage may be reapplied to the counter as soon as the discharge is over. From the instant of breakdown to the time when the ion sheath is far enough away from the anode for the field near the wire to have reached operating condition again there elapses about 10^{-4} sec., during which time a particle entering cannot initiate a count. This interval is the " dead-time " for the counter, and is not a reliably fixed quantity, so that the usual procedure again is to use some external circuit to shut down the counter for a slightly longer, but accurately known, time, thus fixing one important experimental condition.

After the dead-time another 10^{-4} sec. (approx.) elapses before all the ions are collected. During this period an entering particle gives a smaller pulse than normal. The sorting out of such pulses is done when desired by the use of amplitude discriminators in the counting device (scaler) which usually follows the Geiger counter.

In actual practice the quenching obtained by the use of the complex gas is not perfect, and spurious counts are of the order of a few per cent.[9]

Effect of Negative Ions

If the counter contains a gas which readily forms negative ions (eg., oxygen), these will be accelerated toward the anode. However, their mobilities are of the same order as those of the positive ions, so that they are likely to arrive near the anode wire after the main count has taken place and after the dead-time has elapsed. In the high field region they may then acquire enough energy to start a new avalanche, or may deionise, an electron thus liberated then provoking a fresh discharge, which will be registered as a spurious count. Any gas with a high electron affinity should therefore be excluded from these counters. This applies to air, on account of its oxygen content.

Voltage Characteristics of Geiger Counters

If a Geiger counter is subjected to a constant irradiation while the voltage across it is slowly raised, this voltage being plotted against the number of counts recorded in unit time, one obtains a curve of the type shown in Fig. 10. It will be

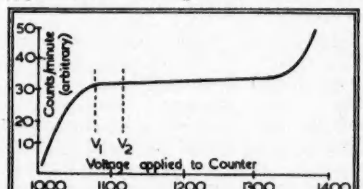

Fig. 10. Voltage characteristic of a Geiger counter

seen that over a wide range of voltage above V_1, the starting potential, there is a " plateau " where the number of counts is almost constant. The reason for the existence of the plateau, expressed in general terms, is that, over this range of applied voltage, every pulse depresses the counter field below threshold, so ensuring cessation of discharge and correct counting. The length of the plateau is thus a function of pulse size, and gases with high specific ionisations such as Hydrogen and Argon will give longer plateaux than gases of low specific ionisation under the same conditions. The specific ionisation of a gas is the number of ion-pairs produced per cm. length of track by the particle in question in traversing the gas at 1 atmosphere pressure. Hence, for a particle traversing x cms. of gas at pressure p, the specific ionisation of the gas being i, the total number of ion-pairs produced will be xip. It follows that increasing the gas pressure will also lengthen the plateau, but this unfortunately raises the starting potential, the latter being proportional, to a first approximation, to p.

By a suitable choice of quenching gas the plateau may be made flat as well as of reasonable length, and a frequent choice for the gas mixture is ethyl alcohol (about 10 per cent) and Argon at 10 cm. pressure or thereabouts.

Output and Life of Geiger Counter

The existence of a plateau region means that the counter can be operated with an output pulse height independent of the initial ionisation, and also that the pulse height will not vary with small changes in applied voltage, so that supply stabilisation is not impossibly critical. A supply constant to ± 1 per cent is sufficient for most purposes. The output pulse will usually lie in the region of 1-100V, and is made large by increasing the applied voltage as far as the plateau allows, and by reducing the capacitance of the counter, plus any associated circuits.

It is not usual to employ the first alternative, however, since the life of a counter is a function of the applied voltage. The reason is that in every discharge a number of complex quenching molecules are dissociated and this number rises with applied voltage. In many cases the complex molecules are chosen so that the fragments are themselves effective as quenching agents, but eventually the counter becomes useless as these in turn are broken down.[10,11] The number of counts to be expected before this happens is of the order of 10^8-10^9, according to the nature and amount of the quenching gas. The usual operating point is round about V_2 in Fig. 10.

Thanks are due to Messrs. E. K. Cole Ltd. (Electronics Division) for permission to publish this article.

Appendix

We require to find the total energy (kinetic plus potential) of

the electron in the Hydrogen atom, assuming circular orbits and quantised angular momentum.

Symbols Used

- c Velocity of light.
- e Electronic charge.
- m Mass of electron.
- h Planck's constant.
- λ Wavelength of emitted photon.
- ν Frequency of emitted photon.
- n Positive integer—the principal quantum number.
- r Radius of orbit.
- ω Angular velocity of electron.
- Z Atomic number.

For each quantised energy state we have:—

$$m\omega r^2 = \frac{nh}{2\pi} \quad \ldots\ldots\ldots\ldots \quad (1)$$

The kinetic energy of the electron is:—

$$E_k = 1/2\ m\omega^2 r^2 \quad \ldots\ldots\ldots\ldots \quad (2)$$

Equating the electrostatic force of attraction, given by Coulomb's Law, and the centrifugal force:—

$$\frac{Ze^2}{r^2} = m\omega^2 r \quad \ldots\ldots\ldots\ldots \quad (3)$$

Combining (1), (2) and (3), eliminating ω and r:—

$$E_k = \frac{2\pi^2 Z^2 e^4 m}{n^2 h^2}$$

TABLE I

	Ionisation Potential (volts)	First Excitation Potential (volts)
Acetone	10.1	—
Ammonia ...	10.5	—
Argon	15.7	11.6
Carbon Dioxide	14.4	—
Ethyl Alcohol ...	11.3	—
Helium	24.5	20.5
Hydrogen (Atomic) ...	13.5	10.2
Hydrogen (Gas)	15.4	11.5
Methane	14.4	—
Neon	21.5	16.6
Nitrogen ...	15.5	6.1
Oxygen	12.5	6.0

Some typical ionisation and excitation potentials.

The figures are taken from S. C. Brown: "Nucleonics" 2, No. 6, 10 June, 1948.

The potential energy of the electron is given by:—

$$E_p = \frac{-Ze^2}{r}$$
$$= -m\omega^2 r^2 \text{ [from (3)]}$$
$$= -2E_k$$

Therefore the total energy E $(= E_p + E_k) = -E_k$

$$= -\frac{2\pi^2 Z^2 e^4 m}{n^2 h^2} \quad \ldots\ldots\ldots\ldots \quad (4)$$

For a transition from an orbit in which $n = n_2$ to a second in which $n = n_1$, we have for the energy of the emitted photon:—

$$h\nu = \Delta E$$
$$= \frac{2\pi^2 Z^2 e^4 m}{h^2}\left\{\frac{1}{n_1^2} - \frac{1}{n_2^2}\right\}$$

$$\text{or } 1/\lambda = \nu/c = \frac{2\pi^2 Z^2 e^4 m}{h^3 c}\left\{\frac{1}{n_1^2} - \frac{1}{n_2^2}\right\}$$

Evaluating (4) for the ground state of the hydrogen atom leads to a value of 13.6 eV. for the total energy. Thus the ionisation potential is 13.6 volts, which is in good agreement with the experimental value of 13.5 volts.

References

1 W. Hume-Rothery: "Atomic Theory for Students of Metallurgy," Institute of Metals (1946).
2 A. M. Tyndall: "Mobility of Positive Ions in Gases," Oxford University Press (1938).
3 R. G. Fluharty: *Nucleonics* 2, No. 5, 28, May, 1948.
4 R. G. Fluharty: *Nucleonics* 3, No. 1, 46, July, 1948.
5 C. G. and D. D. Montgomery: *Jour. F. Inst.*, 231, 447, 1941.
6 K. Z. Morgan: *Proc. I.R.E.*, 37, 74, Jan., 1949.
7 J. A. Victoreen: *Proc. I.R.E.*, 37, 189, Feb., 1949.
8 N. F. Mott and H. S. W. Massey: "Theory of Atomic Collisions," Oxford University Press (1933).
9 J. L. Putman: *Proc. Phys. Soc.*, 61, 312, Oct., 1948.
10 S. S. Friedland: *Phys. Rev.*, 74, 8, 898, Oct. 15, 1948.
11 E. C. Farmer and S. C. Brown: *Phys. Rev.*, 74, 8, 902, Oct. 15, 1948.
For a more detailed bibliography of Geiger Counters *see* M. Healea: *Nucleonics* 1, No. 4, 68, 1947.

H.T. SUPPLY FOR TELEVISION RECEIVERS

By C. H. BANTHORPE *

IN many television receivers, the H.T. supply must provide approximately 230 volts for vision and sound valves, and up to 330 volts for time bases and anode 1 of the C.R.T., if a tetrode.

These voltages can be produced in a number of ways, but one used by the writer is economical, kind to components, and has no H.T. mains transformer, and can thus be used in compact equipment without magnetic fields, which might be a source of trouble.

To get the higher voltages without a step-up transformer requires some form of voltage doubler, and the type chosen has several advantages and one disadvantage. Firstly, the lower voltage, at high current, can be obtained without wasteful voltage dropping in resistors, which dissipate many watts of heat; always a nuisance in compact equipment. The second advantage is that the voltage across any electrolytic can never exceed the peak voltage of the mains, approximately 325 volts, instead of the 500 volts or so from a 350 volt supply, and this allows higher value capacitors to be used for a given price, or cheaper capacitors for a given capacitance. The third advantage is that the D.C. through the choke is that of the 230 volt line only, and therefore for a given price, more inductance can be obtained, or for a given inductance, a cheaper component can be made.

A disadvantage of a transformerless set is that the mains are connected to the receiver chassis and safety precautions must be taken to prevent shocks. In this supply neither side is directly joined to the mains, but the same precautions must be taken. The circuit shows one such circuit used successfully in production. The capacitors are contained in two cans and are made by B.E.C. One is a 50-50-100 μF 275 V wkg., C.E.15620, and the other is a 24 μF 275 V wkg., C.E.15621. As the 330 V line feeds anodes only, the current through the focus coil is partially stabilised and variations due to temperature changes of the coil are not troublesome.

* Central Equipment, Ltd.

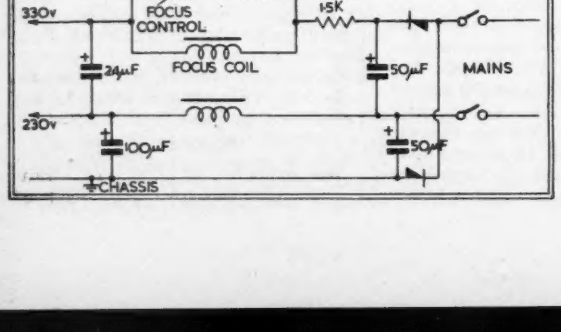

This voltage-doubler circuit gives transformerless H.T. for sound and vision receivers and time bases

Television in Birmingham

(Many readers of *Electronic Engineering* will be aware of the recent demonstration of Television Signals in Birmingham on Nov. 3, 1949, by means of the Radio Relay Link between Museum Telephone Exchange, London and Telephone House, Birmingham.

The following is a brief description, with illustrations, of the Relay Link based on information supplied by the General Electric Co. Ltd., who designed, manufactured and installed the system to Post Office specifications.)

THE London-Birmingham Radio Television Link marks a great advance in television transmission technique, and places Britain right in the fore-front of television development. Indeed, it can now be fairly claimed that nowhere else in the world does there exist a television relay system so technically advanced for continuous public service. The many new inventions embodied in the Link and the invaluable information gained during its construction will be of the greatest value in designing radio links for other telecommunication projects, such as multi-channel telephone, teleprinter and picture telegraph systems. Even greater possibilities can be envisaged in their use in establishing communications over desert country, river crossings and even in jungle country, where the nature of the terrain renders virtually impossible the use of more normal modes of communication.

The Link is suitable for the transmission of 405 line, 50 frames/second, television signals of the waveform transmitted at present by the B.B.C. from Alexandra Palace and to be transmitted from Sutton Coldfield. The contract issued by the Post Office in May, 1947, was for the interconnexion of London and Birmingham, but required that the system should be so designed that it could be extended up to 400 miles.

When completed, the radio-television Link will provide for simultaneous two-way transmission of television signals between the two cities. At the present stage a reversible link is installed, so that transmission in either direction can be obtained as desired. This reversible service has been provided with just over 60 per cent of the complete radio equipment and without the erection of the final special repeater-station towers. The aerials are erected on temporary masts and the equipment is installed in the buildings at the foot of the masts. For the two-way link the radio equipment will be installed in special cabins at the tops of the repeater station towers. The present reversible system uses two frequencies of transmission: 870 and 890 Mc/s. A station which receives on 870 Mc/s. transmits on 890 Mc/s. and vice versa. These two frequencies are used for either direction of transmission with the reversible link and will eventually be used for one direction of the two-way link, 917 and 937 Mc/s. being used in similar fashion for the other direction.

The use of these frequencies necessitates optical paths between transmitters and receivers for satisfactory and consistent performance. It has therefore been necessary to use repeater stations at Harrow, Dunstable, Blackdown and Rowley Regis.

The television signal is transmitted over the television link by frequency-modulation of the 900 Mc/s. carrier; this being achieved at a terminal station in two steps. The vision-frequency signal is used to frequency-modulate an oscillator between 32.5 and 35.5 Mc/s. and the modulated oscillation is amplified and applied, together with the output of a 900 Mc/s. generating chain, to the final stage of the transmitter. In this stage, frequencies are produced which differ from that of the R.F. generating chain by amounts equal to the frequency of the modulated oscillation. Both these signals, the frequency of one of which is above, and the other below, that of the R.F. generating chain, are frequency-modulated by the vision-frequency signal to the same extent as was the original 34 Mc/s. oscillator. One of these frequency-modulated carriers is selected by filters and is the signal transmitted.

At a repeater station, the received signal is heterodyned by a local oscillator to give a difference frequency of 34 Mc/s. This I.F. signal is amplified, and the transmission process is repeated. The transmitted signal is not demodulated to vision-frequency until the receiving terminal is reached. By the use of this system the difficulties of amplifier design and operation at low vision frequencies are avoided.

The transmitting frequency at a repeater station cannot be the same as the receiving frequency, since the receiver would then receive power from the local transmitter as well as from the previous station. For this reason the frequency of the receiver local oscillator cannot be the same as that of the transmitter master-oscillator. Therefore, at a repeater station the local oscillator frequency is derived from part of the transmitter master-oscillator output by heterodyning it with the output of a crystal controlled oscillator whose frequency is equal to the difference between the received and transmitted frequencies. By arranging that the local and master oscillator frequencies are each above, or each below, the received and transmitted frequencies respectively the transmitted frequency is made independent of the drift of the station master oscillator and is affected only by the small drift of the crystal controlled oscillator. Since only two frequencies are used for one channel the shift frequency is the same at all repeater stations, and is alternately added to or subtracted from the station master oscillator frequency.

The power transmitted from each station is of the order of 10 watts, and the received power for free space propagation over a 40-mile path is just over a microwatt. Thus the gain of a repeater station is 70 db.

The vision-frequency signal is fed into the terminal modulator from Post Office equipment via a coaxial cable. The output of the terminal

London—Birmingham

Terminal and Repeater

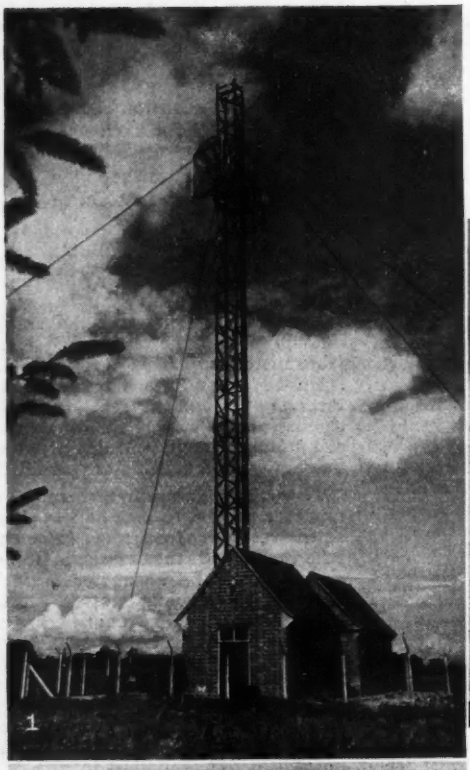

Fig. 1.—Exterior view of Dunstable repeater station, showing aerial arrays erected on a temporary mast. The buildings at the foot of the tower house the standby generator equipment, the transmitter-receiver power and monitoring equipment.

Fig. 2.—The terminal aerial array at Telephone House, Birmingham. From Telephone House the vision signals are carried by coaxial cable to the B.B.C.'s transmitter at Sutton Coldfield

Fig. 3.—Model of a final repeater station, showing special cabin at the top of the mast to house the transmitter-receiver and equipment in the final simultaneous two-way transmission project.

Fig. 4.—The terminal aerial array at Museum Exchange, London.

Television Link

Station Equipment

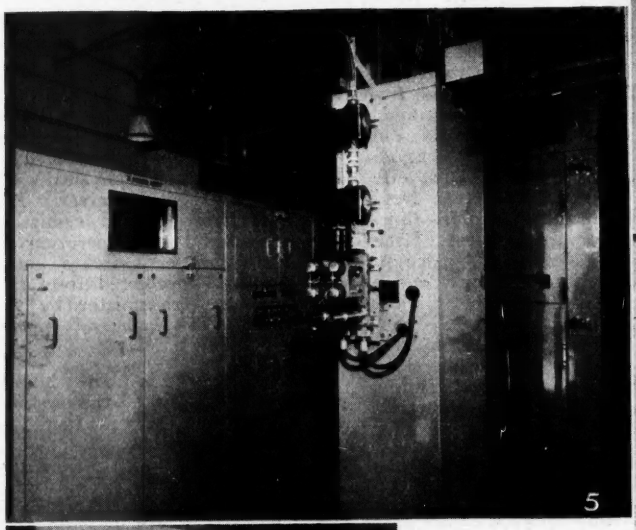

Fig. 5.—Equipment building at Blackdown repeater station, showing contactless R.F. *switch mounted on the side of the receiver with resonant cavity filters above.*

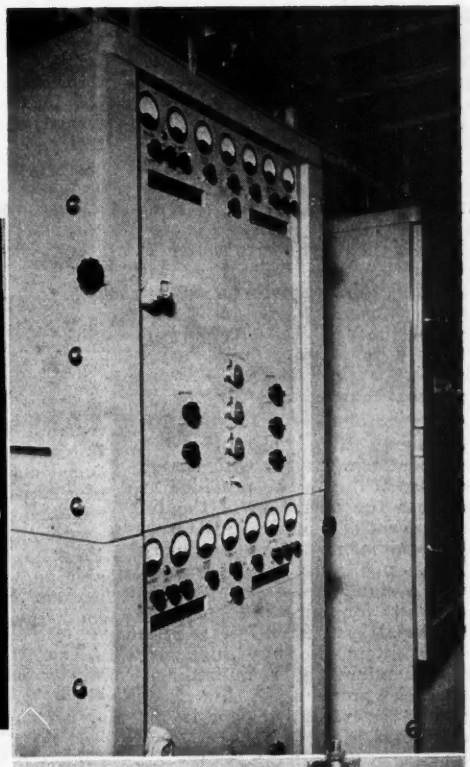

Fig. 6.—Exterior of transmitter cabinets, showing alternative transmitters.

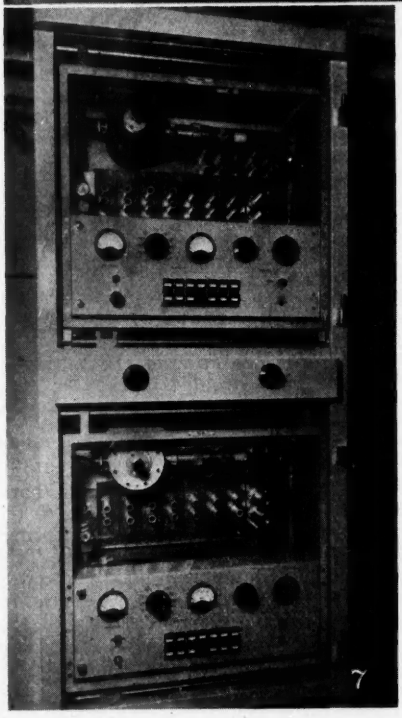

Fig. 7.—Interior view of receivers.

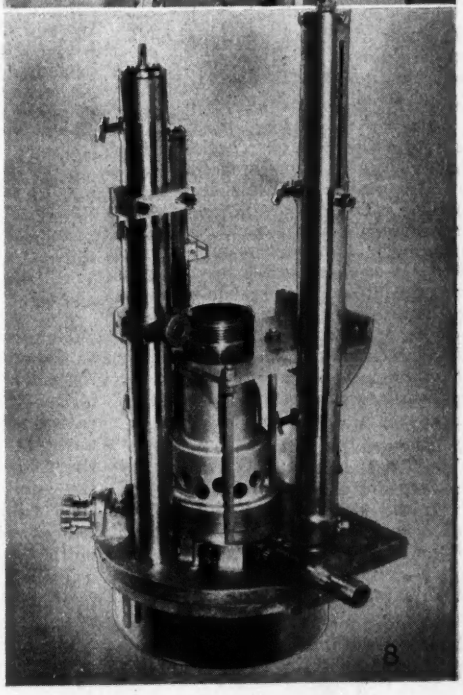

Fig. 8.—Typical R.F. *transmitter amplifier, using an* ACT 25 *valve.*

modulator is a frequency-modulated 34 Mc/s. signal which is applied to the terminal transmitter, and the R.F. output of the transmitter is taken through output filters and an output monitor to the transmitting aerial. This consists of a paraboloid reflector formed from light-alloy tubes and energised by a coaxial-line fed dipole and parasitic reflector. The full diameter of the paraboloid is 14 ft., but its horizontal aperture has been cut to 10 ft. with very little loss of gain (since horizontal polarisation is used). The gain of the aerial is 27.5 db. with reference to that of a half-wave dipole. Coaxial cables are used throughout as feeders for the 900 Mc/s. energy.

Duplicate signal channel equipment and power units with changeover switching are provided to maintain the operation of the link in the event of a failure in the working equipment. The equipment which is not in use is kept warmed-up in a standby condition, so that it is ready for immediate operation. The aerial system and transmitter output filters are not duplicated, and therefore a radio-frequency switch is provided in the feeder between the transmitter and its output filters.

Changeover switching between the power units and the signal channel equipment is so arranged that each channel equipment can be connected to either power unit.

At repeater stations, the R.F. input from the receiving aerial is fed through the receiver input filter and an R.F. switch to the selected receiver. The transmitter feeder arrangement is the same as at a terminal transmitting station. Duplicate equipment is provided as at a terminal station, the receiver and transmitter being considered for switching as one unit. At a terminal receiving station, the feeder arrangement is the same as for the receiver at a repeater station.

Control and monitoring equipment is provided at each station by which all the normal operations for that station can be carried out. All the radio stations and the control points are linked by a control telephone which has selective ringing but a common speech channel for all the stations.

In addition to the main signal channel equipment, comprehensive test equipment is being supplied for the assessment of the overall vision-frequency response of the complete system from terminal to terminal. In addition, a monitor for the transmitted picture and waveform is being supplied for each control point, each radio terminal and each repeater station. Special radio-frequency testing equipment is also being provided for each radio station.

The system makes use of a range of advanced techniques in valve and circuit design, and the radio frequency equipment is based upon disk-seal triodes type DET 24 and ACT 25 which are used in coaxial-line circuit equipment. Such circuits are markedly different from circuits performing similar functions at lower frequencies. Each tuned circuit is essentially a length of coaxial transmission line, and a particular feature of the circuits used in the Television Link is that they have been designed for reliable and stable operation over long periods by elimination of sliding contacts and by robust construction.

The transmitter consists of a master oscillator (DET 24) stage, a first R.F. amplifier (DET 24) stage, a second R.F. *amplifier* (ACT 25) stage and a modulated (ACT 25) or frequency-changer stage. In addition, there is a (DET 24) frequency-shifter stage for the derivation of local-oscillator power, together with its associated 20 Mc/s. crystal-controlled shift-frequency generator. The transmitter is designed for normal operation at full output with a drive of 4 volts peak-to-peak of intermediate-frequency signal. This I.F. signal is amplified to a level sufficient fully to modulate the end stage of the transmitter in a wide-band amplifier using A1820 and KT67 valves.

The receiver uses a silicon crystal as frequency-changer, local oscillator power being fed from the transmitter via a filter consisting of two cavity resonators, which removes unwanted components generated in the frequency-shifter. The receiver I.F. amplifier consists of two stages each using a pair of E1714 low-noise triodes, followed by three automatic gain-controlled stages each using a pair of Z77 pentodes, and a further two stages each using a pair of Z77 valves, the output stage being a cathode-follower consisting of a pair of Osram valves.

The radio-frequency filters used in the system are of two main types, i.e., band-pass filters comprising pairs of coupled resonant cavities, and special band elimination filters, which are based on the properties of multiple resonant lengths of transmission lines. Similar resonant line principles are made use of in the contactless R.F. switch, which is used for switching over to standby receivers and transmitters.

For the reversible link which is now being operated, only two aerials are provided at each repeater station, and since the transmitter and receiver are both connected to each aerial, there is a physical path from transmitter to receiver. The change of direction of transmission is produced by the operation of further contactless-switches, and the receiver is protected from signals from the transmitter by the combination of line and cavity filters.

In conclusion, it is worthwhile to record the history of the system. The Post Office specification was issued in November, 1946, and extensive field-trials to prove the practicability of the system were carried out by a small research team from the G.E.C. Research Laboratories during December, 1946, and January, 1947, at the depth of the most severe winter for many years. The building up of the team at the Wembley Research Laboratories began immediately, and the design of the system was commenced. Just over a year later, in June, 1948, a successful demonstration was given of transmission of 405-line television signals, using apparatus typical of that which had been developed. This followed upon the conclusion of extensive field-testing of the route which had been finally chosen. The next year was devoted to the elimination of teething troubles and to the engineering of the equipment. The first transmission of television signals took place on August 31, 1949, from a temporary terminal station at the Wembley Research Laboratories, through Harrow Weald, Dunstable, Blackdown and Turners Hill Repeater Stations to the Telephone House Terminal Station at Birmingham. This transmission included pictures broadcast by the B.B.C. from Alexandra Palace and received at Wembley for relaying through the Link.

The Hammond Spinet

A New Electrical Musical Instrument

By ALAN DOUGLAS

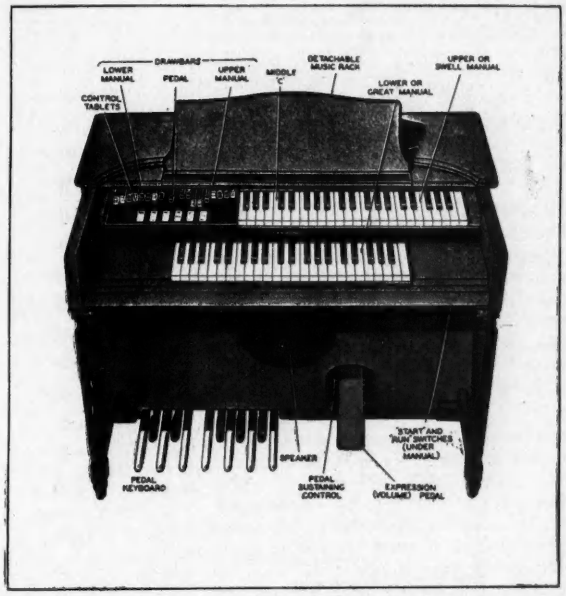

THE Hammond organ and its electro-mechanical tone generating system is well known in this country. Since the end of the war, a number of improvements have been made to this instrument, but so far the exchange position has prevented their importation. Recently the Hammond Instrument Company has introduced a simplified organesque type of instrument for use in the home. There are many ingenious features in the design.

The appearance of the console is shown above. It will be seen that there are two manuals, each of $3\frac{1}{2}$ octaves compass, which overlap. There is also a series of 12 pedal keys, permanently attached to the instrument. One set of harmonic drawbars controlling eight harmonics provides a variable tonal set-up for the lower manual, while one set of nine drawbars supplies the upper manual. In this organ, harmonics up to the 12th are controlled by the drawbars. A single drawbar regulates the volume of the pedals, which are of 16 ft. pitch only. Fig. 1 shows the controls.

One of the major criticisms of previous Hammond instruments was the abrupt attack and decay of the sound. This feature is still evident on the manuals, though it can be prevented by correct fingering. The pedal department in this instrument has, however, a number of controls by which the rate of attack and decay can be varied.

In previous instruments, the vibrato or tremulant effect was produced by a rotating interrupter, which varied the volume but not the pitch. This is not comparable with the effect from a pipe organ, in which both the frequency and volume are modulated.

In the Spinet model, there is a phase shift network which alters the frequency in a continuous fashion. By means of an ingenious circuit fixed phase differences may also be produced for various applied frequencies; so that an added subtlety of tone can be obtained by proper manipulation. This device replaces the chorus generator on all models.

The amplifying and loudspeaking equipment is contained in the console, so that the entire system is portable and of very small size. The name of the instrument is derived from a type of piano very popular in the U.S.A., known as a spinet; it is intermediate in size between a minipiano and a small upright piano.

The generating system of this organ employs 86 rotating iron wheels, as against 91 in the standard organs. Of these, the lowest 12 are used for the pedals only, and have a special contour which generates a pre-formed wave. There is no harmonic mixing from these wheels.

The manual generators run from 18 to 91; thus 13 to 17 are omitted. This range covers from F = 87.307 c/s to B = 5919.9 c/s, there being, in effect, an extended F octave in the bass of the lower manual and an extended C octave in the treble of the upper manual.

Most of the generators have a tuned filter across their outputs, this now being a series resonant transformer in place of the centre-tapped choke previously used. The manual generators have the familiar contour designed to produce a sinuisoidal wave as nearly as possible.

Each manual playing key closes the usual set of eight or nine contacts, thus introducing the full series of generators to the mixing controls, but the pedal department is interesting. Only one pedal key at a time may be depressed. Fig. 2 shows the pedal amplifier. When a key is operated, a contact selects the correct generator and couples it to the grid of *V*7. This valve is, however, biased to cut-off Later in the movement of the pedal, a "pedal keying contact" (common to all pedals) closes. This discharges *C*50 and allows the note to sound.

If the pedal attack control is at "normal," a single resistor discharges *C*50; this allows a rapid attack. If the control is at "slow," an additional resistor *R*45 is introduced, so that the delay in speaking is increased.

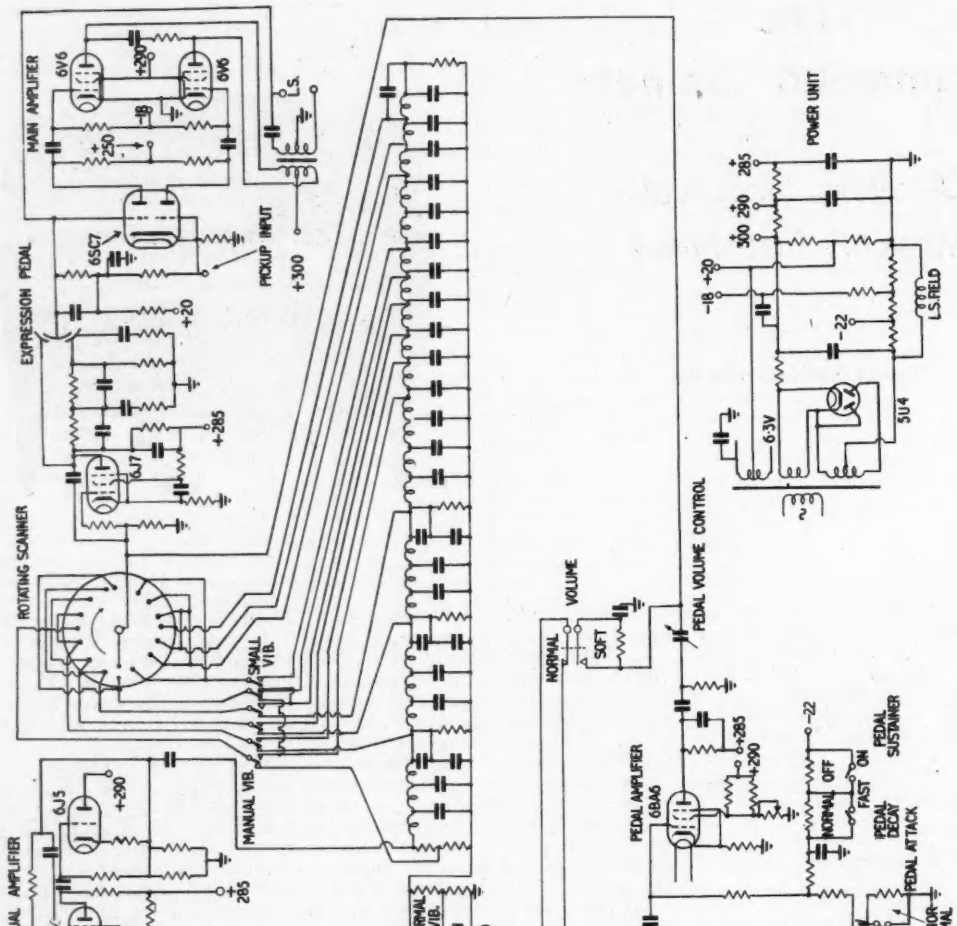

Fig. 3. Simplified circuit of the complete instrument

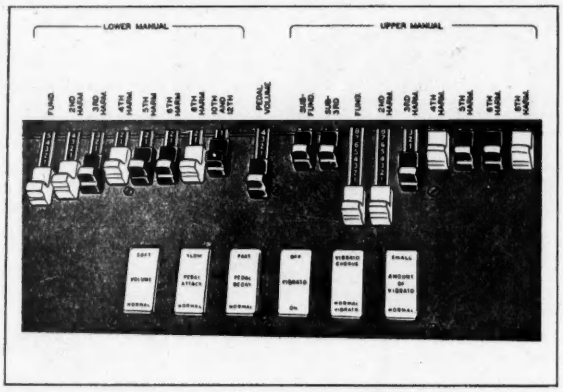

Fig. 1. Drawbars and control tablets

Now when a pedal key is released, the keying contact opens, and this allows cut-off bias to be applied to *V7*. With the "decay" control at "fast," *R52* charges *C50* in a short time. When set at "normal," additional resistance still further increases the charging time. There is a sustaining control on the expression pedal, and if this is used, still further resistance is introduced, so that the note sounds for quite a long time.

To prevent a pedal note from sounding when the organ is first switched on, a resistor in series with the heater of *V7* delays the warming-up period until bias has been applied to this valve.

The foregoing amplifier is, of course, a pre-amplifier before the main section. The volume of the pedal amplifier is adjusted (by the drawbar) by altering the capacitance of a small variable capacitor. It will be recalled that this method is used to control the volume of the "Novachord," also a Hammond product.

To turn now to the other novel feature. The comparatively limited tonal resources of the instrument at any one time suggest that an effective vibrato would enhance its appeal. The Hammond vibrato is a frequency shifting device consisting of a number of low-pass filter sections in series, with a capacitance scanner which is applied continuously up and down the line by means of a rotating capacitor.

Waves fed into the line are retarded in phase in each section of the line, the amount per section being proportional to frequency. As the scanner travels along the line, it alternatively raises and lowers the output frequency, the average remaining equal to the input frequency. There are 16 sets of stationary plates on the scanner and one rotating set, which meshes with each stationary set once in each revolution.

The depth of the vibrato can be controlled by causing only parts of the line network to be scanned; the smaller the number of sections connected, the smaller the degree of vibrato. An ingenious arrangement allows part of the generator signals to be passed through the line delay, and part directly to the amplifier; this gives a certain degree of richness to the sound, producing a chorus effect.

The vibrato is turned off by placing a very high resistance in series with the line. Practically all the signal appears across this resistor and the vibrato effect is eliminated.

A simplified circuit diagram, in which all the foregoing elements can be seen, is shown in Fig. 3 opposite. It will be noted that the smoothing of the power supply is economically carried out; to assist in reducing hum due to heater emission, the centre tap of the amplifier heater transformer winding is connected to a positive potential.

The author was able to play this instrument on several occasions when in the U.S.A. recently, and found it most interesting and colourful. Although reduced to the bare minimum from a design point of view, it is tonally much superior to the original Hammond organs. It is not suitable for normal organ replacement, as registration is slow owing to the absence of pre-set tone-colours.

Fig. 2. Pedal amplifier using 6BA6 valve for V7 position

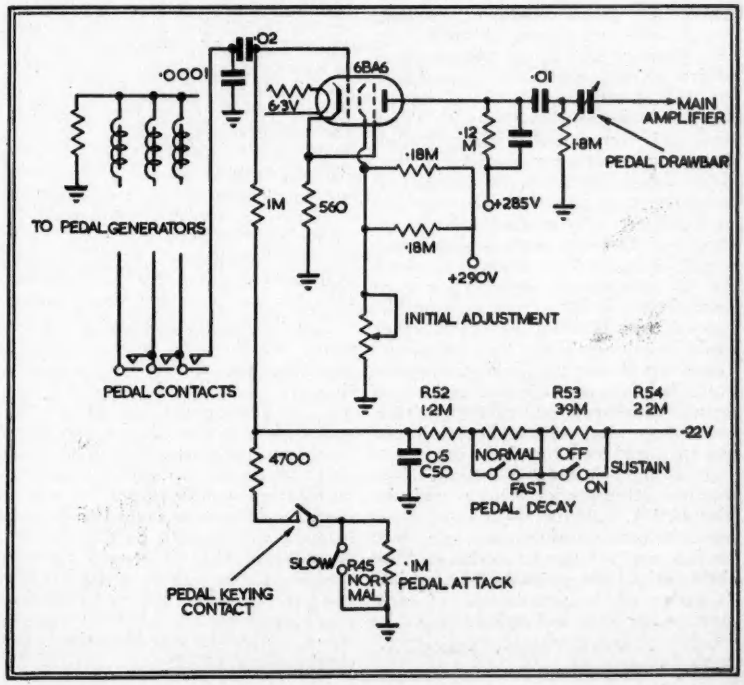

Obstacle Detection Using Ultrasonic Waves in Air

By G. BRADFIELD *

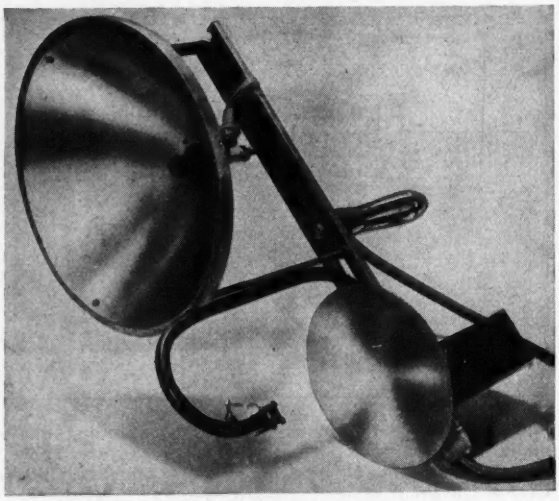

Fig. 1. View of combined transmitting and receiving device

EVERYONE is familiar with the delayed returned sound wave, the echo. Its presence is readily apparent when the travel time of the sound wave between transmission and reception by the ear is about 1/10th second, corresponding to a total distance of 100 ft. or more, but, with practice, aural perception of an echo is possible for much shorter times and distances. Clearly electronic equipment could be devised which would surpass the ear when reception and demonstration of such short time intervals are of interest. These considerations lead to the possibility of an obstacle detector using airborne waves. Warning of the close proximity of obstacles is of first importance to the user of any obstacle detector, but directivity in such a device is also essential. The ear and conveniently sized sound sources are not very good for directivity until the pitch of the sound becomes quite high. The use of audible waves for obstacle detection, however, has two serious disadvantages. Firstly, they may be masked by the common noises of our surroundings and, secondly, audible signals may themselves be obtrusive and disturbing. These two disadvantages are at once eliminated if ultrasonic frequencies are used and these bring, furthermore, the positive advantage that ample directivity is readily achieved by their use.

It is only fair to point out that various attempts have been made in the U.S.A. and in this country to use ultrasonic guiding devices, but so far without much success. Few data have been published on which to judge of the possibilities of such devices for practical applications. It is the purpose of this article to do something to fill this gap.

The equipment used for this investigation was not the most suitable from every point of view; indeed, much of it had been designed for quite a different purpose. Although it is believed that the receiver used (of the piezo-electric type) was fairly sensitive for the 50 Kc/s. region, it is recognised that the ultrasonic source employed, an electric spark, was very inefficient. The disadvantage of inefficiency, itself not serious because the acoustic output was quite powerful, was more than offset with this type of source by the ease of generation, by its wide frequency spectrum and by the smallness of its physical dimensions, a feature very favourable for use with focusing mirrors.

Apart from the industrial applications, which were instrumental in directing the author's attention to these problems, two obstacle detecting applications, Blind Man's Aid and Safety-in-Fog device—to assist road transport—are worthy of study and the results obtained in this investigation would appear to provide useful guidance in regard to both of them; but it cannot be too strongly emphasised that it would be very unwise to speculate optimistically concerning either until a great deal more careful work has been done on them. Now to consider these two applications briefly.

The Blind Man's Aid

In the absence of any "artificial eye" for light, which, with the interpreting system necessary to supplement it, seems much too cumbersome an equipment ever to be carried by a blind man, a "radar" technique (i.e., a range-plus-direction technique) seems most promising. Equipment using electromagnetic waves appears to be out of the question, but ultrasonic waves provide a possible answer, though with limitations, some of which will be discussed in this article.

It must be emphasised that even if ultrasonic waves could reveal all the details concerning his surroundings which a blind man needs, and this is by no means the case, a second development of considerable complexity would be required to interpret the data to him; and, finally, a perhaps impossibly difficult development would be needed to reduce the bulk and weight of the equipment to the necessary degree so as to make it not only portable but, above all, inconspicuous.

Putting aside the foregoing considerations, it is certain that a blind man would wish to have warning concerning the following three types of hazard:—

(a) Wall, glass window, lamp post or another person;
(b) Kerb or up-going steps;

* Telecommunications Research Establishment, Ministry of Supply.

(c) Down-going step or flight of steps.

The experiments described herein deal with all of these, or with simulations of them.

Safety-in-Fog to Aid Road Transport

For vehicles, in place of visible light, it is desired to find waves which will penetrate fog, but although these may be either electro-magnetic or mechanical, waves of the former type demand for their generation and detection equipment far more complex than for the latter. In general, a radar technique, using pulses or trains of waves, seems most promising.

The problems encountered are thought to be—

(a) Detect waves reflected from kerbs and walls at the side of the road.

(b) Detect waves reflected from on-coming traffic.

The experiments recorded here show what has been achieved with simple equipment in this way.

Design Considerations for Ultrasonic Transmitters and Receivers for Use in Air

Alternatives to the spark source used in these tests would be magneto-strictive or, and these are more promising, piezo-electric devices. To produce powerful waves in such a weak medium as air, large amplitudes are necessary but the forces involved will be quite small. The double crystal type of piezo-electric element is therefore most suitable. This operates rather like the bi-metallic strip which curls on heating. Two thin "expander" crystals, chosen for polarity so that one expands when the other contracts, can be cemented together and will bend or curl when polarised. Shear cut crystals can also be used in this way.

When we are proposing to use such devices for ranging, although we need to radiate intense waves, we must not store too much vibrational energy in our transmitter or its slow rate of decay will cause serious embarrassment in our task of measuring very short time intervals. We cannot therefore build up a high amplitude by resonance and we are very much limited in output power by breakdown voltage conditions and saturation piezo-electric effects. We have not therefore used piezo-electric transmitting transducers in these tests. For the reasons given, explosions (an electric spark has the nature of an explosion) and modulated air stream devices are to be preferred as sources of intense sound waves; it is believed that worthwhile advances can be made with the latter, especially where frequency- or amplitude-modulated continuous waves are employed for ranging rather than pulses.

For receivers, breakdown voltage and saturation effects are not present to discourage the use of piezo-electric elements and, on account of their good sensitivity and convenience, these devices were used in the experiments to be described.

Choice of Frequency for Ultrasonic Ranging in Air

It can readily be shown that for sonic transmission in fluids between an *extensive* radiator and an *extensive* receiving element, both of circular aperture D:—

$$\frac{P_r}{P_G} = \frac{D^4}{9\lambda^2 d^4} exp\left(\frac{-2\alpha d}{\lambda^2}\right) \ldots\ (1)$$

where

P_r is the received electrical signal,

P_G is the generated electrical signal power,

λ is the wavelength,

d is the separation of the radiator and the receiver,

α is an attenuation constant for the fluid under consideration; it is independent of frequency for all fluids, except those which exhibit relaxation phenomena. The assumption has been made that the transducers are 100 per cent efficient (mechanical/electrical power) and that perfect matching exists between the propagating medium and the transducers.

Where the above holds there is a minimum attenuation at an optimum wavelength of λ_o which is obtained by differentiation:—

$$\lambda_o = \sqrt{2\alpha d} \quad \ldots\ (2)$$

Taking a pessimistic assumption for air, at ordinary temperature α is .0017 if d is in cm.

From this the optimum wavelength λ_o and frequency for minimum overall attentuation for various distances for the above specified conditions will be as in Table 1:—

Table I

Distance d in feet...	10	20	40	80
Distance d in cm.	305	610	1220	2440
Optimum wavelength λo/ in cms.	1.02	1.44	2.04	2.88
Optimum wavelength λo/ in inches	0.4	0.57	0.8	1.14
Optimum frequency in Kc/s. ...	33	23	16½	11½

The above equation holds for total reflexion from extensive plane surfaces where the total path is d, while for the more interesting case where the returned signals are from small perfectly scattering objects several wavelengths in extent, the optimum wavelength is the same, but the complete expression for the received electrical power on the above assumption is:—

$$\frac{P_r}{P_G} = \text{constant} \times \frac{D^4 A}{\lambda^2 d_1^4} exp — 4\alpha d_1/\lambda \ \ldots\ (3)$$

In this expression d_1 is the separation between the common transmitting/receiving position and the scattering object, and A is the effective echoing area of the latter which, in the case of a sphere, is approximately its projected area. In the case of returns from a cluster of small objects, each of which is distinctly smaller than a wavelength, the expression is similar to (3) with change of constant and an increase of the index of λ in the denominator to 6. The optimum wavelength is then approximately halved.

If we are concerned with a distance of say 20 feet from the observer to the object sought, we shall thus, for large objects, expect to find it best to use a frequency of 23 Kc/s. and for clusters of tiny objects 50 Kc/s. In the tests to be described 52 Kc/s. and 110 Kc/s. were used.

Details of Ultrasonic Equipment Used in the Experiments

The combined transmitting and receiving device is shown in the photograph of Fig. 1 and, in some detail, in the sketches of Fig. 2. The spark transmitter had a standard 14 mm. spark plug fixed in it, with the gap at the focus of the 7½ in. diameter paraboloid. The gap itself was a little over one millimetre so that it was short compared with the wavelength used (3 to 7 mm.).

The microphone incorporated a hollow double bimorph (twister-type) Rochelle salt crystal of dimensions 9.5 × 9.5 × 3 mm.; the crystal was of the sensitive, temperature-dependent cut and it had a resonance around 19 Kc/s. It was clamped onto the end of a swan-neck, the latter being lightly packed with cotton-wool; this also served as a shield for the lead going to the CV138 Head Amplifier (see schematic Fig. 3). The crystal was

located at the focus of a 5 in. diameter paraboloid and, at 50 Kc/s., the main lobe of its polar diagram approximately filled this aperture.

The spark occurred when the charging of the 0.25μF capacitor from the 6 KV supply via a 1.2 megohm resistor raised the voltage to about 4 KV. The discharge provided a synchronising signal over a 20 pF to 10 K. network (shown in Fig. 3).

The received signal was further amplified by an amplifier having a maximum gain of about 100 db. centred on 52 Kc/s. with an overall band-width of 14 Kc/s., the output being fed to the cathode ray tube display. (See Fig. 3). A 110 Kc/s. amplifier with a bandwidth of about 20 Kc/s. was used for the higher frequency tests. In most of these tests the signal was rectified before the final amplifying stage.

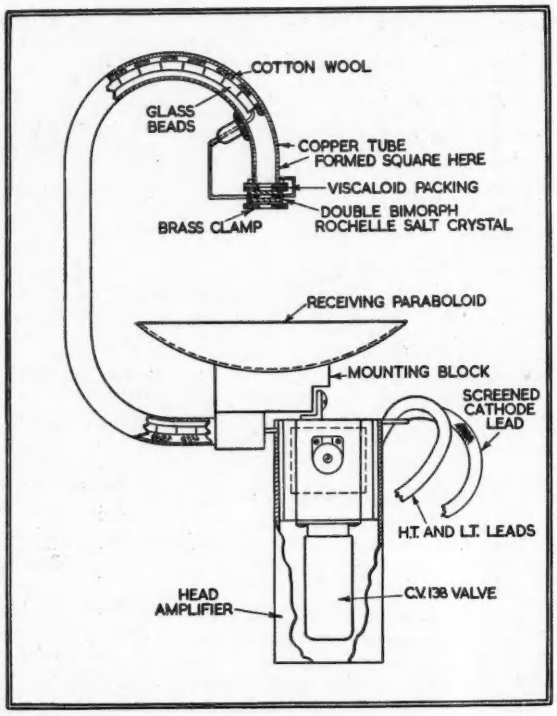

Fig. 2(b) (*right*). Details of receiver and head amplifier

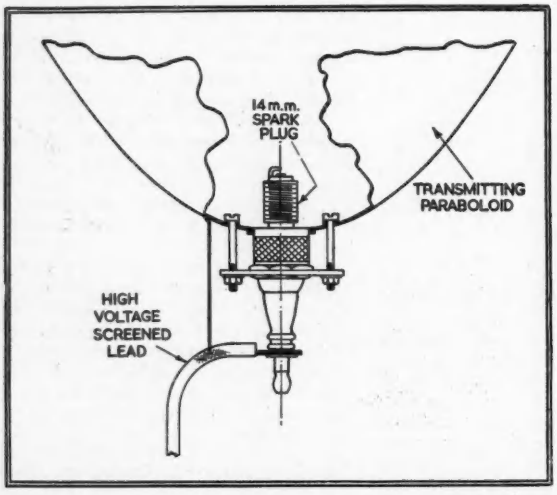

Fig. 2(a) (*left*). Details of transmitter

Frequency Kc/s.	Subject	Approx. RMS Voltage on Crystal (capacitance ≈ 250 pF.)	Approx. db. above thermal agitation level
52	Person at 16 feet and wall at about 20 feet	400 μV 1.2 mV (wall)	48 58
52	1 ft. ball at 16 feet and wall at about 20 feet	386 μV 1.46 mV (wall)	48 59
52	Brick (on laboratory floor) to simulate a kerb at 16 feet	430 μV	49
52	Beam on lip of down-going step	200 μV	42
52	Beam on cinder path at 8 feet	13 μV	18
110	Beam directed down on cinder path at 8 feet	5½ μV	11
52	Automobile head-on at 29 feet	7.2 μV	13
52	Brick (on laboratory floor) at 9 feet	110 μV	37
110	Brick (on laboratory floor) at 9 feet	2.5 mV	64
52	Beam on foot of 3½ in. 3 ft. long steel tube at 9 feet (to simulate lamp post)	140 μV 1.62 mV	39 40
52	Cluster of 36 6BA by ¼ in. screws at 9 feet	29 μV	25
110	Cluster of 36 6BA by ¼ in. screws at 9 feet	14 μV	19
110	Beam on foot of 3½ in. diameter, 3 ft. long steel tube at 9 feet	236 μV	43
52	Teacup at 9 feet on laboratory floor	250 μV	44
110	Teacup at 9 feet on laboratory floor	108 μV	37
52	Beam on foot of 3½ in. diameter, 3 ft. long steel tube at 16ft.	84 μV	35
52	Beam normal on 2 ft. by 15 in. sheet at 8 ft. 4 in.	37 mV	88
110	Beam normal on 2 ft. by 15 in. sheet at 8 ft. 4 in.	790 μV	54
110	1 ft. diameter ball at 16 feet	66 μV	33

Results

Some of the results obtained are summarised in the table opposite, a typical test being shown in Fig. 4. Adjustments to equipment were made in the laboratory, using the ball target to assess the effect of using different types of spark plug and amplifier, to check the alignment of the parabolic reflectors used in the device and the effect of changes in the earthing system in reducing paralysis. At the two frequencies under discussion, 52 and 110 Kc/s., replacement of the spark plug by a spark gap of much more open construction had no marked effect on the signal received. It was found that a great reduction in paralysis could be achieved by completely insulating the earth return of the spark from the earth return of the microphone and by placing a large copper screening can over the back of the spark plug. These are

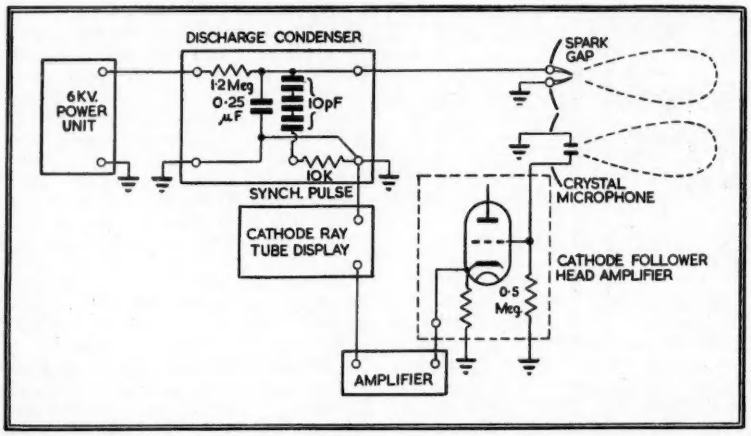

quite important points in the design. It is also best for the whole of the transmitting paraboloid metal parts to be completely insulated from the main frame.

The spark transmitter conditions were measured. The rate was 3 to 4 a second, the mean feed current was 2.7 mA, the D.C. supply 5.4 KV and the spark occurred at about 4 KV with a peak current of about 500 amps. From these results it would appear that the duration of the spark was 1 to 1½ microseconds.

Tests were carried out in the laboratory to supplement those made out of doors. The effect of a lamp-post target located on tarmac was simulated by standing a 3½ in. diameter 3 ft. long tube on the linoleum of the laboratory floor. Good returns were consistently obtained from its foot with a beam sloping downwards at 20° to 30°, but beam elevation was rather critical for nearly horizontal incidence. Bricks were readily seen since they acted as corner reflectors when on the floor, but to give a good echo their edges needed to be substantially normal to the beam. An object such as a teacup on the floor gave a very good echo. To assess the effect of a degree of roughness on the floor, a cluster of three dozen 6 BA × ½ in. screws were used and gave readily visible returns. When testing at 52 Kc/s. for the magnitude of the reflexion from a large sheet, an experiment was carried out which proved that the active area at 8 ft. 4in. was only about 9 in. in diameter, i.e., 5°.

The amplifiers used were calibrated and approximate values of the peak echoes were made by measurement of the photographs of the oscillograms. Wide variations from these often occur because the orientations of the ultrasonic device and of the subject were quite critical.

Fig. 3 *(at top of page).* **Circuit of combined transmitting and receiving device**

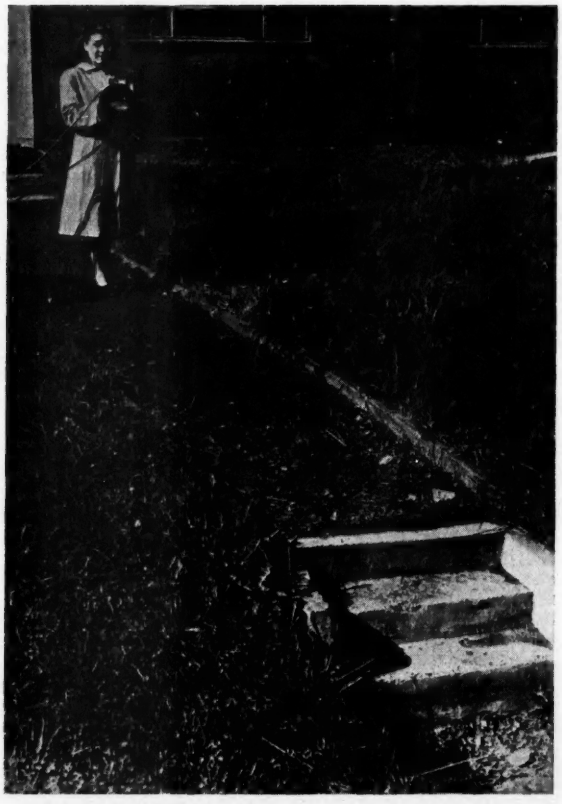

[Fig. 4 *(left).* **Viewing cinder path and steps**

Directivity

The directivity of the combined transmitting and receiving device was very high. Some measurements on the half amplitude widths of a rather similar parabolic reflector with spark plug (transmitter only) are tabulated below:—

Frequency Kc/s	Measured BeamWidth	Theoretical BeamWidth
20	12½°	10°
40	8°	5°
55	12°	3.6°
75	9°	2.7°
110	3½°	1.8°

The 5 in. receiving parabola has a somewhat larger angle and the combined device has, of course, a directivity characteristic corresponding to the product of those of its two elements.

For specular reflexion from an extensive plane, as is the optical case, a given inclination of the plane is effectively doubled and results in very critical conditions. When off normal by more than a few degrees, the echo returned from a smooth plane surface is very tiny indeed.

Tests were made on reflexions from

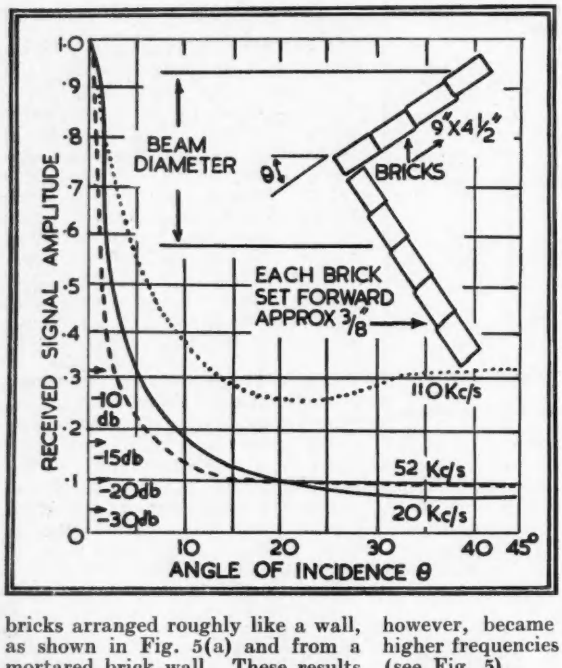

Fig. 5(a) Approximate course of scattered or reflected signal from a rough loose brick corner, as angle of incidence is changed

bricks arranged roughly like a wall, as shown in Fig. 5(a) and from a mortared brick wall. These results are illustrated in Figs. 5(a) and 5(b) respectively. In each case the beam was horizontal. The directivity of the receiver was small, but the half-amplitude beam widths of the transmitter were about $12\frac{1}{2}^{\circ}$, 12° and $3\frac{1}{3}^{\circ}$ for frequencies of 20, 55 and 110 Kc/s., respectively.

Discussion of Results and Conclusions

Analysis of the received energy levels shows that the equipment is working very much more efficiently at 50 Kc/s. than at 110 Kc/s. Allowing for this, the scattering from small objects, such as screws and cinders on the cinder path, was very much greater with the higher frequency. When detecting an obstacle such as a lamp-post, returns appear to be most reliable when the beam is directed at its foot. The only example of a down-going step which was tried gave rise to a discrete reflexion which was quite marked at 10 ft. and, moreover, perhaps because the path preceding the step was slightly rough, a noticeable difference in the signal occurred when the beam was on the path compared with that when the beam proceeded unimpeded in air.

Owing to the high degree of directivity of the device, walls at oblique incidence gave very weak echoes. The scattering from walls, however, became quite marked at higher frequencies such as 110 Kc/s. (see Fig. 5).

Useful returns were obtained from an automobile head-on at about 30 ft. Kerbs, if similar to a row of brick on the ground, give good reflexions provided that the beam is substantially normal to the edge. Similarly a wall gives excellent reflexions for normal incidence.

In general, there is a conflict between achieving high sensitivity of detection of small scattering objects by focusing the beam, (which is attended by good resolution of side-by-side objects), and the worsening of returns obtained from poor scattering surfaces, such as walls and the like which occurs through the enhanced directivity, since the latter inevitably accompanies the improved sensitivity when focused beams are used. For ranges of about 10 ft. it would appear advisable to use quite high frequencies of around 60 Kc/s. to make the best possible use of any roughness, and consequently scattering, which available surfaces offer. For ranges of about 30 ft., a frequency of around 20 Kc/s. seems suitable.

The high directivity of the beam which obtains when a reasonable compromise is struck between increasing equipment power and increasing sensitivity by focusing the beam is a serious drawback of the ultrasonic obstacle detector. This might possibly be overcome at the expense of some complexity in a Safety-in-Fog device by using two transmitting-receiving assemblies, one directed forward and the other sideways and down. Extensive trials would be needed to decide whether reliable indications were obtained from such equipment. For the Blind Man's Aid, however, the diverse nature of the hazards encountered would make most formidable demands on the equipment and it would be a very bold man who would prophesy even ultimate success for such a device in a portable form.

Acknowledgement is made to the Director of the National Physical Laboratory and the Chief Scientist, Ministry of Supply, for permission to publish this paper. (*Crown copyright reserved. Reproduced with the permission of the Controller of H.M. Stationery Office.*)

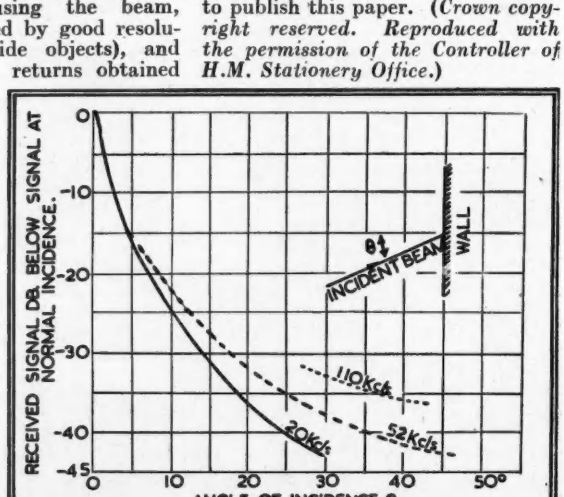

Fig. 5(b). Approximate course of scattered signal from mortared brick wall as angle of incidence is changed

A HIGH IMPEDANCE INPUT STAGE for a Valve Amplifier

By P. O. BISHOP, M.B., B.S. (Sydney)*

BY means of a valve amplifier it is possible to measure small changes in electrical potential having frequency components over a wide range even when they are derived from a source with a very high internal resistance. When the source impedance is very high and it is required to amplify and record a wide range of frequencies the use of a valve amplifier becomes essential. For this purpose a very high input impedance is required which normally calls for the use of special electrometer valves. Several attempts have been made to achieve the same result with common valve types. The methods adopted will be briefly reviewed and the application of these methods to the design of an input stage to a valve amplifier will be discussed.

The most important factors in determining the maximum resistance which may be placed in the grid circuit are the magnitude of the grid current and the nature of the grid current characteristics. By the use of common valve types under reduced operating potentials it is possible to achieve grid currents of 10^{-13} ampere or less. Nielsen[1] reviewed the earlier publications and investigated the possibilities of using the types 38, 954 and 959 as reduced grid current valves. He includes much quantitative information showing the dependence of grid current upon applied potentials and reports grid currents less than 10^{-15} ampere in the 959 valve associated with a stability comparable with that of special electrometer valves. Reducing the filament temperature and anode potential will minimise the grid current from all sources except that due to insulation or surface leakage and the portion that results from the emission of positive ions from the cathode.

* Department of Anatomy, University College, London.

The grid current due to positive ion emission can be substantially reduced by using an "electrometer connected" pentode in which the suppressor electrode (*G*3) acts as the control grid and the screen acts as the space charge grid shielding the control grid from cathode ions. The normal control grid (*G*1) is operated at a small positive potential relative to the cathode. It is not possible to use an "electrometer connected" valve as a true cathode follower because variations of control grid (*G*3) potential have relatively little effect on the total cathode current. The control grid in this case exerts its effect by partitioning the cathode current between the screen grid (*G*2) and the anode. Grid currents as small as those reported by Nielsen cannot be expected when the grid (*G*1) is used as the control grid in a normal cathode follower circuit. With due precautions for minimising surface leakage the lower limit to the value of the grid current in a valve operated as a cathode follower will be set by the positive ion current from the cathode and will be of the order of 10^{-13} ampere.

Despite this limitation, the cathode follower has many advantages that make it desirable as the input stage to an amplifier. The effect of feedback in increasing the grid-cathode resistance and reducing the grid cathode capacitance is well known. A further important property of this circuit was reported by Sowerby[2] in that it allows a much higher resistance to be placed in the grid circuit without causing instability than would be the case if the valve were operated in a normal amplifying stage. The explanation of this observation has been given by Crawford[3]. The maximum value of grid leak with which stability can be maintained is given by the expression $1/gmK$, where K is the maximum slope of the grid current/anode current curve and gm the transconductance at that point. With a cathode follower the effective transconductance becomes

$$gm(eff) = gm \frac{1}{1 + gmRc}$$

where Rc is the cathode load resistor. Thus, the maximum value of the grid leak (Rg) becomes

$$Rg(max) = \frac{1}{\frac{gm + Rc}{K}}$$

The use of a high cathode load resistor makes the variations of calibration with source impedance very small even when grid leaks up to 10^{12} ohms are used. The magnitude of the grid current is, however, not affected by the fact that the valve is a cathode follower and it will have the same value as that obtained with a normal circuit operating at the same anode voltage and current.

The acorn types RCA 954 (pentode) and 955 (triode) are very suitable for the input stage. They are very small and their electrodes are connected to leads brought out through seals well separated on the envelope. The cathode follower circuit shown in Fig. 1 was designed as the input stage to a balanced direct coupled amplifier.

The operating potentials and characteristics for the 954 and 955

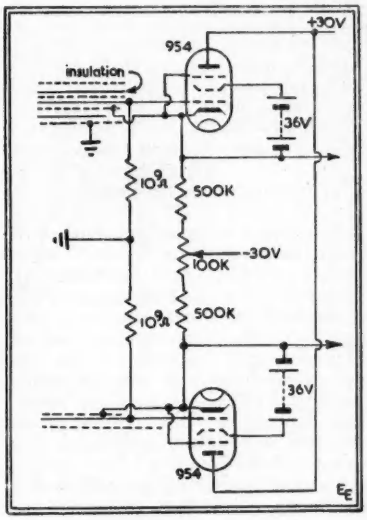

Fig. 1. Cathode follower input stage to a balanced D.C. amplifier

are given in the table below.

	954	955
Heater potential	4V	4V
V_a	30V	36V
Screen grid (g2)	36V	—
V_g	—1.4V	—1.5V
I_a (+I_{g_2} for 954)	50 μA	60 μA
μ	—	25
g_m	170×10^{-6} mhos	130×10^{-6} mhos
R_a	>5 MΩ	$2 \times 10^5 \Omega$
i_g	5×10^{-13} amp	5×10^{-13} amp

The choice of operating potentials is largely determined by the output impedance that can be tolerated. Reducing the operating potentials reduces the grid current but it also decreases the transconductance of the valve and so increases the output impedance of the cathode follower. The increase in anode impedance of the valve also requires a higher value of the cathode load resistor than would otherwise be the case. Thus the operating potentials chosen for the valve will be largely determined by the requirements of the particular application of the cathode follower. The circuit parameters given above gave an output impedance for the stage of about 10 KΩ. This did not limit the frequency response of the following amplifier which was designed to have a uniform amplification up to 10 Kc/s.

It is desirable to make the cathode load resistor as large as possible in order to avoid non-linear distortion with large input signals and in order to make the amplification of the stage approximate to unity. In the case of the triode valve with small input signals it is sometimes convenient to earth the cathode load resistor, 25K being a suitable value to give a grid bias of -1.5 V when using the operating potentials given above. In the case of the pentode the high anode impedance makes a high value of cathode load resistor essential and this requires a negative high tension supply. When the cathode follower is used as the input stage to a high gain direct coupled amplifier it is desirable to use wire wound resistors. This places a practical limit to the value of the load resistor rather than the available negative high tension supply. The potentiometer in the cathode circuit of Fig. 1 enables the D.C. levels of the two cathodes to be balanced. The actual value of the grid current for a given valve type varies from valve to valve by a factor of about ten. In the case of the triode, 955, the grid current was about 5×10^{-12} amp. while for the pentode it was about 5×10^{-13} amp. When the pentode is used the anode potential should be a few volts negative to the screen potential. Raising the anode voltage above that of the screen causes an increase in grid current.

The input capacitance is considerably reduced by operating the valve as a cathode follower. The capacitance between the grid and earth can be reduced in the same ratio as the reduction of the grid-cathode capacitance by joining the shielding on the grid lead to the cathode[4]. This shielding must be insulated from earth and the whole again covered with an earthed screen. To obtain the minimum input capacitance the valves should be mounted on the pick-up electrodes themselves or in such a way that the input grids are joined directly to the source of the E.M.F. With the 955 the effective input capacitance to the valve will be little more than the grid-plate capacitance (1.4 $\mu\mu$F). When the pentode is used the effective input capacitance is very much less, the calculated value being about 0.05 $\mu\mu$F. This is achieved by using small floating batteries to provide the screen potentials, so that the grid-screen capacitance is also reduced by the negative feedback. In practice stray capacitances associated with the pick-up electrode system are likely to be of a much higher order than the actual input capacitances of the valve.

References

[1] Nielsen, *Rev. Sci. Instrum*, *18*, 18, 1947.
[2] Sowerby, *J. Sci. Instrum.* *21*, 42, 1944.
[3] Crawford, *Electronic Engineering*, *20*, 227, 1948
[4] Attree, *Electronic Engineering*, *21*, 100, 1949.

A "Zero-Beat" Indicator for Heterodyne Measuring Systems

By K. GOLDSMITH, M.Sc., A.M.I.E.E.*

CATHODE-RAY tubes are widely used as detectors of frequency balance in heterodyne measuring systems, but the information given by the tubes does not lend itself readily to remote measurement and automatic control purposes. Electronic frequency meters, which are suitable for this purpose, become very insensitive in the range near zero frequency. If, therefore, an electronic frequency meter is to be used in a heterodyne system, some device must be incorporated which permits accurate detection of the zero frequency.

* Research Department, Lever Bros. & Unilever, Ltd., Port Sunlight, Cheshire.

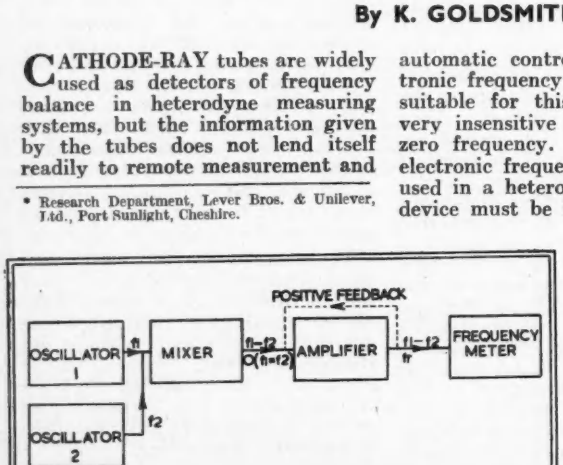

Fig. 1. Block schematic of the Zero-Beat indicator in a heterodyne circuit.

In the conventional heterodyne system, the frequencies of two oscillators, $f1$ and $f2$, are fed into a mixer circuit, the output of which, $f1-f2$, is applied to a frequency measuring circuit. When $f1 = f2$, the mixer output is zero. The introduction of an amplifier between the mixer and the frequency measuring stages does not materially affect the operation of the frequency meter. If, however, the amplifier is provided with a slight amount of positive feedback, it will become oscillatory as soon as the input impedance is sufficiently high. The feedback circuit and the time constant of the amplifier can be so arranged that it will be oscillatory only at very low frequencies, *i.e.*,

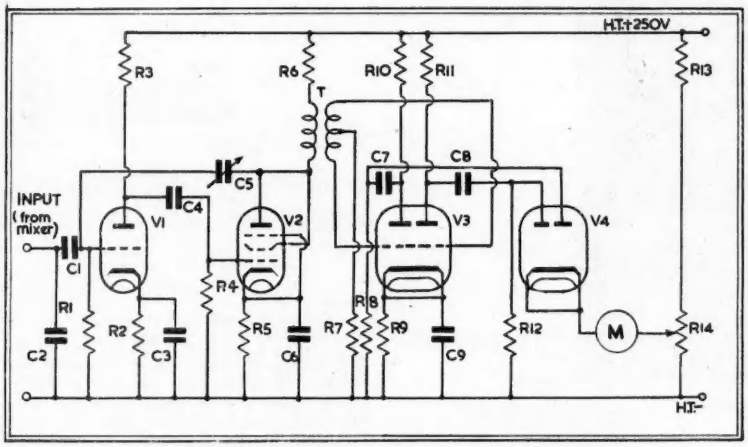

Fig. 2. Schematic of the amplifier and frequency meter

R1, R4, 1MΩ	*R7, R8, R12, 27KΩ*	*C2, C7, C8, .0005μF*	*V2, KTZ 63*
R2, 2.2KΩ	*R9, 4.7KΩ*	*C3, C6, C9. 25μF*	*V3 ECC 35*
R3, 270KΩ	*R10, R11, R13, 100KΩ*	*C4, 0.01μF*	*V4, D 63*
R5, 1KΩ	*R14, 5KΩ*	*C5 Trimmer, 10-25pF*	*M, Milliammeter, 0-1m A*
R6, 10KΩ	*C1, 0.1μF*	*V1 H63*	*T, Intervalve Transformer*

when the mixer output frequency approaches zero. The amplifier then functions like a super-regenerative circuit. At very low frequencies, its self-oscillation is modulated by the output frequency of the mixer, the oscillation building up to a maximum at zero frequency input. The oscillation of the amplifier will virtually cease when the mixer output frequency is increased, and the amplifier will then function normally. The frequency of self-oscillation of the amplifier (*fr*) can be made sufficiently high for the frequency meter to show a large deflexion at "zero-beat," where $f1 = f2$. A block diagram of this arrangement is shown in Fig. 1.

In the device here described, mixer and frequency meter are separated by a two-stage *R-C* coupled amplifier, the output of which is coupled to the input by means of a small trimmer capacitor.

The amplifier frequency (*fr*) is chosen to give full-scale deflexion on the frequency meter at "zero-beat." The positive feedback, and hence the intensity of oscillation, can be adjusted by means of the trimmer. This should be adjusted to give very loose coupling, so that the oscillation can readily be stopped by small changes in the input frequency. Excessive coupling between amplifier output and input by stray capacitances should therefore be avoided. The frequency meter is of the *R-C* type, with an approximately linear response between 100 c/s. and 10 Kc/s. It can thus be used to measure the amount and detect the direction of the frequency deviation from zero. A circuit diagram of the amplifier and frequency meter is given in Fig. 2.

The advantage of using a "zero-beat" indicator in conjunction with an electronic frequency meter is illustrated in Fig. 3. The very flat response of the meter below 100 c/s. would render it useless as a detector in a heterodyne system, but, with the indicator, a sharp peak is obtained at zero frequency. The frequency band width at the base of the cusp of the "zero-beat" indicator is 20 c/s. in this case. This can be adjusted to some extent by means of the back-coupling of the amplifier. At very low frequencies, between 1 c/s. and 10 c/s., the modulation of the amplifier oscillation by the output frequency of the mixer results in pulses of the needle of the output meter *M*. Accurate zero balance can therefore be determined by observing the maximum steady deflexion of the needle, and small out-of-balance frequencies can be found by timing the pulses.

The "zero-beat" indicator has been used successfully in the measurement of dielectric constant by means of the heterodyne method. The indicator was found to be more convenient for visual indication of "zero-beat" over a long period of time than a cathode-ray tube. If an electronic relay is substituted for the output meter, remote indication of zero balance can be obtained, and this can be used for purposes of automatic control.

Fig. 3. Effect of the Zero-Beat indicator on the scale reading of a frequency meter in a heterodyne circuit

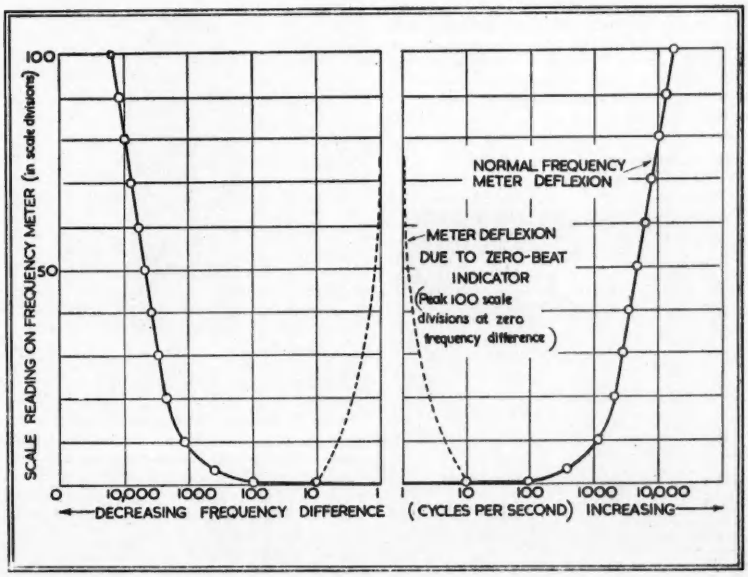

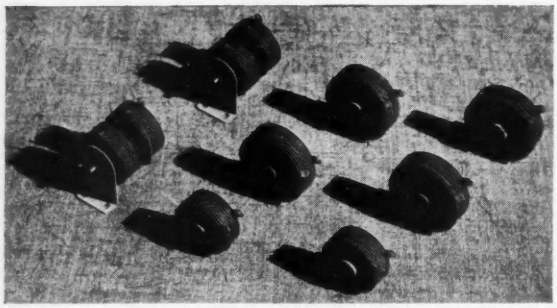

Electronic

A monthly record of British elec-
accessories, compiled from information

SenTerCel Miniature H.T. and H.F. Rectifiers

(Illustrated above)

To meet the need of the radio and electronic industry for miniature H.T. selenium rectifiers a new range of SenTerCel rectifiers has been developed.

The rectifiers are constructed to employ a tubular rivet instead of the conventional spindle, so reducing their size. Together with improved manufacturing technique, claim the makers, this enables the rectifiers to be produced at prices lower than the equivalent thermionic valve.

The range is made up of three basic types of half-wave rectifiers. If an output greater than can be obtained from a single rectifier is required, further rectifiers may be connected in series or parallel. An assembly of two rectifiers mounted on a bracket can be supplied.

The SenTerCel type M1 rectifier measures only ¼ by ¼ by ¼ in., and consists of a single element mounted in an aluminium case, weighing only 0.015 oz. With frequencies below about 5 Mc/s. it can usually replace a thermionic diode. In addition to the saving of space, the use of the M1 rectifier effects a considerable reduction in cost, for not only is the rectifier itself inexpensive, but the cost of a valve base and associated wiring is saved. As no heating is required, a low hum level in high impedance circuits is attained, and the heat loss of a thermionic valve is avoided.

Its average characteristics are:—

Self capacitance ...	20 pF.
Forward resistance at 5 volts D.C.	12,000 ohms.
Reverse resistance at 5 volts D.C.	20 megohms.
Maximum peak inverse voltage	50 volts.
Minimum A.C. input for satisfactory rectification	0.5 volts.

Standard Telephones and Cables Ltd.
Connaught House,
Aldwych,
London, W.C.2.

Ratings of SenTerCel H.T. Rectifiers

Type	RM.1		RM.2		RM.3	
Maximum ambient temperature	35°C.	55°C.	35°C.	55°C.	35°C.	55°C.
Maximum output current (mean)	60mA	30mA	100mA	60mA	120mA	90mA
Maximum input voltage (r.m.s.)	125 volts		125 volts		125 volts	
Maximum peak inverse voltage	350 volts		350 volts		350 volts	
Maximum instantaneous peak current ...	Unlimited		Unlimited		Unlimited	

A Low-Hum Input Pentode for Audio Amplifiers

(Illustrated below)

MULLARD Electronic Products, Ltd., have produced an input valve combining the features of high gain, low microphony and low hum : the EF37A pentode.

The valve is an improved model of the EF37, and should prove useful in the design of audio amplifiers operating from low input levels. Applications include microphone input stages, sound-on-film and disk-recording equipment.

The makers claim that the magnetic hum of the EF37A is less than one-fifth that of the EF37; the actual value, referred to the control grid, being less than 5 microvolts. The operating conditions of the new valve are identical with those of the EF37.

Mullard Electronic Products, Ltd.,
Century House,
Shaftesbury Avenue.
London, W.C.2.

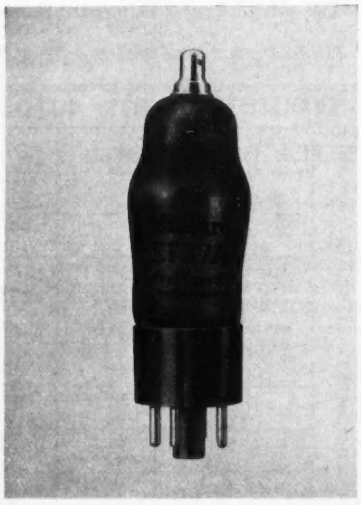

Television Wobbulator

THE Type 36 Television Wobbulator has been designed for television manufacturers and those engaged on the development of television receivers. It is a mechanically swept complete visual alignment equipment enabling accurate response measurements to be taken. The display is viewed on a 3½ in. cathode ray tube. The frequency modulation system sweeps 10 Mc/s. ; 40-50 Mc/s or 8-18 Mc/s. outputs are switched from the front panel. A trace expansion system is incorporated enabling any 3 Mc/s. to be expanded to occupy the full 7 cms. "X" trace. The output is monitored and continuously variable from 1 μV to 100 mV ; the output impedance of the attenuator being 75 ohms. The signal from the receiver under test is fed to a calibrated "Y" amplifier, which at maximum gain, requires an input of 1 volt to produce a 4 cms. "Y" trace. For production use master curves may be fixed into the tube mask and receivers aligned by unskilled personnel to these master curves. The size of the instrument is height 14½ in. width 10¼ in., length 16 in.

The Type 39 Wobbulator is a similar instrument for use on Birmingham receivers. R.F. frequency 55-65 Mc/s. I.F. frequency 20-30 Mc/s.

Samwell and Hutton,
Combine Works,
Ilford, Essex

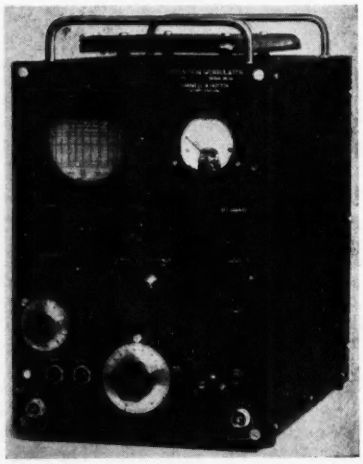

Equipment

tronic apparatus, components and supplied by the manufacturers.

Dynamic Balancing Machine

THIS apparatus is designed to measure out of balance components on mechanisms weighing up to 7 lb. and gives direct readings, electrically indicated. The machine consists of a cradle upon which is mounted the test specimen, the cradle being supported so that it can vibrate freely in all planes. Electrical voltages are derived from the supports of the cradle and are amplified to a suitable level. The test piece is rotated at speeds from 1,000 to 3,000 r.p.m. by means of a belt driven from an electric motor mounted above the cradle. Any out of balance components will cause the supporting structure to vibrate, and generate a voltage proportional to the amplitude of the vibration. The high gain amplifier will measure vibrations as small as 0.000025 inches, and by means of a filter network only those vibrations that occur once each revolution are recorded.

By means of switches on the control unit the amount and angle of unbalance are indicated. A stroboscopic light source produces a pulse of light which is electrically timed to coincide with the unbalance of the rotating work piece. By means of a scale mounted on the workpiece only the appropriate section is shown up by the light source.

Dawe Instruments, Ltd.
Hanwell, London, W.7.

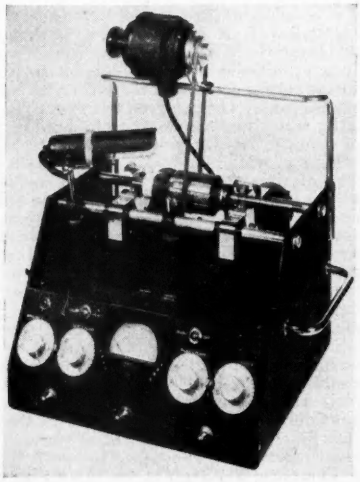

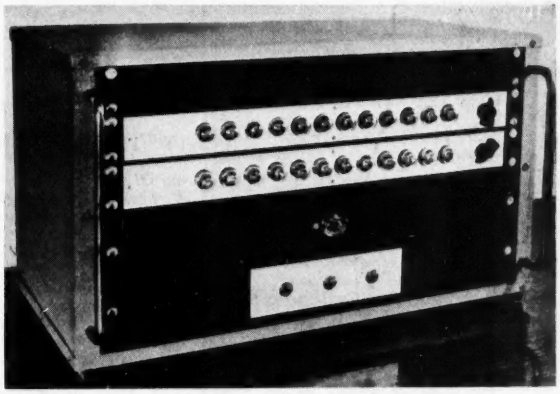

Indicator Lamp

(Shown below)

THE new Bulgin signal lamp bush and holder can be fitted to panels up to $\frac{1}{2}$ in. thick, only a single fixing hole being required. The thermo-plastic lens can be supplied in a variety of colours, and, in quantity, bushes can be given any of the usual metal finishes to order. Normal stocked finish is polished nickel plating. The holder takes mains voltage 15 watt lamps, S.E.S. cap type (B.S.98/E.14).

A. F. Bulgin & Co. Ltd.
By-Pass Road,
Barking, Essex.

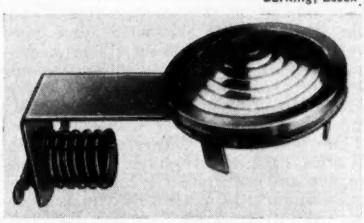

The Elliott Potentiometer Recorder

(Illustrated right)

THE Elliott Potentiometer Recorder is a continuous type high speed recorder, taking only three seconds to move across the chart. It has been simply designed, consisting of interchangeable sub-assemblies, which facilitate servicing, and combines a magnetic inverter and oil-immersed slide wire.

On the same panel is mounted the Elliott pneumatic control system, which is very flexible. The various control elements can be accommodated in the recorder casing as shown, or situated in the plant where convenient.

The system incorporates the Elliott "Pneulec" electro-pneumatic transformer which converts electrical signals into proportionate pneumatic signals, and the Elliott "Trimod" pneumatic controller to produce proportionate integral and rate functions. Features of the controller are: sealed system, calibrated setting and exceptionally long integral times.

Elliott Brothers (London) Ltd.
Century Works S.E.13.

Electronic Counter—Batcher Type E.C.B. 144

THIS instrument (illustrated above) has been developed to meet the demand for an apparatus at a reasonable price that will fill the needs of manufacturers and packers interested in the counting and batching of small articles at high speed. The maximum counting speed of which this apparatus is capable can be fully utilised only in certain scientific applications.

The E.C.B.144 will count and batch in quantities predetermined by the setting of two switches, and give visual indication of units, tens, dozens and grosses or any other combination in this range, and will automatically repeat the cycle on completion of each batch.

Batching can be effected by an electro-mechanically operated trap or gate specially designed for the articles to be batched, which diverts the stream of articles from the full container to the empty one waiting. At the same time a record of batches completed may be obtained on an electro-magnetic counter which, if required, can be positioned remote from the main apparatus.

The largest batch for which the standard model counter can be used is one gross, but the addition of one further stage will enable the instrument to operate up to 12 gross.

Sargrove Electronics Ltd.
Effingham, Surrey.

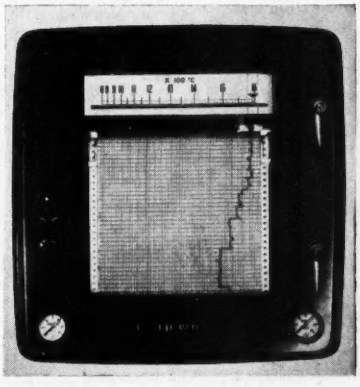

Just out

The New 8th Edition of

P. H. Brans'

RADIO VALVE

VADE MECUM 1950

The most copied book of the technical literature, giving complete information on well over 15,000 valves, as per data supplied by 247 valve-manufacturers from all over the world.

The ideal reference book for radio and television technicians, electronic engineers, servicemen, research workers, students, repairers, amateurs, etc., etc.

The book is published in 17 languages, including English. A hundred thousand copies are sold every year n 73 countries.

530 *pp.* (12" x 8") *In all libraries*

PRICE: 20/-

(*plus* 1/- *postage*)

Single copy service:

Universal Services,
16 Lyndhurst Avenue,
London, N.12.

BOOK

Terrestrial Radio Waves

By Dr. H. Bremmer. 1st Edition. 343 pp. 91 figs. Elsevier Publishing Co., distributed by the Cleaver-Hume Press. Price 42s.

PHYSICISTS and engineers concerned with the theory of the propagation of radio waves round the earth often find themselves interested in the relations between the radio theory and the theory of allied phenomena in other branches of physics. For example, when considering diffraction round the earth they are reminded of problems concerning the interaction of a parallel beam of radiation with a conducting or dielectric sphere, and the application of the results to scattering from small particles, either in colloidal solutions or in the rainbow. The "skip distance" phenomenon encountered when waves are propagated through the ionosphere presents interesting analogies to the optical phenomena near a caustic; when the magnetic field of the earth is taken into account the ionisphere becomes doubly refracting so that it is possibly to use the theoretical methods applicable to the propagation of light in crystals, and the deduction of the wave- and ray-velocities is of importance. The propagation through an inhomogenous medium has many analogies to the problems encountered in wave-mechanics.

In this book, "Terrestrial Radio Waves," Dr. H. Bremmer attempts to survey and correlate the highly mathematical work of Watson, Love, Eckersley and Millington, van der Pol and Bremmer. Wedensky, Booker and others, also to show how the radio problem is related to those other physical problems mentioned above. It seems to the reviewer that those who worked on these theories of radio-wave propagation were primarily mathematicians, interested more in the mathematical methods than in physical explanations, and it was hoped that the author of the present book would have been able to explain the essentials of the problems by some simple physical arguments. He has not, however, found this possible. Instead he outlines the various types of mathematical approach, shows how they are related, and then points out what the mathematical results mean physically. This is interesting, and valuable, but does not help the physicist very much: he is left in the position of having to accept the very complicated mathematics, though he is given some help in their interpretation.

To those interested in the different types of theory the book should be a useful guide, though it will be necessary for the reader to consult the original papers before he can follow the arguments in detail. For others who are interested in results the numerous graphs which summarise the theoretical deductions in several important special cases will be useful. Those who think, as the reviewer does, that there is usually a simple explanation of natural phenomena, will be disappointed that such complicated mathematics is still necessary in order to explain the behaviour of the waves, and will feel that there is still room for someone to simplify the presentation of the theories. They will, however, be grateful to the author for giving them some idea of how nature works by drawing attention to the similarities between diverse physical phenomena.

In at least two important fields the book contains material hitherto unpublished. In one of these the reflexion of very long waves from a sharply-bounded ionosphere in the presence of a magnetic field is computed: in the other the focusing and absorbing effects of the ionosphere on radio waves incident from outside the earth is discussed. Other topics include diffraction round the earth and propagation through an inhomogeneous medium, treated by ray and wave methods, and with applications both to tropospheric and ionospheric propagation.

J. A. RATCLIFFE.

Waveforms

By Britton Chance, V. Hughes, etc. M.I.T. Radiation Laboratory Series; volume 19. 785 pages. McGraw Hill. 85s.

IN a book of this magnitude (nearly 800 pages) it is difficult in a short review to do full justice to its contents. It is essentially a reference book to be consulted on occasion rather than to be read minutely from cover to cover. The title, which has the merits and demerits of brevity, hardly gives an idea of the contents, which deal with the generation of almost every (at present) useful wave form from sinusoidal to pulse, and their amplitude and time selection, comparison and discrimination. Sections are also included on amplitude and time modulation and demodulation, on methods of multiplying and dividing frequency, and on the use and control of electrical waveforms in performing the equivalent of simple (counting) and complicated (differentiation, square root, etc.) mathematical operations. Full acknowledgement is made to the considerable contributions made in this field by British workers and in particular to F. C. Williams.

There are 23 chapters, two appendices

REVIEWS

(on the negative capacitance and the cathode compensated amplifier), a two-page glossary and an appendix. Chapter 1 affords an excellent introduction, indicating the relationship to preceding and succeeding volumes in the M.I.T. series. Volume 17 on components is stated to be an essential companion to this volume if the precision circuits described are to be constructed. In the latter part of this chapter (further amplified in Chapter 2) F. C. Williams discusses pulse shaping by linear networks (*R*, *L* and *C*) and by non-linear devices such as valves, using the cause and effect diagrams originally presented in his paper* to the I.E.E. Radiolocation Convention. Chapter 3 considers the use of non-linear circuits in performing the basic operations of amplitude and time selection, discrimination and comparison of waveforms.

A succinct and comprehensive account of sinusoidal waveform generators is provided in Chapter 4; the subject matter, ranging from crystal controlled radio frequency oscillators to phase shift and bridge controlled audio frequency oscillators, is of interest to radio engineers generally. Short duration waveforms (generally less than 0.1 microseconds) having abrupt changes of shape are dealt with in the next two chapters, the first of which treats multivibrators and phantastron type circuits. This and the next chapter on blocking oscillator and delay-line pulse generators really cover some of the ground surveyed in Volume 5, but the method of presentation here will have greater appeal to the general circuit designer and student. In chapter 7 is a description of the generation and uses of triangular waveforms, and the next is devoted to special types of waveforms made up of a mixture of linear and curved shapes, which in their variety and possibilities will stagger the "plain" electrical engineer.

Amplitude selection, comparison and discriminate circuits are reviewed in the ninth chapter. The importance of the diode (often in association with a cathode follower) as a selector is emphasised, and it is shown that comparison is achieved by using the input wave (or a modified form of it) to trigger some regenerative device, and that discrimination involves the difference between two voltages as the operational feature. Time selection requires a "gating" pulse and chapter 10 deals with circuit arrangements.

The difficulties associated with the amplification of waveforms containing D.C. components can be lessened by using the wave to modulate a carrier which is then amplified and later demodulated. A useful summary of methods of modulation and a table of performance of recommended circuits are found in Chapter 11. The title of Chapter 12 "Electromechanical Modulators" is liable to shock many readers, (if they have forgotten the carbon microphone), since it deals with transducing systems for changing a mechanical displacement into a directly related electrical amplitude variation. The performance of four devices, potential divider, variable coupling transformer, variable capacitor and photoelectric system, are considered and their performances summarised in a table. The importance of time modulation (Chapter 13) needs no stressing for radar work, and its usefulness is being exploited more and more for measurement and computing.

The basic principles of amplitude and time demodulation of non-sinusoidal waveforms are shown in Chapter 14 to be the same as for sinusoidally varying signals. Thus amplitude modulation requires a peak detector and for time demodulation an area detector (often known as a counter) is necessary, or the time variation must be converted first into an amplitude modulation.

The next three chapters on sinusoidal and pulse recurrence frequency division will be of particular interest to designers of television synchronising pulse generators. Electrical circuits for performing mathematical operations are examined in Chapters 18 and 19. A description of oscilloscope techniques follows and contains nothing new to users of this instrument.

The storage of information on a special photo-sensitive surface in a cathode-ray tube is a comparatively new development and Chapter 21 makes no pretensions to completeness. The characteristics of electrical delay lines (for delays up to about 10 microseconds) and of supersonic delay lines (giving delays up to several milliseconds) are discussed in the last two chapters.

For the circuit designer this is one of the most useful books in the whole of the M.I.T. Radiation Laboratory Series, and is one that the teacher of advanced circuit technique and the television specialist will certainly want to possess and use.

K. R. STURLEY

* Introduction to Circuit Techniques for Radiolocation. *Journal I.E.E.* Part IIIA. March, 1946.

Electronics in the Factory

Edited by Prof. H. F. Trewman. 183 pp. 63 figs. Pitman & Sons, Ltd. 20s. net.

THIS book has been compiled by members of the staff of Electrical and Musical Industries, Ltd.—in fact the company's monogram appears on the cover. Nevertheless, it must not

CHAPMAN & HALL

Just Published

A
SYMPOSIUM ON ELECTRONICS
IN RESEARCH AND INDUSTRY
Papers read at the First Electronics Symposium of the Scientific Instrument Manufacturers' Association, 1948.
Edited by
A. G. Peacock.
Introduction by
SIR EDWARD APPLETON, K.C.B., F.R.S.
216 pages, 112 figures, 16s. net.

THE TECHNIQUE OF RADIO DESIGN
by
E. E. Zepler,
Ph.D.
(*Second Edition Revised*)
412 pages, 283 figures, 25s. net.

37, ESSEX STREET, LONDON, W.C.2.

THESE ARE IN STOCK

ELEMENTS OF SOUND RECORDING, by John G. Frayne and H. Wolfe. 51s. Postage 1s.

THE TECHNIQUE OF RADIO DESIGN, by E. E. Zepler. 25s. Postage 9d.

CATHODE RAY TUBE TRACES, by Hilary Moss. 10s. 6d. Postage 6d.

RADIO ENGINEERING—Vol. 2, by E. K. Sandeman. 40s. Postage 9d.

INTERNATIONAL RADIO TUBE ENCYCLOPAEDIA, edit. B. B. Babani. 42s. Postage 9d.

RADIO RECEIVER SERVICING AND MAINTENANCE, by E. J. G. Lewis. 8s. 6d. Postage 5d.

BRIMAR RADIO VALVE AND TELETUBE MANUAL. 4s. Postage 3d.

SUPERHETERODYNE TELEVISION UNIT FOR LONDON AND BIRMINGHAM AREAS. 2s. 6d. Postage 2d.

RADIO VALVE DATA, compiled by *Wireless World.* 3s. 6d. Postage 3d.

THE RADIO AMATEUR'S HANDBOOK, by A. R. R. L. 15s. 6d. Postage 9d.

TELEVISION SERVICING MANUAL, by E. N. Bradley. 4s. 6d. Postage 3d.

THE ELECTRONIC MUSICAL INSTRUMENT MANUAL, by A. Douglas. 18s. Postage 6d.

We have the finest selection of British and American radio books. Complete list on application.

THE MODERN BOOK COMPANY
(Dept. E.12)
19-23, Praed Street, LONDON, W.2

A NEW

FIELDEN TECHNIQUE

in micro-measurement and control

FOR ANY INDUSTRIAL OR RESEARCH PROBLEM RESOLVABLE INTO MINUTE ELECTRICAL CAPACITANCE CHANGE

ACTUATION BY PROXIMITY of solid or liquid conductors or insulators to an electrode terminating a co-axial cable

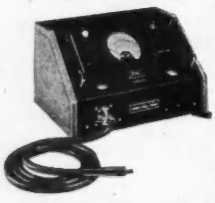

The Fielden Proximity Meter—Sensitivity 0.01 pF—indicates minute capacitance changes, whether caused by very small mechanical displacement or dielectric change. It measures, for instance, strains in structures, it gauges components to less than 0.00001 in., monitors sheet, foil and wire sizes, measures liquid and other levels precisely, monitors dimensions and compositions, compares dielectric properties of non-conducting liquids, etc. It does what is impossible mechanically and, in many fields, surpasses all other micro-measurement methods.

The Fielden Tektor-Sensitivity 0.25 pF—is a unique, stable, high-speed capacity relay which solves many problems of counting, temperature control, level control of liquids and solids, and so on where simple direct-switching is impossible.

Please send for Specification FE/5 to the

SPECIALISTS IN INDUSTRIAL ELECTRONIC EQUIPMENT

Fielden

(ELECTRONICS) LIMITED

HOLT TOWN : MANCHESTER

Tel: ARDwick 2619

BOOK REVIEWS *(continued)*

be considered as a one-sided book; the contents are well representative of all branches and manufacturers, and the fact that E.M.I. have put their imprint on it is perhaps a guarantee of the quality of the contents.

One may say that at the start that survey is very well carried out. The writing is clear and not too tedious to to be read by the directors, general managers, and production engineers to whom the book is addressed. The chapters are headed: Time Delay and Timing Circuits; Counting Equipment; Motor Control; Voltage and Current Regulation; Electronic Heating; Welding Control; Servo Mechanisms; Photocell Applications; and there are concluding chapters on electronics in medicine and chemistry, not forgetting strain gauges, moisture indicators and ultrasonics.

The introductory chapter gives an excellent picture of the relations between the electronic engineer and the factory engineer, and points out the necessity of the works electrician having some knowledge of electronic devices in order to save time and expense in calling in the expert for comparatively trivial faults. In the main text, no attempt is made to make the examples exhaustive—such a task would belong to an encyclopaedia of electronic applications—but the descriptions of typical installations are sufficiently thorough to suggest other applications to specific problems. And, of course, there is an experienced consultation service available to those who have such problems (*vide* p. 189).

A good book, which should enhance the reputation of E.M.I. Institutes and its able Professor.

G. PARR

Discharge Lamps for Photography and Projection

by H. K. Bourne, M.Sc., M.I.E.E., F.R.P.S. Chapman & Hall, 36s.

THE steadily growing application of discharge lamps to photography, projection and lighting in general has created a demand for a book which describes the lamps and gives performance data for various conditions of operation. Mr. Bourne's book not only fulfils this demand and discusses a number of specific applications but also gives a clear account of discharge lamp development and design, so that the reader can assess the suitability of these sources for various purposes.

The subject matter is systematically presented and the numbering of the paragraphs on the decimal system makes for easy reference. Chapters 1 to 4 give the lighting requirements for photography and projection and the behaviour of tungsten filament lamps and carbon arcs for these purposes.

Chapters 5 to 11 are devoted to mercury vapour discharge lamps. It is always difficult to decide how much of the theoretical and fundamental background should be discussed, but Mr. Bourne includes just sufficient of the physics of the discharge to explain the important characteristics in simple terms. For those who wish to delve deeper into the theory there is an excellent bibliography at the end of each chapter.

There are one or two minor criticisms of the theoretical matter: in paragraph 5.3 page 67, a little more explanation is needed to correct the impression that luminous efficency is directly related to the values of excitation potentials at which visible light is emitted.

In paragraph 10.3 page 196 the size of the anode relative to the cathode in a D.C. lamp is attributed to a higher voltage drop at the anode: surely the explanation lies in the fact that the current is carried mainly by electrons which must dissipate energy when they arrive at the anode. However, these are small details in an otherwise excellent account.

Mr. Bourne's long experience in the field of high pressure mercury vapour lamps has enabled him to treat this section of the book with particular thoroughness. This is fortunate, as so little of this work has been published in book form in the English language. Moreover, the small size, high intensity sources which the mercury arc can provide are of special interest for photography.

In Chapter 12 flash discharge lamps are described and compared with photo flash bulbs. Repeated flash or stroboscopic lamps are also discussed with reference to a number of commercially available equipments.

Among the applications of discharge lamps in Chapter 13 perhaps the most important is film studio lighting. The compact source lamp is already in use in the studios in considerable numbers. The lamps and equipment are basically as described, and changes since this book was prepared are mainly towards simplification of the equipment and the development of larger units.

In addition to clear diagrams and illustrations on almost every page, the book contains useful appendices including definitions of terms used in photography and illumination and a collection of photographic and optical data.

In short, Mr. Bourne's book is thoroughly recommended not only to the photographic or projection expert but also to lighting engineers in general.

G. G. ISAACS

NOTES FROM THE INDUSTRY

Television Servicing Certificate Examination

The Radio Trades Examination Board and the City and Guilds of London Institute announce that the first Television Servicing Certificate Examination will be held on May 2 and 4, 1950, and the practical examination on a date to be announced later. In this instance London will be the only centre and it may, therefore, be necessary to restrict the number of entries. Admission to the examination is limited to candidates who have passed one of the following examinations:—

(i) The Radio Servicing Certificate Examination held jointly by the City and Guilds of London Institute and the Radio Trades Examination Board,

(ii) the examination in Radio Servicing held by the Radio Trades Examination Board from 1944 to 1946,

(iii) the examination in Radio Service Work of the City and Guilds of London Institute held from 1938 to 1947,

(iv) the "third year" examination in Radio Service Work of the Union of Lancashire and Cheshire Institutes,

(v) the examination in Radio Servicing held prior to 1944 by the British Institution of Radio Engineers,

(vi) the examination in Radio Servicing held prior to 1944 by the Scottish Radio Retailers' Association.

The closing date for the examination is Thursday, 15 December, 1949. Regulations and entry forms are obtainable on application to the Secretary of the Board, 9 Bedford Square, London, W.C.1.

Large Screen Home Television

Philip's Electrical, Ltd., recently demonstrated an adaptation of their projection unit for domestic television receivers (described in ELECTRONIC ENGINEERING, *21*, 259, 1949) to give a four by three feet image on a home-ciné type of screen. The only modifications required to give this size of picture is a change of Schmidt corrector lens and an increase of projectory distance to nine feet.

Tube life is estimated to be normal (i.e., 1,000 hours) and replacements will not cost more than 50 per cent of direct-viewing tube prices. The complete projection receiver will probably retail at a similar price to present 12-in. tube console models.

The Science Museum Televisor

The Science Museum have honoured us by accepting a working model of the Home Built Televisor for exhibition in the Electronics Section. The model specially built for this purpose by the designers, has now been installed, and may be seen during the normal Museum hours in the Radio and Television Section of the gallery above the main entrance.

Educational Films

The British Electrical Development Association has produced four more educational films explaining in the simplest terms, and with commendably clear demonstrations, the theory of electrical phenomena.

"What is Electricity" describes in two parts the electronic composition of conductors, and how this facilitates the flow of current.

"Electricity and Movement" shows how electricity was harnessed to supply one of man's most essential needs, rotary motion.

"Putting Free Electrons to Work" continues the theory of electron movement to explain the action of simple valves.

"Alternating Current and Direct Current" outlines the difference between the two types of electric mains supplies and why D.C. has lost favour compared with A.C.

Twelve of these instructional films have now been completed. Each lasts about ten minutes and is available on both 16 mm. and 35 mm. film on free loan to responsible organisations. Application should be made to the Secretary, British Electrical Development Association, 2 Savoy Hill, London, W.C.2.

HOME SUBSCRIPTIONS

To ensure receiving ELECTRONIC ENGINEERING regularly readers are advised to order through their newsagent. If any difficulty is experienced, please write to the Circulation Department at 28 Essex Street, Strand, W.C.2.

DOLLAR SUBSCRIPTIONS

Attention is drawn to the reduction in the rates from $5.50 to $3.75 for new and renewal annual subscriptions to ELECTRONIC ENGINEERING.

We ask our subscribers in the dollar areas to bring this opportunity of reading the journal of the British electronic industry at so small a cost to the notice of their friends.

B.B.C. Engineering Staff Changes

The B.B.C. announce that it has decided to split the Operations and Maintenance Department of the Engineering Division into two parts. One part, consisting of the Studio, Transmitter, Recording and Lines Department, will continue to be in the charge of Mr. L. Hotine, Senior Superintendent Engineer.

Mr. M. J. D. Pulling, M.A., M.I.E.E., has been appointed to take charge of the other part, the Television Department, with the title of Senior Superintendent Engineer, Television.

Mr. D. C. Birkinshaw's post as Superintendent Engineer, Television, is not affected.

Timula Cement

Timula Cement is being used by a number of wireless set repairers for refixing loose top-cap terminals and loose bases of radio valves with satisfactory results.

Timula adheres strongly to metal, glass and wood, and self-sets in a short time to a porcelain-like hardness. It withstands high and intermittent heat, without contracting, cracking or crumbling.

Brochure on Apprenticeship

The English Electric Company has, for many years, paid particular attention to evolving a good scheme for the training of apprentices and students in all branches of engineering. Among the 35,000 workers employed by the "English Electric" group of companies, there are some thousands of apprentices of all types, and the management have thought that, in view of the present need which exists to reinforce the ranks of trained technical personnel, it would be appropriate to summarise their activities in this direction in a brochure.

To preserve the high standard of technical skill necessary to maintain and enhance Britain's engineering prestige, it is felt desirable to do everything possible to draw attention to some of the facilities offered to young men to take up engineering training, and this booklet gives them a glance of what is happening in the English Electric group.

Salvaging Electrically Twinned Quartz

In the above article the following corrections should be made:

P. 413. In Fig. 5(c) the diagrams for before treatment and after treatment should be interchanged.

P. 414. In Fig. 8 the remainder of the caption after 22 Kg-cm should be omitted.

DECEMBER MEETINGS

Institution of Electrical Engineers

Unless otherwise stated, all meetings are held at the Institution of Electrical Engineers, Savoy Place, London, W.C.2.

Radio Section

Date: December 7. Time: 5.30 p.m.
Lecture: "Solar Radio-Frequency Radiation."
By: J. L. Pawsey, M.Sc., Ph.D. (Read by J. S. Hey, M.B.E., M.Sc.)
Date: December 19. Time: 5.30 p.m.
Informal Lecture: "The Acoustics of Studios and Auditoria."
By: W. Allen.
Secretary, Institution of Electrical Engineers, Savoy Place, W.C.2.

Cambridge Radio Group

Date: December 13. Time: 6 p.m.
Held at: Cambridgeshire Technical College.
Address by: R. T. B. Wynn, C.B.E., M.A., Chairman of the Radio Section.
Secretary: G. E. Middleton, M.A., University Engineering Laboratory, Cambridge.

South Midland Centre

Date: December 5. Time: 6 p.m.
Held at: The Town Hall, Birmingham.
Lecture: Faraday Lecture on "Radar."
By: R. A. Smith, M.A., Ph.D.
Date: December 20. Time: 6 p.m.
Held at: James Watt Memorial Institute, Great Charles Street, Birmingham.
Lecture: "Electricity in the Service of Man."
By: P. Dunsheath, C.B.E., M.A., D.Sc.
Secretary: H. Hooper, British Electricity Authority, 53 Wake Green Road, Moseley, Birmingham 13.

North Staffordshire Sub-Section

Date: December 9. Time: 7 p.m.
Held at: King Edward Grammar School, Stafford.
Discussion on: "Rectifiers."
Opened by: J. E. Boul.
Secretary: D. Smith, B.Sc.(Eng.), 82 Beatty Hall, Stone, Staffs.

The Royal Society

Date: December 15.
Lecture: The Wilkins Lecture for 1949.
By: Professor E. N. da C. Andrade, F.R.S.
The Secretary, The Royal Society, Burlington House, London, W.1.

Inc. Radio Society of Great Britain

Date: December 16. Time: 6.30 p.m.
Held at: Institution of Electrical Engineers, Savoy Place, W.C.2.
Annual General Meeting.
General Secretary, New Ruskin House, Little Russell Street, W.C.1.

Institute of Physics

Manchester and District Branch

Date: December 9. Time: 7 p.m.
Held at: The New Physics Theatre, University of Manchester.
Lecture by: Professor P. M. S. Blackett, F.R.S.
Secretary: Dr. F. A. Vick, O.B.E., F.Inst.P., Physics Department, The University, Manchester 13.

Electronics Group

Date: December 13. Time: 5.30 p.m.
Held at: The Institute's House, 47 Belgrave Square, S.W.1.
Lecture: "The Nervous System as an Electrical Machine."
By: Dr. W. Grey Walter.
Secretary: G. W. Warren, F.Inst.P., Research Laboratories, The G.E.C., Ltd., Wembley, Middx.

Institute of Navigation

Date: December 16. Time: 5 p.m.
Lecture: "Radar Charts."
By: Lt. Commander P. G. Satow, D.S.C., R.N.
Executive Secretary: M. W. Richey, The Institute of Navigation, c/o. Royal Geographical Society, 1 Kensington Gore, London, S.W.7.

British Institution of Radio Engineers

London Section

Date: December 15. Time: 6.30 p.m.
Held at: London School of Hygiene and Tropical Medicine, Gower Street, W.C.1.
Lecture: "Electronics in Aircraft Design."
By: A. L. Whitwell.
The General Secretary, 9 Bedford Square, London, W.C.1.

North-Eastern Section

Date: December 21. Time: 6 p.m.
Held at: Neville Hall, Newcastle-upon-Tyne.
Lecture: "A Review of the Basis of Electronics."
Secretary: c/o. 26 Denewell Avenue, High Heaton, Newcastle-upon-Tyne.

South Midlands Section

Date: December 15. Time: 7 p.m.
Held at: The Technical College, the Butts, Coventry.
Lecture: "H.T. Supply for High Power Transmitters."
By: Mr. Lane.
Secretary: C. Stokes, B.Sc., 6 Esterton Close, Coventry.

Scottish Section

Date: December 1. Time: 6.30 p.m.
Held at: Electrical Department, The University, Glasgow.
Lecture: "Electronics in Industry."
By: A. A. M. Turnbull.
Secretary: A. A. M. Turnbull, 68 Launderdale Gardens, Glasgow W.2.

Television Society

Constructors' Group

Date: December 8. Time: 7 p.m.
Held at: Cinema Exhibitor's Association, 164 Shaftesbury Avenue, W.C.2.
Lecture: "Baird Television Receivers."
By: P. Wigley, B.Sc. (Scophony-Baird, Ltd.)

Main Society

Date: December 30.
Held at: Cinema Exhibitor's Association, 164 Shaftesbury Avenue, W.C.2.
Exhibition and Social.
Secretary: T. M. Lance, 35 Albemarle Road, Beckenham, Kent.

Bedford Centre

Date: December 14. Time: 7.30 p.m.
Held at: Flying Services Club, St. Mary's Street, Bedford.
Lecture: "Television Aerial Problems."
By: E. M. Lee.
Date: December 30. Time: 7.30 p.m.
Held at: Flying Services Club, St. Mary's Street, Bedford.

Discussion Group

Secretary: M. Bradbury, 36 Grafton Road, Bedford.

Midland Centre

Date: December 5. Time: 7 p.m.
Held at: Lecture Hall (1st Floor), The Crown Restaurant, Corporation Street, Birmingham.
Open Meeting.
Secretary: W. Summer, 31 Beech Road, Bournville, Birmingham 30.

Bristol and South Western Centre

Date: December 6.
Held at: The Royal Hotel, Bristol.
Lecture: "Television Aerials and Interference Problems."
By: E. M. Lee.
Secretary: A. G. Williams, 43 Horse Street, Chipping Sodbury, Bristol

Radar Association

Date: December 6. Time: 7 p.m.
Held at: Albert Tavern, Victoria Street, London, S.W.1.

Monthly Meeting

Hon. Secretary, Technical Committee: J. C. Warren, 57 Gallows Hill, Kings Langley, Herts.

The Institution of Post Office Engineers

Date: December 6. Time: 5 p.m.
Held at: Institution of Electrical Engineers, Savoy Place, W.C.2.
Lecture: "Some Recent Developments in Telegraph Apparatus."
By: R. O. Carter, M.Sc., D.I.C., A.C.G.I., A.M.I.E.E., and L. K. Wheeler, B.Sc., A.M.I.E.E.
Secretary: W. H. Fox, A.M.I.E.E., Engineer-in-Chief's Office, (T.P. Branch), Alder House, London, E.C.1.

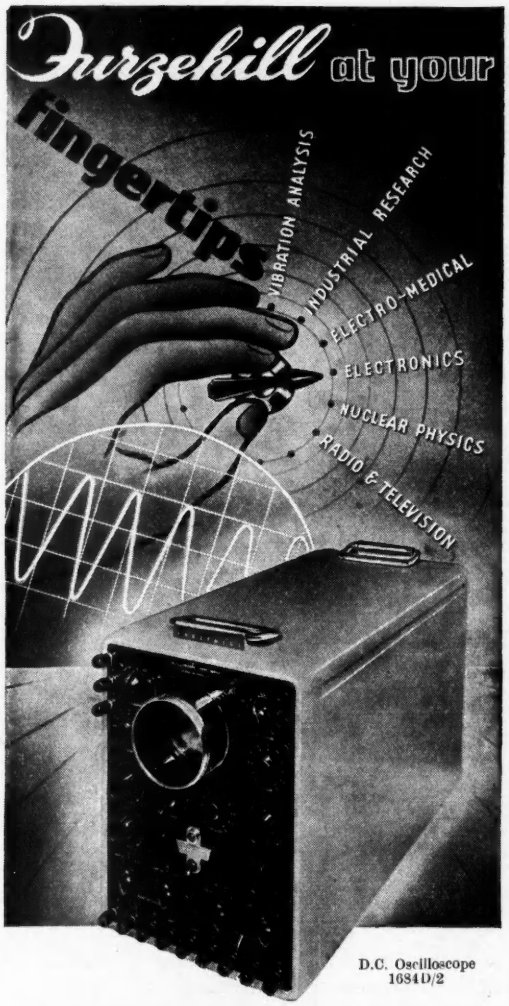

D.C. Oscilloscope 1684D/2

AN EXAMPLE from the Furzehill range of fine instruments is this high-grade oscilloscope for industrial radio and television applications. Both axes have identical d.c. coupled high sensitivity amplifiers with symmetrical inputs and a level frequency characteristic from Zero to 3 Mc/s. Particularly valuable features are the instantaneous action of the shift controls, expansion of the time-base scan from ½ to 5 screen diameters, negligible phase shift in the amplifiers and automatic amplitude-limited synchronisation.

For full details of this, and other instruments in the Furzehill range, write for our new illustrated catalogue.

Furzehill

FURZEHILL LABORATORIES LTD.
BOREHAM WOOD, HERTS. ELStree 1137

BLIND ALLEYS
ON THE EBB TIDE...

The sting in the salt air is likely to be intensified by the language of harbour masters should a vessel approach any anchorage as casually as the holiday-maker in his dinghy.

Hazards of 'getting in' safely have been reduced considerably by the electronic development of the 'blind approach' to harbour or aerodromes in foul weather.

To the manufacturer of electronic and electrical equipment fogged or grounded by transformer trouble - Parmeko extend the guiding hand of the specialist to ensure successful landing.

Parmeko

of Leicester (Tel. 32287)

Makers of Transformers for the Electronic and Electrical Industries

Of Interest

TO ALL ELECTRICAL AND WIRELESS ENGINEERS

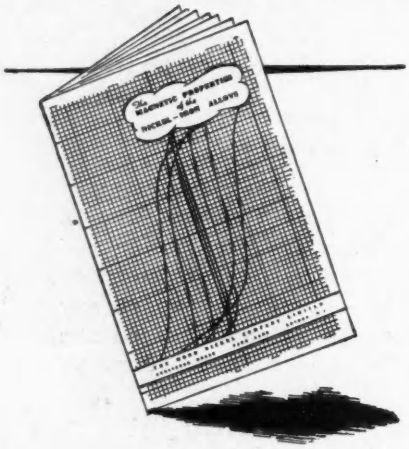

THIS BOOK dealing with the magnetic properties of the nickel-iron alloys will be sent free on request. It contains information on:

1. NON-MAGNETIC AND WEAKLY-MAGNETIC ALLOYS
Non-magnetic ferrous engineering materials—Temperature compensation alloys.

2. HIGH PERMEABILITY NICKEL-IRON ALLOYS
General and historical—Early uses: cable loading—Further development: transformers, screens, dust-cores, etc., radar, specialized alloys.

3. MAGNETOSTRICTION
General—Echo sounding—Frequency control.

4. PERMANENT MAGNETS
Development: Alni, Alnico, Alcomax—Properties—Sintered magnets—Applications—Ductile alloys.

Application should be made to:

THE MOND NICKEL COMPANY LIMITED

Sunderland House, Curzon Street, London, W.1 12/QA/3

TELCON
TELEVISION AERIAL DOWNLEADS

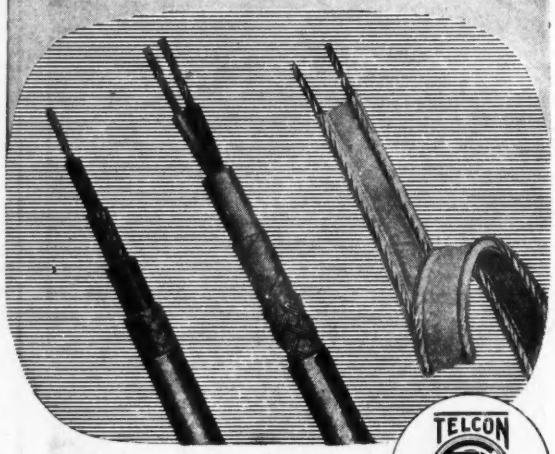

TELCON TM YOUR GUARANTEE

ALL TELCON CABLES are scientifically *designed.* EVERY COIL is TESTED to ensure that the Impedance and Attenuation characteristics are uniformly maintained within close limits. This background of technical knowledge and care in manufacture is a *guarantee* that Aerial Installations using TELCON TELEVISION CABLES are a source of *maximum signal* and *satisfaction.* There is a TELCON CABLE designed for every Receiver and for all reception areas—PT1M Co-axial for high signal strength and AS 60M Co-axial for "fringe" areas are two examples.

The TELEGRAPH CONSTRUCTION & MAINTENANCE Co. Ltd
Founded 1864
Head Office: 22 OLD BROAD ST., LONDON, E.C.2
Telephone: LONdon Wall 3141
Enquiries to: TELCON WORKS, GREENWICH, S.E.10
Telephone: GREenwich 3291

LABORATORY INSTRUMENTS

♦

The practical exploitation of piezo-electric phenomena in relation to all forms of acoustic, ultrasonic and vibration problems has long been the special care of the acos research section. Today acos have made available a series of laboratory instruments, including WIDE RANGE MICROPHONES, VIBRATION PICK-UPS, WATCH-RATE RECORDER MICROPHONES, PRESSURE STANDARDS and ARTIFICIAL EARS. This announcement, one of a series, briefly describes the acos

ARTIFICIAL EARS

The **acos** Artificial Ear, S.I.3, has been designed to meet the requirements laid down by the Medical Research Council in their Report No. 261, Hearing Aids and Audiometers. The cavity is 3 ccs, with an acoustic resistance of 100 ohms in parallel. This resistance is obtained by connecting two semi-infinite tubes of suitable cross-section and terminated with an acoustic damping network. An adaptor is arranged to reduce the volume of the cavity to 1½ ccs, and at the same time to remove one of the resistance tubes from the circuit. The microphone response is maintained to well beyond 15 Kc/s.

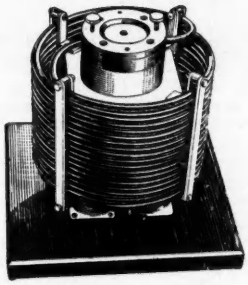

Full technical data of the Artificial Ear or any other of the acos instruments will gladly be sent on request.

COSMOCORD LIMITED
ENFIELD, MIDDLESEX PHONE: ENFIELD 4022

NILO K for use in seals in medium-hard boro-silicate glasses.

NILO 48 for thermostats operating up to 450°C. and seals in certain soft glasses.

NILO 42 for oven thermostats, lead-in wires for lamps and valves.

NILO 36 for clock pendulums, precision gauges, surveyors' tapes, etc.

NILO ALLOYS FOR CONTROLLED EXPANSION

The Nilo alloys are nickel-iron and nickel-cobalt-iron alloys with small controlled coefficients of thermal expansion.
Nilo 36 has a coefficient of expansion approaching zero at atmospheric temperatures.
Nilo 42 has a slightly higher expansion, but it holds this figure at higher temperatures than Nilo 36.
Nilo 48 has a coefficient of thermal expansion similar to that of certain soft glasses, and may be used at temperatures up to about 450°C.
Nilo K has a coefficient of thermal expansion similar to that of medium-hard boro-silicate glasses. These glasses, having good thermal shock resistance, are widely used in the construction of electronic equipment.

**Nilo is a registered trade mark*

For further particulars, write to . . .

HENRY WIGGIN & CO. LTD
WIGGIN STREET, BIRMINGHAM, 16

36/HA/2

DAWE

Wave ANALYSER

TYPE 705A

A comprehensive equipment for measuring the component frequencies and amplitudes of electrical waveforms. Covers the frequency range 50–16,000 c/s. and voltage range 1 mV to 500 V. Special feature: Selectivity continuously variable.

Data forwarded on request :—

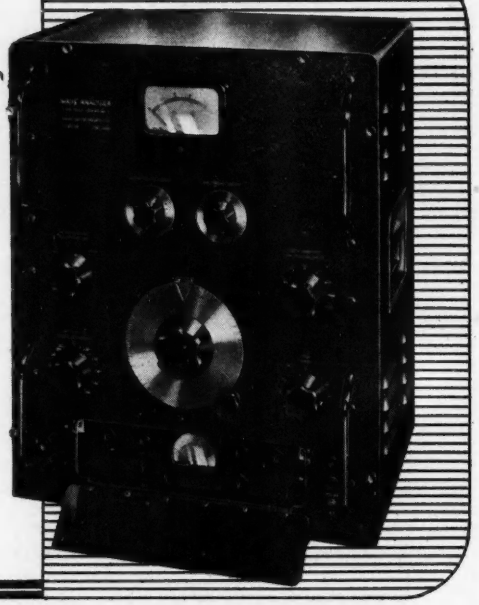

DAWE INSTRUMENTS LTD

130 UXBRIDGE ROAD, HANWELL, LONDON, W.7. EALing 6215

● *Visit the ELECTRONICS CENTRE, our new London Showrooms, at 83, Piccadilly, W.1. MAYfair 4613*

Somerford Chosen Again!

THESE ARE THE SPECIFIED TYPES

For the TELEVISOR

R.135A. C.247
C.268 HV.357

For the RECEIVER

R.110B C232B
OP. 748B

For the "Electronic Engineering" HOME-BUILT TELEVISOR AND FREQUENCY MODULATED RECEIVER

We are proud to announce that the designers of these two famous receivers used "Somerford" Transformers and Chokes in their Prototype models.

Chosen for their accuracy and reliability "Somerford" components contribute in no small measure to the success of these outstanding designs.

The constructor can be assured of obtaining the very high standard of reliability of which these sets are capable only by using the specified components—"Somerford" is your safeguard.

Full details and specifications may be had upon request.

GARDNERS RADIO Ltd

SOMERFORD . CHRISTCHURCH . HANTS

Telephone: CHRISTCHURCH 1025

Which switch fits the niche?

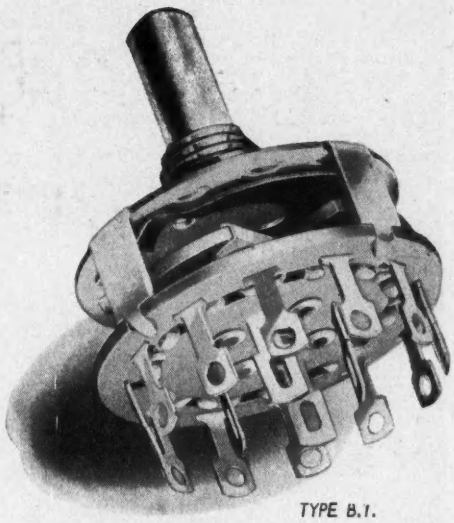

TYPE B.T.

By the time that has rolled round your tongue half a dozen times the Type B.T. Switch could be fitted! It's that sort of switch—small, compact, designed specially to fit easily into small spaces. It'll save you a lot of trouble. We have recently included some new features. Here they are—

- **The contact blades are fixed in a new way. This makes them completely rigid all the time.**
- **The drive spindle is positioned definitely in the wafer. This provides double bearing.**
- **Steady contact resistance.**
- **Improved insulation between contacts.**
- **Positive contact.**
- **Self-cleaning action.**

All these make the Type B.T. a better switch —more efficient and lasting. In fact just the switch you need for limited space and simple switching.

WALTER SWITCHES—MADE FOR LIFE

Walter Instruments LIMITED

WALTER INSTRUMENTS LIMITED, GARTH ROAD, LOWER MORDEN, SURREY. TELEPHONE: DERWENT 4421-2-3

C.M.C.47

Made in Britain - - - acclaimed by U.S.A. Television Manufacturers

ERSIN Multicore

TECHNICAL ADVANTAGES: MULTICORE SOLDER

- Three separate cores of flux eliminate possibility of no flux in a portion of the wire, which may occur in single cored solder. Guaranteed continuity of the flux stream prevents "dry" joints.
- Although there are three cores of flux in Multicore, the total percentage of flux to solder is less than many single cored solders.
- Very rapid melting results from the multiple core construction which provides thinner walls of solder than are found in same gauge single cored solder.
- Ability to tin rapidly produces perfect joints with less solder. Greater coverage per pound.

ERSIN FLUX

- Ersin Flux is exclusive to Multicore and will not be found in any other solder. It is high grade rosin, homogeneously activated.
- Ersin Flux has a vigorous fluxing action and possesses the non-corrosive and protective texture of the original rosin.
- Soldered joints made with Ersin Flux do not corrode even after prolonged exposure to any degree of humidity. It has been tested under climatic conditions ranging from the Arctic to the Tropics.
- Free from objectionable odour. Non-toxic in use.

Technical information and samples for manufacturers on request.

The economy and reliability of Ersin Multicore Solder are preferred by almost all British Television Manufacturers. Pye of Cambridge, have used it exclusively for 10 years.

One of the 20 U.S.A. Television factories where British made Ersin Multicore Solder is used—the DuMont factory at Newark, U.S.A.

INTERNATIONALLY PREFERRED BY LEADING TELEVISION MANUFACTURERS

The Finest Cored Solder in the World.

For television servicing and use in the home, we particularly recommend ERSIN MULTICORE SOLDER 60 40 alloy, 18 S.W.G., available in Size 1 Cartons, Ref. C.16018, containing 60 ft. of solder—5 - each retail.

MULTICORE SOLDERS LTD.

MELLIER HOUSE, ALBEMARLE STREET, LONDON, W.1. ● REGent 1411

UNBREAKABLE RUBBER MOULDED PLUG

MOULDED PLASTIC SOCKET

BERYLLIUM COPPER CONTACTS

Control by PAINTON

& COMPANY LTD

KINGSTHORPE • NORTHAMPTON

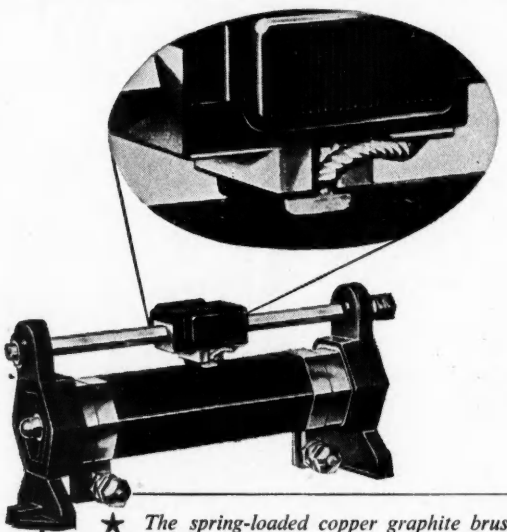

PERFECT CONTACT★

To ensure perfect contact at all temperatures and to prevent undue wear of the windings BERCO sliding rheostats and potentiometers are fitted with a spring-loaded copper graphite self-lubricating brush operating on the flat surface of a hexagonal solid drawn steel tube.

Open, protected or ganged types are available in a wide variety of sizes. Graded windings can be supplied for special applications.

★ *The spring-loaded copper graphite brush is held accurately in alignment in a diecast holder, providing a permanently lubricated contact at high temperature. The pigtail connection ensures current is not carried by the springs.*

BERCO

SLIDING RESISTANCES

THE BRITISH ELECTRIC RESISTANCE CO. LTD.
QUEENSWAY, PONDERS END, MIDDLESEX. *Phone:* Howard 1492. *Grams:* Vitrohm Enfield.

BR. 6013 - THX 1

Quality ELECTRONIC COMPONENTS

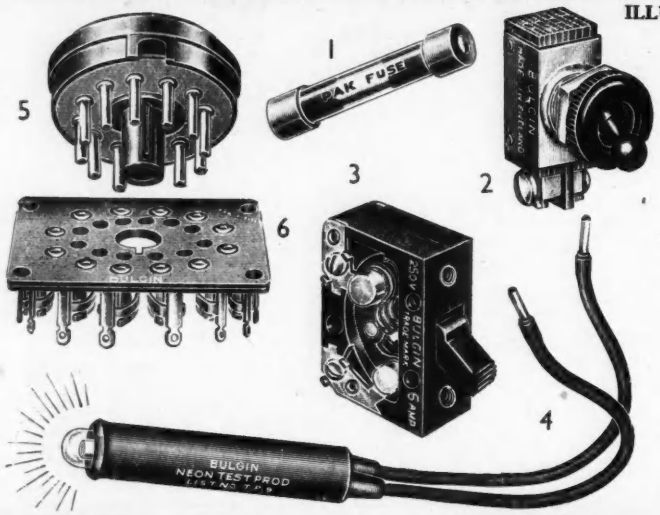

ILLUSTRATED CATALOGUE
1/- POST FREE

1 Pak Delay Fuses have unique surge-handling capacity. They withstand 75-100 per cent overload for approximately 120 seconds, and blow instantly at 200 per cent or more. Available in ranges, for carrying 250mA-2.0A. LIST NOS. PAK 1-6

2 This new version of a famous model shows some of the varieties obtainable on all **Bulgin** switches. This 1-pole M.-B., for 6-250V, 3A max., circuits has moulded ball dolly and front ring—obtainable in colours. LIST NO. S.478

3 Popular lever-action heavy duty 2-pole M.-B. Switch, moulded structure. For above circuits, at 12-6A max. respectively. LIST NO. S.377

4 This new and useful model is heavily shrouded in flexible tough rubber; leads flexible, with ferruled tips. Suitable for testing 200-250V. supplies; indicating polarity and leakage, etc. Removable lamp; replacements available. LIST NO. T.P.9

5 C.R.T. Plug; 12 pins and spigot, and lam. board socket to mate. The plug is moulded in polished black plastic, and takes up to 3A per pole. The socket has silver-plated contacts and integral solder-tags. LIST NOS. P.245 and V.H.80 respectively.

BULGIN A. F. BULGIN & CO. LTD.
BYE-PASS ROAD, BARKING
Telephone: RIPpleway 3474 (5 lines)

CERAMICS *by* U.I.C

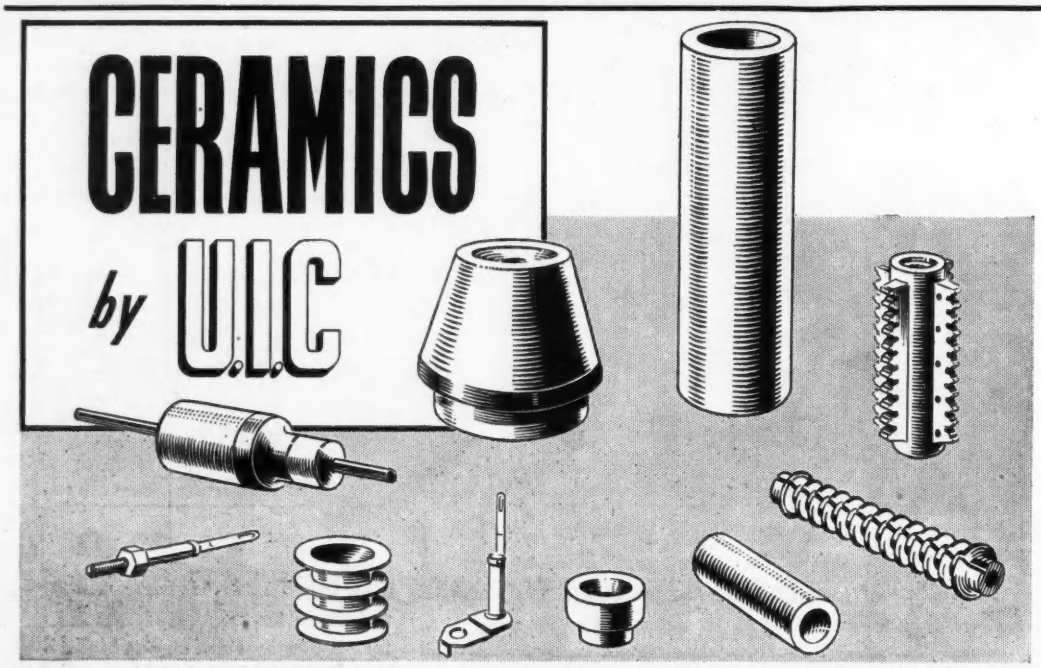

UNITED INSULATOR COMPANY LTD · TOLWORTH · SURBITON · SURREY · ENGLAND
Cables: Calanel, Surbiton Telephone: Elmbridge 5241

BALDWIN

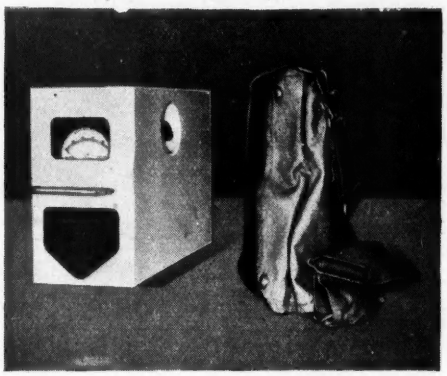

GAMMA RADIATION DETECTOR

(TYPE PP)

A light-weight tropicalised dry-battery-operated Geiger-Müller detector with both audible and visible indication; the latter on an instrument dial. It is useful for prospecting for any radio-active minerals and also for finding lost radium containers, etc.

May be used in the hand or slung in the haversack

BATTERY LIFE APPROXIMATELY SIX MONTHS

BALDWIN INSTRUMENT CO., LTD., DARTFORD, KENT.

Agents for Lancashire, Cheshire and Derbyshire:

F. C. ROBINSON & PARTNERS, LTD., 308, DEANSGATE, MANCHESTER, 3.

WODEN

QUALITY COMPONENTS SPECIFIED FOR

"ELECTRONIC ENGINEERING" HOME BUILT TELEVISOR

	s.	d.
E.H.T. TRANSFORMER, POTTED TYPE		
4 KV. 5mA. 0-2-4V 1.5A.	Price 65	0
5 KV. 5mA. 0-2-4V 1.5A.	Price 72	6
MAINS TRANSFORMER, POTTED TYPE		
350V-0-350V 250mA. 6.V 6A. 4V 8A. 4V 3A. 0-2-6.3V 2A.	Price 98	6
SMOOTHING CHOKES		
5 Hy 250mA.	Price 29	0
10 Hy 80mA.	Price 17	0

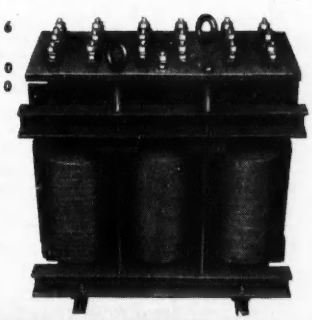

We also manufacture transformers from **10VA** to **100KVA** for all types of Electronic Equipment. We are pleased to co-operate on any special designs required, and we already supply many prominent manufacturers.

The Transformer shown is typical of our larger types. Rated at 6,000V 30KVA, it is designed for R.F. Heating Equipment.

Send for latest Catalogue to:

WODEN TRANSFORMER CO LTD

MOXLEY ROAD · BILSTON · STAFFS TEL: BILSTON 41959

WEBB'S

Christmas suggestion

If you're doing the giving, any of your radio-minded friends will prefer a Webb's Globe of the World to anything else. If you expect to be on the receiving end this Xmas, why not drop a hint in the right quarter that Webb's Radio Globe at 50/- (47/6 to callers) will be much more acceptable than the usual selection of socks and ties?

COMMUNICATIONS RECEIVERS

We advise our friends that our stocks of Eddystone '640' receivers are now sold. The new Eddystone '750,' price £45, will be available soon, details free on request. As regards the Eddystone '680,' price £85, the outstanding performance of this specialised receiver has resulted in Export orders taking the bulk of production, but WEBB'S usually have a demonstration model and orders are being booked for rotational delivery. Also we often have interesting second-hand bargains in receivers of U.S.A. and British origin—inquiries invited, though Webb's offers do not remain long unsold!

WEBB'S *Radio*

TWO INFORMATIVE BOOKS

by an expert on Loudspeakers and reproduction in general—G. A. Briggs.

'LOUDSPEAKERS"

88 pages, 36 illustrations (3rd edition now ready), 5/- (*or* 5/3 *post free*). The book that tells you the HOW and WHY of good reproduction.

SOUND REPRODUCTION"

144 pages, 120 illustrations. Fine art paper, bound full rexine. Gives the practical results of many careful and precise experiments on L.S. cabinets, also chapters on various aspects of sound-reproduction. Part 2 deals with recordings, needles and record wear, tracking, surface noise, microgroove recording, etc. 7/6 (*or* 8/- *post free*).

NEW 'Leak'

MOVING COIL PICK-UP

Call and hear this outstanding addition to our large range of disk reproducing apparatus. Price with ruby stylus and transformer, **£14 . 10 . 8.**

Webb's Radio, 14, Soho St., Oxford St., London, W.1

Phone: GERrard 2089. Shop Hours 9 a.m.—5.30 p.m. Sats. 9 a.m.—1 p.m.

ALEC Davis SUPPLIES Ltd.

18, TOTTENHAM COURT ROAD, LONDON, W.1

Tel. MUSeum 2453. Shop Hours: Mon. to Fri. 9—5.30. Sats. 9—1.

T.C.C. (Post Free)

2pF, 10pF, 15pF, 47pF. 500 V. D.C. wkg.		Ceramic disc type	... ...	...	1/3
0.001μF	500V. D.C. wkg.	Metalmite	CP30S	... ...	1/9
0.002μF	350V. D.C. wkg.	,,	CP30S	... ...	1/9
0.005μF	350V. D.C. wkg.	,,	CP31N	... ...	1/8
0.01μF	350V. D.C. wkg.	,,	CP32N	... ...	1/8
0.02μF	350V. D.C. wkg.	,,	CP33N	... ...	1/9
0.05μF	350V. D.C. wkg.	,,	CP35N	... ...	2/-
0.1μF	350V. D.C. wkg.	,,	CP37N	... ...	2/3
500pF	350V. D.C. wkg.	Micadisc	CM30	... ...	1/6
1μF	350V. D.C. wkg.	Picopack	CE30N	... ...	2/6
2μF	350V. D.C. wkg.	,,	CE30G	... ...	2/6
20μF	12V. D.C. wkg.	,,	CE30B	... ...	2/6
0.001μF	6KV. D.C. wkg.	Visconal	CP55QO	... ...	4/6
0.01μF	5KV. D.C. wkg.	,,	CP56QO	... ...	7/6
0.1μF	2KV. D.C. wkg.	,,	CP56X	... ...	7/6
01.μF	7KV. D.C. wkg.	,,	CP58QO	... ...	15/-

CHOKES (Post Free)

10Hy	75mA	150 ohms	Size 2½"×1½"×1¼" high ...	4/9
10Hy	80mA	250 ohms	,, 2¾"×2"×2" high (E.E. spec.) ...	12/6
10Hy	100mA	300 ohms	,, 2¼"×2¼"×3¼" high—shrouded ...	9/-
10Hy	150mA	200 ohms	,, 2¼"×3¼"×3¼" high—shrouded ...	10/6
15Hy	150mA	160 ohms	,, 3½"×2½"×3¼" high—shrouded ...	19/6
20Hy	120mA	400 ohms	,, 3¼"×2½"×3½" high—shrouded ...	19/6
30Hy	40mA	750 ohms	,, 2⅞"×2¼"×3½" high—open ...	12/6
50Hy	20mA	1500 ohms	,, 2⅞"×1½"×2" high—open ...	5/6

ALL "E.E." TECHNICAL BOOKS IN STOCK

TRANSFORMERS (Post, 9d. extra)

4.0 volt 2 amp., centre tapped	Pri 200/230V. 50 c/s.		8/6
4.0 volt 2 amp., not centre tapped	,, 200/230V. 5 c/s.		7/6
6.3 volt 6 amp., centre tapped	,, 200/250V. 50 c/s.—shrouded		16/-
6.3 volt 1½ amp. not centre tapped	,, 200/230 V. 50 c/s.—open ...		7/6
5.0 volt 3 amp., not centre tapped	,, 200/230V. 50 c/s.—open ...		10/6
12 volt. 1 amp., not centre tapped	, 200/230V. 50 c/s.—open ...		10/6
250-0-250V. 80mA ; 6.3V. tapped	4V. 4A ; 5V. tapped 4V. 2A. Pir 200/250V. 50 c/s.		20/-
300-0-300V. 60mA ; 6.3V. 2A ; 5V. 2A.	Pri 200/250V. 50 c/s.		19/6
1750V. 4mA ; 4V. 2A C.T. ; 4V. 2A C.T. ; (for rectifier)	Pri 230V. 50c/s.		35/-
Heater Auto Transformer	0-4V. 3A-5V. 2A ,, ...		6/-
,, ,, ,,	0-4V. 3A-6.3V. 2A		6/-

VALVES (Post 6d. extra). All prices include Purchase Tax.

Mullard	EA50	... ...	12/10	Mazda	Pen45	... ...	12/10
,,	EB91	... ...	12/10	,,	Pen46	... ...	18/3
,,	EBC33	...	11/7	,,	T41	... ...	12/10
,,	EC52	... ...	18/3	,,	UU8	... ...	18/3
,,	EF37	... ...	14/-	,,	U22	... ...	18/3
,,	EF50	... ...	21/4	,,	6K25	... ...	12/10
,,	EL33	... ...	12/10	,,	6P28	... ...	21/4
,,	EN31	... ...	21/4	Cossor	45IU	... ...	18/3
,,	HVR2 or 2A	...	24/4	,,	S130	... ...	7/6
,,	KT61	... ...	12/10	Csram	PX4	... ...	16/6
,,	PL33	... ...	12/10	,,	U14	... ...	11/-
,,	PL38	... ...	24/4	Brimar	3S4;	... ...	14/-
				Tungsram	6X5	... ...	10/9

FULL POSTAL FACILITIES. PLEASE ADD POSTAGE.

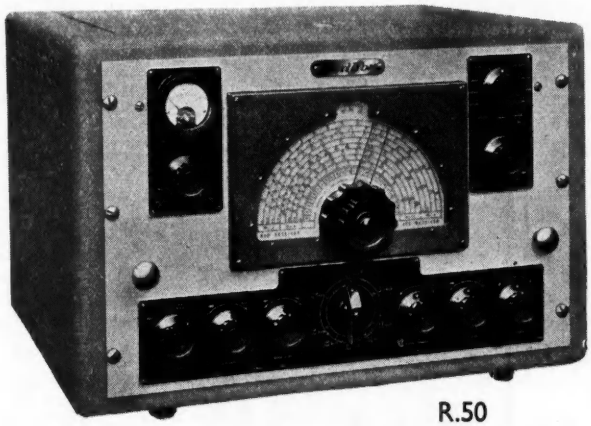

Supreme Communications Receiver

R.50

COMMUNICATIONS RECEIVER

This high-grade communications receiver incorporates the most highly developed techniques in modern receiver design. Five degrees of selectivity, including a crystal gate and crystal filter are provided, and the sensitivity is such that an input of between 1-5 microvolts gives a signal/noise ratio of at least 10 dB over the entire frequency range of 13.5 to 26 kc/s and 95 kc/s to 32 Mc/s. Separate power units for A.C. or D.C. operation are available.

COMMUNICATIONS
Redifon
Radio

REDIFON LIMITED, BROOMHILL ROAD, WANDSWORTH, S.W. 18

DESIGNERS & MANUFACTURERS OF RADIO COMMUNICATION & INDUSTRIAL ELECTRONIC EQUIPMENT 'Phone: VANdyke 5691 R.C. 203

ALL-POWER

CONSTANT VOLTAGE POWER SUPPLIES

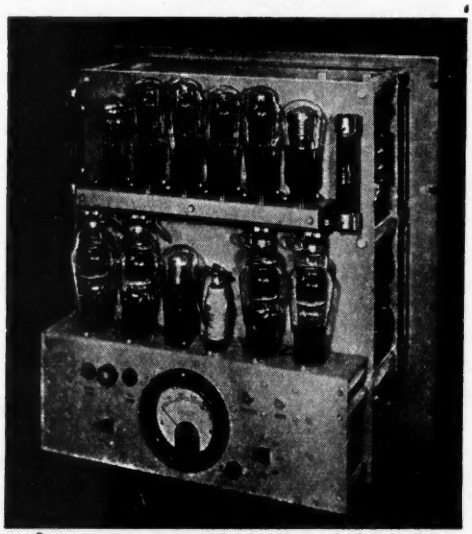

SPECIAL LABORATORY UNITS

This forward mounting Rack Unit, illustrated with cover removed, provides a constant output voltage of 300 D.C. at any current up to 600 mA. The output impedance is a fraction of an Ohm, and the residual output ripple is less than 2 mV.

This is only one of the many special Power Supply Units we are making to customers' requirements.

ALL-POWER TRANSFORMERS LTD.
Instrument Dept., Chertsey Road, Byfleet, Surrey.
Tel. Byfleet 3224-5.

Scophony BAIRD

TRANSFORMERS & CHOKES

designed and manufactured to suit your specific needs

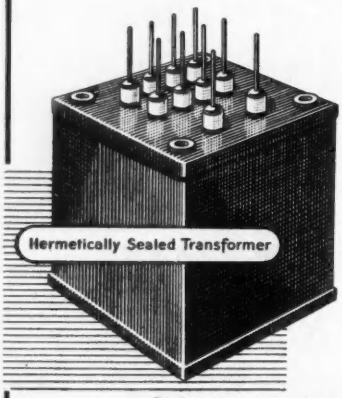

HERMETICALLY SEALED TYPES –up to 1 KVA.

OIL/AIR COOLED TYPES –up to 50 KVA (Single or 3 phase)

AUTO-TRANSFORMERS –up to 200 VA.

Send your next enquiry to:—
SCOPHONY-BAIRD LTD., (Division 6) WELLS, SOMERSET.
Telephone: WELLS 2081-5.

The active Radiochemist

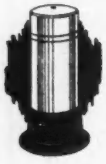

The radiochemist who expends time and energy in obtaining amplifiers, scalers, ratemeters, radiation monitors, Geiger-Müller tubes and lead castles from separate sources is certainly active. He could, however, save himself time and trouble by obtaining all nucleonic equipment from the specialist firm of E. K. Cole Ltd. We invite all radiochemists to write for our comprehensive catalogue of laboratory supplies, which includes specifications, prices and delivery dates.

Linear Amplifier type 1008A · Scaler Unit type 1009A · Power Unit type 1033A · Ratemeter type 1037A Vibrating Reed Electrometer type 1079B · C.R. Oscillograph type 1009B Radiation Monitors type 1118A, 1132A and 1043C.

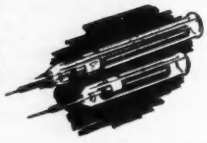

EKCO General Purpose G.M. tube · Liquid type G.M. tube · Immersion type G.M. tube · Gas Analysis G.M. tube · Square Lead Castles for End Window G.M. tube · Circular Lead Castles · Rabbit Lead Castles · Isotope Containers Interlocking Lead Bricks.

ELECTRONICS

E. K. COLE LTD., *ELECTRONICS DIVISION*, 5 VIGO ST., W.1

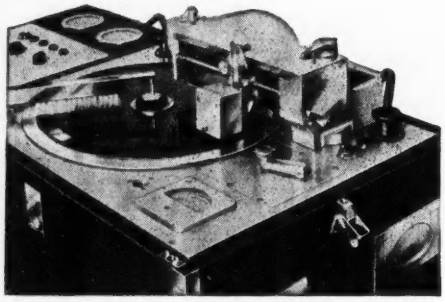

13" PROFESSIONAL

Brown - E.R.D.

High Fidelity Sound on Disc Recorders for every Purpose

Particulars from

S. G. BROWN LTD.

SHAKESPEARE STREET
WATFORD, HERTS, ENGLAND
Telephone: Watford 7241

LAMINATIONS

FOR

ALL RADIO AND ELECTRICAL USES.

IN SILICON, DYNAMO, INTERMEDIATE AND TRANSFORMER QUALITIES.

PERMALLOY, MUMETAL, RADIOMETAL.

SCREENS FOR ALL ELECTRICAL USES.

TRANSFORMER SHROUDS FOR 35 AND 74 LAMS.

GENERAL PRECISION ENGINEERS.

SHERARDISING TO THE TRADE.

ELECTRICAL SOUND & TELEVISION PATENTS LTD.

12 PEMBROKE STREET, LONDON, N.1. — TERminus 4355
2/4 MANOR WAY, BOREHAM WOOD, HERTS. – ELStree 2138

MODEL 920

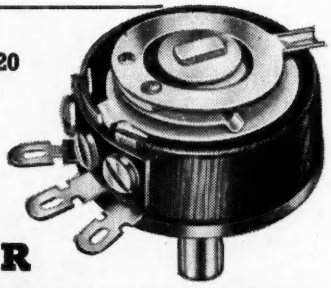

THE TAYLOR POTENTIOMETER

This wire-wound linear law potentiometer is available in a number of resistance values.

- **CONSTRUCTION.** A moulded body carries the spindle, fixing bush, potential brush and connection tags.
- **RESISTANCE.** This is wire wound on a flat strip and fitted after winding to the moulded body.
- **BRUSH.** A well-sprung and insulated brush gives good contact and smooth action under all working conditions.
- **RESISTANCE VALUES.** Standard values available from 10 ohms up to 50,000 ohms
- **WATTAGE.** The maximum dissipation over the whole resistance is 5 watts continuous.
- **FIXING.** A bush is provided for one-hole fixing on panels up to ¼ in. thick.

TAYLOR ELECTRICAL INSTRUMENTS LTD
419-424 MONTROSE AVENUE, SLOUGH, BUCKS, ENGLAND
Telephone SLOUGH 21381 (4 lines) • Grams & Cables TAYLINS, SLOUGH

'SINTREX' BRAND
ELECTROLYTIC IRON POWDER
FOR POWDER METALLURGY

Especially suitable for electro-magnetic applications, due to its exceptional purity, and supplied in a wide range of mesh gradings.

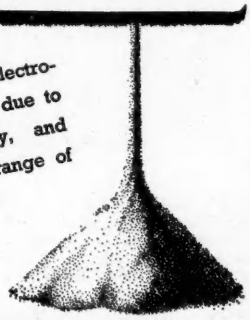

THE 600 GROUP OF COMPANIES

GEORGE COHEN SONS & CO. LTD
BROADWAY CHAMBERS LONDON, W.6
Telephone: Riverside 4141

BUILD YOUR OWN E.H.T. UNIT

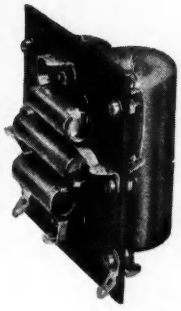

5KV, 3KV or 1·7KV
from
350–0–350 volt input using standard mains transformer and "Westeht" balanced voltage multiplier circuit

The circuit is simple, easily constructed and readily extended or adapted to follow developments in the receiving equipment. No E.H.T. transformer or R.F. oscillator and rectifier are needed and the additional burden on the mains transformer is less than 1mA.

WESTINGHOUSE
WESTALITE
36 E.H.T. RECTIFIERS

Full details are given in "The All Metal Way," a copy of which may be obtained, price 6d., from Dept. E.E.12,

WESTINGHOUSE BRAKE & SIGNAL CO., LTD.,
82, York Way, King's Cross, London, N.1.

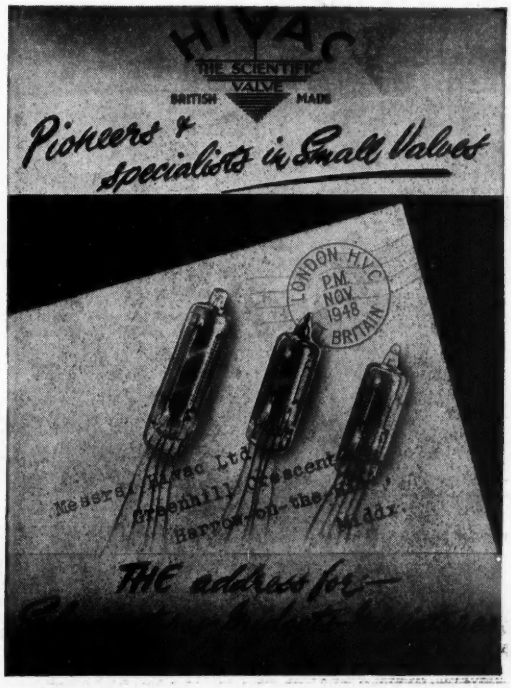

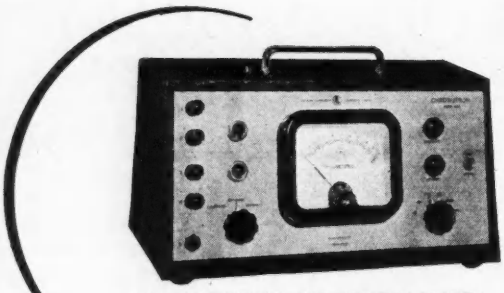

MILLISECOND MEASUREMENT

The CHRONOTRON

USED as a stop-clock for timing in the millisecond region. Controlled by relay contacts, photo-cell or any abrupt voltage change.

MODEL 25A 0-4, 10, 40, 100, 400, 1,000 Milliseconds
MODEL 25B 0-40, 100, 400, 1,000, 4,000, 10,000 Milliseconds

ELECTRONIC INSTRUMENTS LTD
IT PARADISE ROAD • RICHMOND • SURREY

VISION *in Design* . . . ADVANCE Signal Generator

Type E.2.

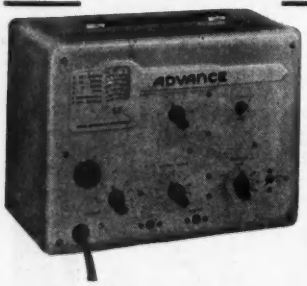

Range: 100 Kc/s.—100 Mc/s. in 6 bands.
Frequency: Guaranteed within ±1%.
Output: Approx. 1 volt unattenuated and variable from 1 μV to 100 mV into a 75 ohm load through a matched transmission line.
Stray Field: Less than 3μV at 100 Mc/s.
Illuminated Dial: Total scale length, 30 in.
Power Supply: 110 — 210 — 230 — 250 volts. 40-100 c/s.
Dimension: 9½ in. high × 13 in. wide × 8 in. deep.
Weight: 15 lb.

The Advance Signal Generator Type E2 has been designed with an eye to future developments in the Radio and Television fields. Its wide range of frequencies, from 100 Kc/s to 100 Mc/s on fundamentals, caters for the rising frequency requirements of modern radio and communications. It is a fine example of 'Advance' design and manufacture. This generator offers an instrument of laboratory standard at a price within the reach of moderate purses. The remarkable high frequency accuracy of ±1% extends over the whole range.

Send for fully descriptive leaflet.

Advance TYPE E2 SIGNAL GENERATOR

ADVANCE COMPONENTS LTD.,
Back Road, Shernhall Street, Walthamstow, London, E.17
Tel. : LARkswood 4366/7/8

AUSTINLITE GOES TO SEA

The Austinlite Rotary Switch *is part of the equipment of the new Bridlington lifeboat.*

Send for folder giving full particulars of this heavy-duty 30 amp. switch.

A Chance PRODUCT

AUSTINLITE LIMITED (*A Subsidiary of Chance Brothers Ltd.*)
Dept. A5, Lighthouse Works, Smethwick, 40, Birmingham.
Telephone : West Bromwich 1051

A NEW B.P.L. INSTRUMENT

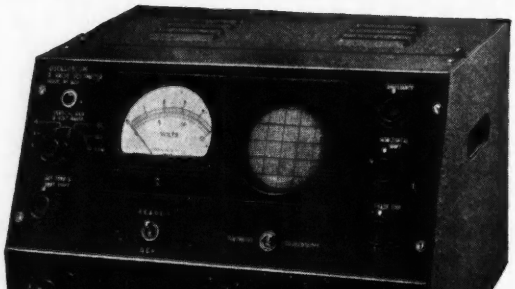

THE VOLTASCOPE—A combined valve-voltmeter and oscilloscope. VALVE-VOLTMETER — Infinite Input Resistance for D.C. ranges 0 to 300 volts. A.C. ranges 0 to 150 volts in 5 ranges. 3½-inch scale meter. OSCILLOSCOPE—3-inch screen tube provided with balanced amplifiers for Y and X plates giving a 5 times trace expansion. Maximum sensitivity 150mV/cm. Response from D.C. to 100 Kc/s.

Limited quantity available for early delivery.

BRITISH PHYSICAL LABORATORIES
HOUSEBOAT WORKS, RADLETT, HERTS.
Tel :Radlett 5674-5-6

USE **Aerialite**
RADIO CABLES
FOR COMPLETE
RELIABILITY

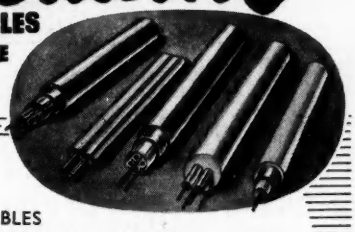

AERIALITE
COAXIAL CABLES
are manufactured under strict Laboratory conditions and to Government Specification where possible. Send for list of the full range of AERIALITE R/F Cables and Feeders.

THE D.P.O. MODEL 50—A new television Aerial. The best Aerial on the market at the lowest price. Available in two types—" London " and " Midlands," and made up for three different styles of mounting. Features: Low-Loss Insulator, Waterproof Plug Assembly, Accessibility. Easy Erection, Strength, Broad Bandwidth, Rigidity. (Prov. Patent 26255/48.) **50/-**

Aerialite LTD.
CASTLE WORKS, STALYBRIDGE, CHESHIRE.
Send for our booklet " Bring the World to your Door " for details of all AERIALITE Products.

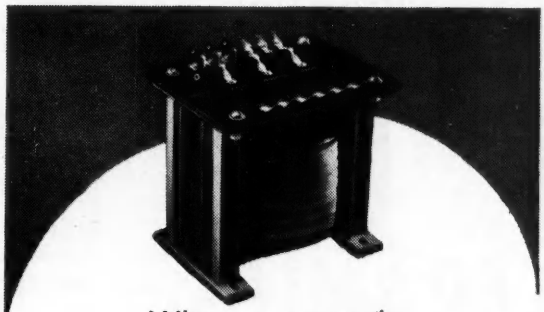

When an unusual
Specification is required

We can give you the benefit of 20 years experience in transformer construction and design. Every instrument is built to suit your most exacting individual specification.

Send your enquiries for the personal attention of our
Mr. W. Bryan Savage.

SAVAGE OF DEVIZES

Telephone : Devizes 536
SAVAGE TRANSFORMERS LTD. NURSTEED ROAD, DEVIZES, WILTS.

PLAN YOUR CAREER

RADIO · TELEVISION
and other INDUSTRIAL
ELECTRONIC subjects
ELEMENTARY & ADVANCED COURSES

WRITE FOR FREE BOOKLET summarising careers available in Electronics and giving particulars of Courses offered by E.M.I. Institutes.

The booklet contains full details of elementary and advanced HOME STUDY and DAYTIME courses in Radio, Television, Telecommunications and Industrial Electronics.

Courses ideal for those seeking recognised qualifications are also available.

Payment for tuition can be made in easy instalments if required.

Write to Dept. **XI**

E.M.I. INSTITUTES
48, GROVE PARK ROAD, LONDON, W.4. CHiswick 4417/8

Associated with
" H.M.V. "
MARCONIPHONE
COLUMBIA
ETC

W.147

HIGH VACUUM PUMP APPARATUS

for the production of metal coatings on glass

BARR & STROUD Ltd.
Works: ANNIESLAND, GLASGOW, W.3.
London Office: 15, VICTORIA ST., S.W. 1.

LOW LOSS CERAMICS

Success through constant research

CAN WE HELP YOU?

Please ask for pamphlets R.T.1 and R.T.2

PROMPT DELIVERY

TAYLOR TUNNICLIFF

(REFRACTORIES) LTD.

Albion Works, Longton, Stoke-on-Trent, Staffs.

London Office:
123 High Holborn, W.C.1
'Phones: Stoke-on-Trent 3272 and Holborn 1951

T.A.S./T.T.78

Partridge News

To your exact Specification

5 VA to 25 KVA

TRANSFORMERS—
POWER or AUDIO FREQUENCY
4 WEEKS DELIVERY

The acknowledged precision of Partridge transformers is available to you in transformers and chokes to your own specification . . . and in double quick time. Whatever your transformer need, first consult Partridge— the specialists.

★ *Note: All Partridge components are now available HERMETICALLY SEALED IN OIL*

PARTRIDGE
TRANSFORMERS LTD
ROEBUCK ROAD, KINGSTON - BY - PASS
TOLWORTH SURREY
Telephone: ELMbridge 6737-8

L.T.P. REWIND SERVICE

All rewinds are Layer Wound, Vacuum Impregnated, Pressure tested at 2,000 volts and guaranteed for three months. 48 hour service.

Enquiries:
London Transformer Products Ltd.
L.T.P. Works, Cobbold Estate, Willesden, London, N.W.10
Telephone WILlesden 6486

Varley
QUALITY RELIABILITY
MAINS TRANSFORMERS
A.F. TRANSFORMERS
SMOOTHING CHOKES
THERMAL DELAY SWITCHES
SLIDER RESISTANCES
Made by
OLIVER PELL CONTROL LTD
CAMBRIDGE ROW, BURRAGE ROAD, S.E.18.
Telephone: Woolwich 1422

MELTON METALLURGICAL LABORATORIES LTD.

Liquid Silver

IMMEDIATE DELIVERY OF GRADES FOR METALLIZING

CERAMICS, MICA, GLASS & PLASTICS

All Enquiries to our NEW ADDRESS—

42, TOWNGATE STREET, POOLE, DORSET

Telephone No. Poole 1241

POTENTIOMETERS

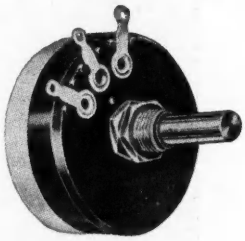

by

RELIANCE

Wire wound and Composition types, Single, Ganged, Tandem Units.

Characteristics: linear, log, semi-log, non-inductive, etc.

Full details from

RELIANCE
Manufacturing Co. (Southwark) Ltd.
Sutherland Rd., Higham Hill, Walthamstow E.17
Telephone: LARkswood 3245

MAKERS OF
R.F. E.H.T. SUPPLIES
for
TELEVISION (2-25 KV)
2-5.5 KV.....£3 15s. od.
5-8.0 KV.....£4 15s. od.
(Trade supplied)

PORTABLE NON-DESTRUCTIVE BREAKDOWN TESTER
CONTINUOUSLY VARIABLE 2-25 KV.

LABORATORY MODEL HIGH VOLTAGE GENERATOR
STABILISED 15-25 KV.

AVAILABLE IN THE NEAR FUTURE
Stabilised and variable supplies at 50 KV. and higher.
Specific enquiries invited.

HAZLEHURST DESIGNS
LIMITED.
186, BROMPTON ROAD, LONDON, S.W.3

DRAYTON MOTOR UNITS

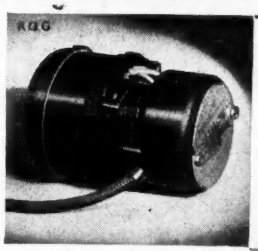

R. Q. G.
GEARLESS MOTOR UNIT

A miniature capacitator induction type motor running at 4,700 r.p.m. Normally supplied with built-in fan, condensor mounted on fan cover. Motor can be supplied totally enclosed, condensor separately mounted. For continuous or intermittent running in either direction or continuously reversed. Torque: 1.75" oz.

R. Q. R.
GEARED MOTOR UNIT

The R.Q.R. is a compact, self-contained component, consisting of the R.Q.G. motor geared to a final shaft. Supplied for continuous or intermittent running in either direction, with or without self-switching. An additional two-way switch is fitted, actuated by the final shaft, for operating auxiliary gear. Final shaft speed: 27 m.p.r. to 600 r.p.m. Torque 60" lbs. to ¼" lbs. according to speed.

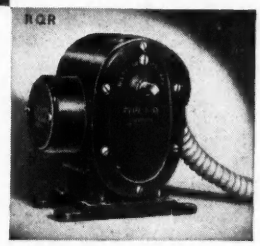

Supplied for Voltages 100/120 or 200/250 A.C. 50 cycles.

Send for List No. M 302-1 R.Q. 8

DRAYTON REGULATOR & INSTRUMENT CO. LTD.,
WEST DRAYTON • MIDDLESEX. West Drayton 2611

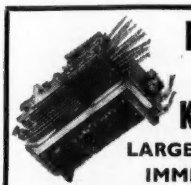

RELAYS
AND
KEY SWITCHES
LARGE EX-GOVT. STOCKS
IMMEDIATE DELIVERY

Types 600-3000 Relays — Siemens High Speed
Uniselector Switches, Carbon Insets, Telephone Components Plugs, Jacks, Handsets, Co-Axial Cables

JACK DAVIS
Dept. E.E.
30 PERCY STREET, LONDON, W.1
Phones: MUSeum 7960, LANgham 4821

AMBITIOUS ENGINEERS

HAVE YOU HAD *YOUR* COPY OF "ENGINEERING OPPORTUNITIES"?
Whatever your age or experience—you must read this highly informative guide to the best paid engineering posts. The handbook contains particulars of A.M.I.C.E., A.M.I.Mech.E., A.M.I.E.E., A.M.I.M.I., A.M.Brit.I.R.E., and other important Engineering Examinations, and outlines home-study courses in all branches of Civil, Mechanical, Electrical, Automobile, Radio and Aeronautical Engineering, Government Employment, Draughtsmanship, Building and Plastics, Matriculation, etc.
We *Guarantee*
"NO PASS — NO FEE"
If you are earning less than £10 a week you cannot afford to miss reading "Engineering Opportunities" It tells you everything you want to know to secure your future. Write for this enlightening guide to well paid posts NOW—FREE and without obligation.
BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
337a, Shakespeare House, 17/18 Stratford Place, London, W.1.
BIET

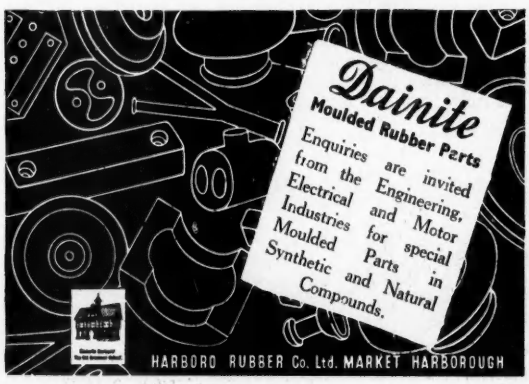
Dainite
Moulded Rubber Parts
Enquiries are invited from the Engineering, Electrical and Motor Industries for special Moulded Parts in Synthetic and Natural Compounds.
HARBORO RUBBER Co. Ltd. MARKET HARBOROUGH

INDEX TO ADVERTISERS

Advance Components Ltd. 34
Aerialite Ltd. 35
All-Power Transformers Ltd. 31

Baldwin Instrument Co., Ltd. 29
Barr & Stroud Ltd. 35
Belling & Lee Ltd. 11
Brans, P. H. 474
Bray & Co., Ltd., George 37
British Electric Resistance Co., Ltd., The 27
British Institute of Engineering Technology 37
British Insulated Callender's Cables Ltd. Cover ii
British N.S.F. Co., Ltd. 6
British Physical Laboratories 34
British Thomson-Houston Co., Ltd., The 8
Brown Ltd., S. G. 32
Bulgin & Co., Ltd., A. F. 28
Brown Ltd., S. G. 32
Bullers Ltd. 10

Chance Bros., Ltd. 34
Chapman & Hall Ltd. 475
Cinema-Television Ltd. 15
Cohen, Sons & Co., Ltd., George .. 33
Cole Ltd., E. K. 32
Cosmocord Ltd. 23
Cossor Ltd., A. C. 17

Davis Supplies Ltd., Alec. 30
Davis, Jack 37
Dawe Instruments Ltd. 24
De La Rue & Co., Ltd., Thomas 4
Drayton Regulator & Instrument Co., Ltd. 37

Edison Swan Electric Co., Ltd., The 5 and 16
Electrical Sound & Television Patents Ltd. 32
Electronic Instruments Ltd. 34
E.M.I. Institutes 35
E.M.I. Sales & Service Ltd. 19
Erie Resistor Ltd. .. .. .. Cover iv

Fielden (Electronics) Ltd. 476
Foster Transformers & Switchgear Ltd. 12
Furzehill Laboratories Ltd. 21

Gardners Radio Ltd. 24
General Electric Co., Ltd., The 7

Harboro' Rubber Co., Ltd., The 37
Hazlehurst Designs Ltd. 37
Hivac Ltd. 33
Hopton Radio 4

London Transformer Products Ltd. .. 36

Melton Metallurgical Laboratories Ltd. 36
Modern Book Co., The 475
Mond Nickel Co., Ltd., The 22
Muirhead & Co., Ltd. 9
Mullard Electronic Products Ltd. 3
Multicore Solders Ltd. 26

Painton & Co., Ltd. 27
Parmeko 21
Partridge Transformers Ltd. 36
Pell Control Ltd., Oliver 36
Pye Ltd. 18

Redifon Ltd. 31
Reliance Mnfg. Co. (Southwark) Ltd. .. 36

Sangamo-Weston Ltd. .. .. Cover iii
Savage Transformers Ltd. 35
Scophony-Baird Ltd. 32

Taylor Electrical Instruments Ltd. .. 33
Taylor Tunnicliff (Refractories) Ltd. .. 36
Telegraph Condenser Co., Ltd., The .. 14
Telegraph Construction & Maintenance Co., Ltd., The 22
Thomas (Richard) & Baldwins Ltd. .. 13
Tufnol Ltd. 20

United Insulator Co., Ltd. 28

Vortexion Ltd. .. .. Cover i

Walter Instruments Ltd. 25
Wayne-Kerr Laboratories Ltd., The .. 38
Webb's Radio 30
Westinghouse Brake & Signal Co., Ltd. 33
Wiggin & Co., Ltd., Henry 23
Wo[illegible]den Transformer Co., Ltd. 29

MEASURING
ELECTROLYTIC
LEAKAGE

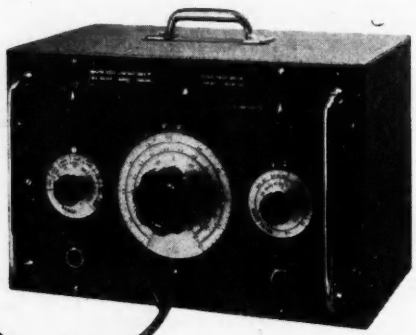

THE generally accepted maximum permissible leakage current after forming is given by I (in μ amps.) = 0.15 x C x V working. This bridge measures leakage direct at voltages of 6, 12, 25, 50, 150, 250, 350 and 450. Capacity can be measured up to 500 microfarads.

COMPONENT
BRIDGE B101

C : 5 pfd. to 500 mfd. —8 ranges.
R : 5 ohms to 500 Mohms—8 ranges.
L : 0.1 Hy. to 5000 Hys.—4 ranges.
Leakage 0 to 1.5 m/a. Q : 0 to 30.
Precision Comparator.

Price 26 Guineas.

Wayne Kerr

THE WAYNE KERR LABORATORIES LTD., NEW MALDEN, SURREY · MALDEN 2202

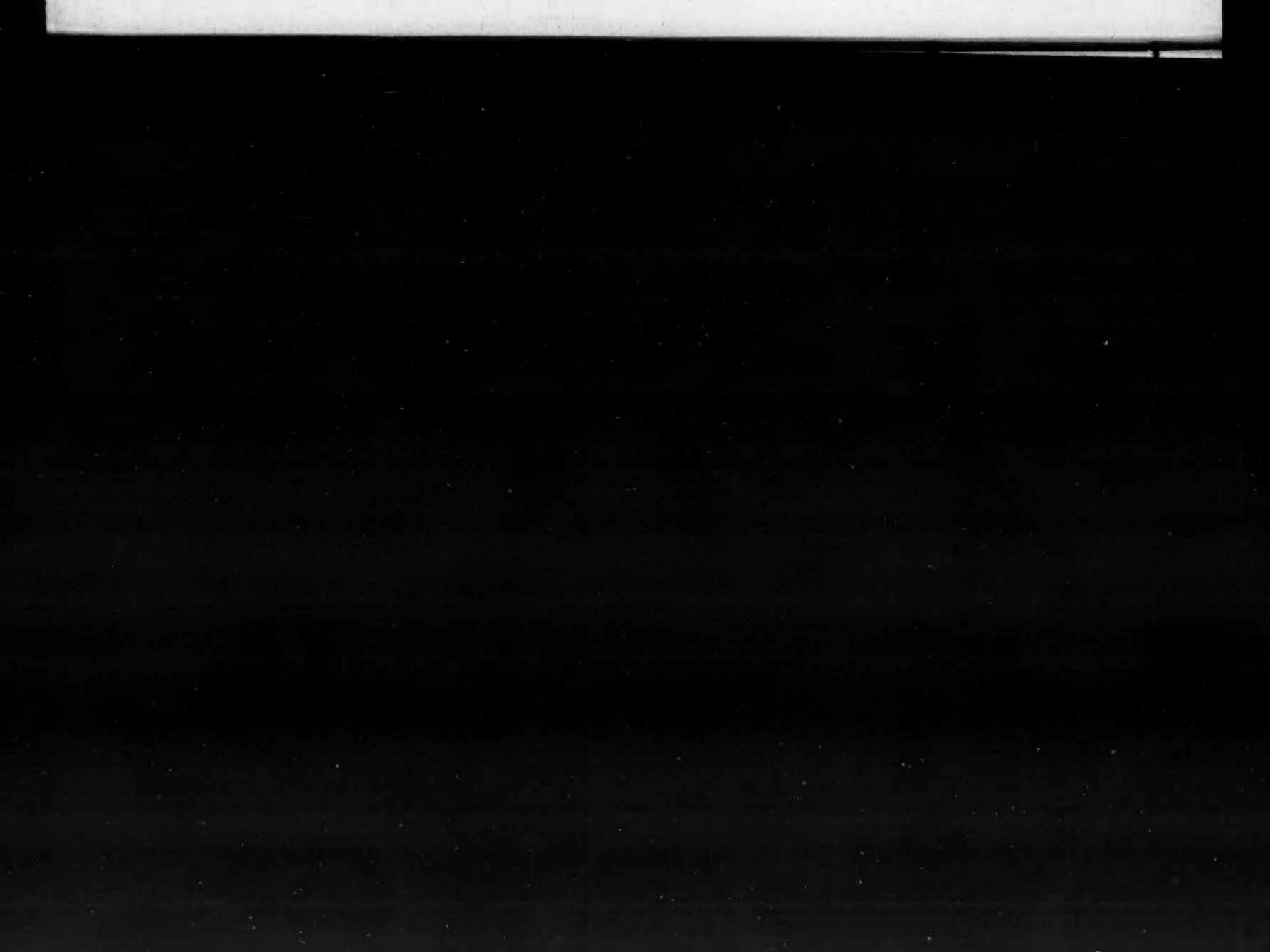

The New WESTON S75 Multi-Range Test Set

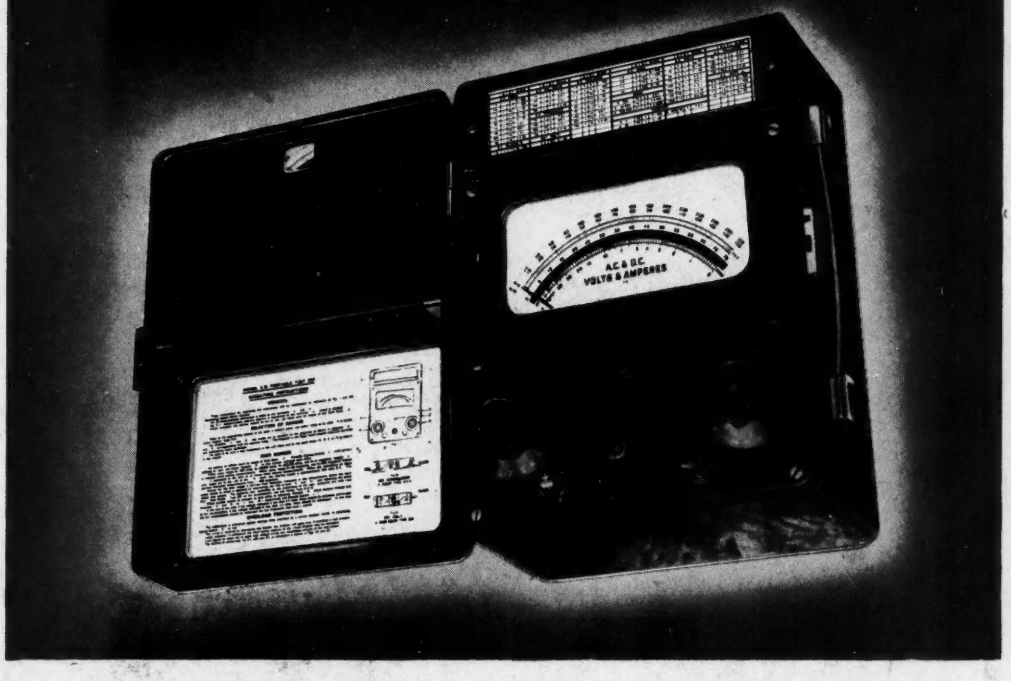

53 Ranges with Rotary Switch Selection

This new and uniquely comprehensive Test Set has 53 ranges for measuring AC and DC current and voltage, resistance and insulation. It is completely self-contained, with internal batteries to provide power for the ohms ranges and self-contained power pack for insulation measurement at 500 v. Selection is carried out by two 20-position switches. A fully protective safety device is fitted and is operative for forward or reverse overload. The 150 division 6 in. scale is uniformly divided and is fitted with an anti-parallax mirror. The set is enclosed in a handsome bakelite case and fully complies with B.S.S. No. 89 covering first grade instruments. Full details of the ranges covered and of the complete specification will gladly be supplied on request. PRICE £65

SANGAMO WESTON LIMITED

ENFIELD · MIDDX · Tel: Enfield 3434 (6 lines) and 1242 (4 lines)

201 *St. Vincent Street, Glasgow, Central* 6208 *Milburn House, Newcastle-on-Tyne, Newcastle* 26867
22 *Booth Street, Manchester, Central* 7904 33 *Princess Street, Wolverhampton, Wolverhampton* 21912

Play the Ace of Trumps against Ignition Noise

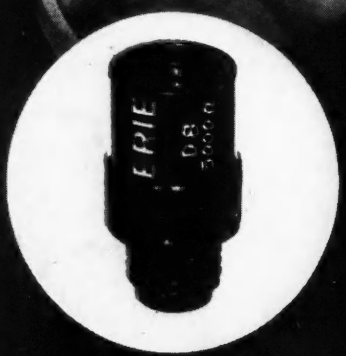

Reduced Price

1/6

Printed in Great Britain by The Press at Coombelands, Ltd., Addlestone, Surrey, for the Proprietors, Morgan Brothers (Publishers) Ltd., 28, Essex Street, Strand, W.C.2.
Registered for Transmission by Canadian Magazine Post